CQ

December 1974
$1.00

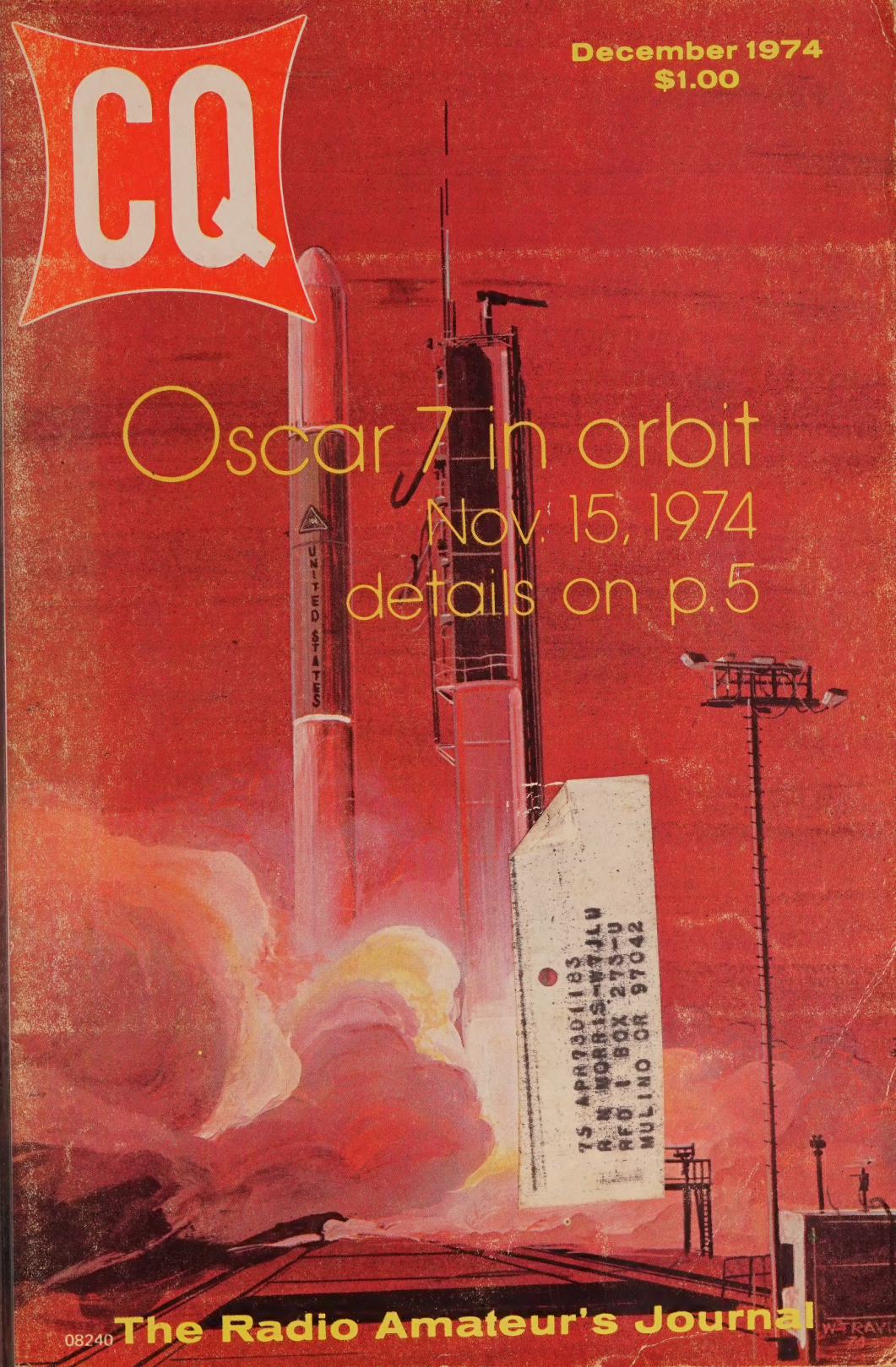

Oscar 7 in orbit
Nov. 15, 1974
details on p. 5

08240 The Radio Amateur's Journal

The Heathkit "104" Systems

FREE

NEW 1975 HEATHKIT CATALOG

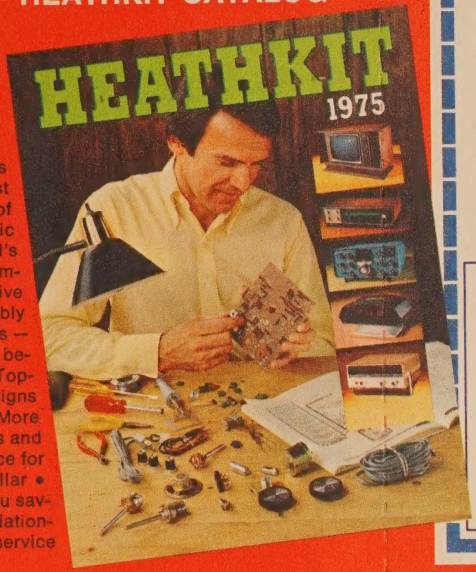

- World's largest selection of electronic kits
- World's most comprehensive assembly manuals — written for beginners
- Top-quality designs & parts
- More features and performance for your dollar
- Direct-to-you savings
- Nationwide service

PC-105

Please send my **FREE** HEATHKIT CATALOG

Name_____

Address_____

City_____

State_____ Zip_____

12-11

CQ

SEND FOR YOUR FREE COPY TODAY!

World's largest electronic kit catalog. A kit for every interest, every budget. Easy credit terms.

HEATH COMPANY

BENTON HARBOR, MICHIGAN 49022

Place
Stamp
Here

DISCOVER THE SATISFACTION OF BUILDING IT YOURSELF

More features and performance for your dollar and direct-to-you savings. No experience or special skills required.

SEND CARD FOR FREE HEATHKIT CATALOG

OVER 350 KITS TO CHOOSE FROM

• digital design color TV • digital clocks & thermometers • stereo & 4-channel hi-fi • fishing & marine • ham radio • home appliances • calculators • treasure finders • weather station • auto tuneup • radio control • test instruments • electronic organs • hundreds more

Heathkit SB-104

Unquestionably the most sophisticated SSB transceiver

A totally new and revolutionary transceiver. If you've been looking for a transceiver with "no compromise" features and performance, here it is.

Completely solid-state from the front-end to the RF output, it uses over 275 solid-state devices including 31 IC's, 75 transistors and 171 diodes. The four finals are totally protected from high SWR and thermal runaway properly used, they should never need replacement. The SB-104 output board and final transistors are warrented for one full year.

The 104 is totally broadbanded.

Switch from 3 to 30 MHz in seconds without preselector, load or tune controls.

True digital readout—six bright digits read out the frequency with resolution down to 100 Hz on all bands. The readout takes all three sources into account—VFO, HFO and BFO, so you get absolutely accurate display of operating frequency.

Unprecedented performance.

The transmitter delivers a solid 100-watt output and, for QRPers, a front-panel button instantly changes the output to one watt. Harmonic and spurious radiation are low, third-order distortion is down 30 dB or better at full power. Carrier and unwanted sideband suppression are down 55 dB. The receiver section is equally impressive. Cross-modulation and intermodulation have been minimized and there are very few active devices ahead of the highly selective crystal filter. Adjacent signal overload is non-existent, yet sensitivity is better than 1 μV.

And what features!

Front panel controls include a large VFO spinner with about 30 kHz per revolution, drive level, AGC (fast, slow, off), pushbuttons for USB/LSB/CW, a tune button for loading linear amps, power on/off, pushbutton metering of DC input voltage, ALC action and relative power. The built-in VOX is controlled by front-panel in/out, gain and delay controls. For instant time updates, there's a 15 MHz WWV receive position on the bandswitch. We've even left space on the readout panel to install your own call sign and included all the letters and numbers you need.

The SB-104 operates from 12-volt power, so it's ready to go mobile when you are. The optional HP-1144 power supply lets you use the SB-104 in a fixed station. Back panel inputs and outputs include: phone patch, separate Tx and Rcv antennas, IF out, driver out, VFO in and out.

An optional 400 Hz crystal filter plugs into one of the circuit boards to improve CW selectivity. An optional digital noise blanker can be installed in the SB-104 to reduce ignition noise. It is controlled by a front-panel in/out switch and provides up to 50 dB of effective blanking with a repetition rate of 10 to 2000 pulses per second and pulse widths of 1 to 250 microseconds.

Easy assembly and alignment.

Even though the SB-104 is a complex piece of equipment, we've kept construction simple by modularizing. All but a handful of the parts mount on 15 glass epoxy circuit boards, and two harnesses eliminate 95% of the wiring. Eleven of the boards plug in for easy assembly and servicing—seven can be extended from the chassis while the transceiver is operating. Because of the broadband design, alignment is fast and requires only a dummy load, mike and VTVM.

It's years ahead in design and features.

Just about the only thing that isn't new about the SB-104 is the quality that's made Heath one of the most respected names in the industry.

Kit SB-104, 31 lbs., mailable 669.95*

Kit SBA-104-3, 400 Hz CW crystal filter, 1 lb., mailable 34.95*

Kit SBA-104-1, noise blanker, 1 lb., mailable ...24.95*

Kit SBA-104-2, mobile mount, 6 lbs., mailable ..34.95*

Heathkit SB-230

The lowest cost conduction-cooled linear anywhere

The best linear value ever!

The super-performance silent partner of the SB-104, it puts out 1200 watts PEP and 1000 watts CW from less than 100 watts input. It's also rated at 400 watts input for slow-scan TV and RTTY. Third order distortion is low—30 dB down. The high-efficiency Eimac 8873 triode is completely enclosed in a double-shielded compartment to reduce stray RF. Super quiet, too, since the massive heat sink eliminates the need for noisy fans or blower.

Complete operating convenience.

All the controls are at your fingertips—single-knob bandswitch, load and tune controls, relative power sensitivity plus metering for relative power, plate current, grid current and plate high voltage.

A full complement of safety features.

The cabinet features microswitch interlocks to cut off the power whenever the top or bottom shells are removed. When thermal shutdown occurs, the Hi-temp light glows. The Exciter light signals that the linear is running straight through without amplification. The Delay light stays on until the output tube is warmed up. The on/off switch includes a circuit breaker for the primary side of the power transformer and the cathode of the tube is fused for additional protection.

Kit to transmit in 15 to 20 hours.

Most components are chassis-mounted and point to point wiring is held to a minimum. After a few preliminary checks with an ohmmeter, you're on the air—no alignment necessary.

The new SB-230 is styled to match the SB-104 transceiver. Check the performance and the price, we think you'll agree that, dollar for dollar, the SB-230 is a super value.

Kit SB-230, 40 lbs., mailable 319.95*

complete your SB-104 rig with Heathkit accessories

A) HP-1144 Fixed-Station AC Power Supply

This new 120 V/240 VAC supply provides the 13.8 VDC required by the SB-104. The full-wave bridge circuit has triple Darlington regulation with an integrated circuit which samples, compares, and automatically adjusts transistor bias to maintain a fixed output level. Output is remotely sampled at the load end of the power cable to compensate for voltage drop across fuse and cable. There's almost no change in voltage from no load to full load. A cable and socket provide output power and a series connection to the SB-104 on-off switch. The generous heat sink fits on the back of the supply and the entire unit may be mounted inside the SB-604 speaker cabinet.

Kit HP-1144, 28 lbs., mailable **89.95***

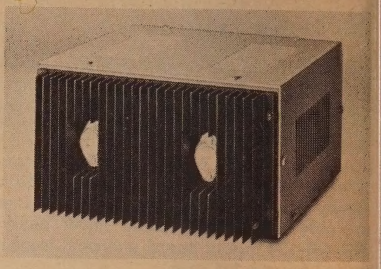

B) SB-604 Station Speaker

Designed and styled to match the new SB-104 Transceiver, the cabinet is large enough to house the HP-1144 AC Power Supply. The 5 x 7″, 3.2 ohm speaker is response-tailored for SSB. Connector cable and plug are included.

Kit SB-604, 8 lbs., mailable **29.95***

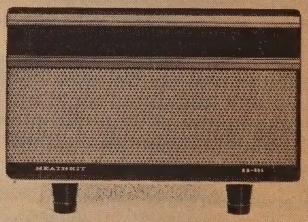

C) New SB-614 Station Monitor

How clean is your signal? With the SB-614, you'll know. It monitors transmitted SSB, CW, and AM signals up to 1 kW from 80—6 meters. The highly visible 1½ x 2″ CRT has push-pull drive for a keystone-free, sharp, clean trace. It reveals a wide variety of common operating problems: non-linearity, insufficient or excessive drive, poor carrier or sideband suppression, regeneration, parasitics and CW key clicks.

Complete controls—Vertical Gain & Position, Horizontal Gain & Position, Focus, Mode (SSB, Trapezoid & Cross for RRTY Mark/Space adjustments). The improved recurrent, automatic sync sweep generator has three ranges from 10 Hz to 10 kHz. Front panel control gives 11 steps of attenuation. The "614" can be used as a normal scope, within its 10 Hz to 50 kHz bandwidth. A rear panel 10:1 vertical attenuator provides extra convenience.

Additional features include all solid-state design; rear panel Astigmatism control; horizontal and vertical inputs for use as a scope; exciter and linear inputs/outputs.

Kit SB-614, 17 lbs., mailable **139.95***

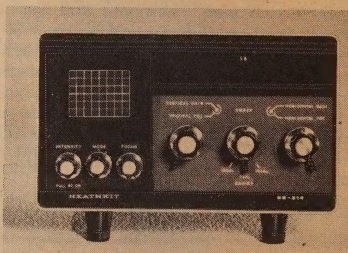

D) New SB-634 Station Console

Five station accessories in one! The new "634" provides five necessary functions that every amateur can use.

24-hour digital clock: six half-inch digits indicate hours, minutes and seconds. And the clock runs independently of all other functions.

Ten-minute ID timer: Three gas discharge digits indicate minutes and seconds up to 9:59. At ten minutes the timer recycles and provides either a visual alarm or both visual and audible alarms. Pushbutton zero reset.

RF wattmeter: The big meter has two ranges—200 watts or 2000 watts full scale ±10% accuracy from 160 through 10 meters.

SWR bridge: Push a button to measure SWR. Separate front panel SWR sensitivity control.

Phone patch: The hybrid patch can be used manually or with VOX control without switching connections. Push a button to select VU capability on the meter and use the separate front panel controls to adjust transmitter and receiver gain independently. Line isolation is at least 30 dB, and can be adjusted with a rear panel control.

Kit SB-634, 14 lbs., mailable **179.95***

E) New SB-644 Remote VFO

Designed exclusively for the new SB-104. Provides split transmit/receive without a separate transmitter and receiver. You aren't frequency limited in any way—the transceiver can be at one end of the band, the remote VFO at the other end.

Multi-mode capability. The "644" allows transceive operation on either itself or the "104"...transmit on the "104" and receive on the "644"...receive on the "104" and transmit on the "644". And you can use either of the two crystal positions in the "644" for fixed-frequency control.

Easy pushbutton operation. Front panel pushbuttons control all transceive, transmit and receive modes on both the "104" and the remote VFO. Status lamps behind the window indicate frequency-control mode.

Digital readout in the SB-104. Although the SB-644 includes a linear dial on its front panel, actual frequency readout takes place in the "104". The digital display automatically changes to the correct frequency as you go from transmit to receive.

Kit-built VFO. The "644" uses the same kit VFO as the new SB-104. The VFO goes together easily, quickly, and with a minimum of adjustments. And the "104" requires no modifications...just plug in the remote VFO and go. If you work serious DX with your new SB-104, you'll want the new "644" to make the job easier. Order it now.

Kit SB-644, 10 lbs., mailable **119.95***

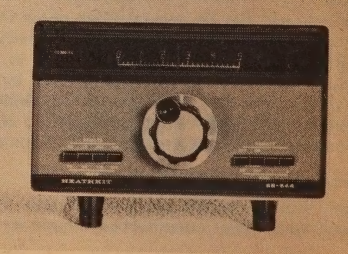

an important message from Heath amateur radio product line manager, Joe Shafer

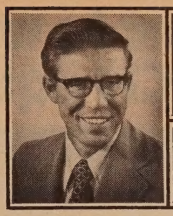

DESIGN NOTES

Joe Shafer K8DCE
Communications
Product Line Manager

Dear Fellow Radio Amateurs:

The development and introduction of the SB-104 SSB Transceiver has been a challenging and exciting experience for us at Heath.

Our engineers worked to a tough set of design goals and developed a truly remarkable SSB transceiver that features digital frequency readout, no receiver or final amplifier tuning, 100 watts output and superior receiver cross modulation performance—all on easy to build plug-in epoxy glass circuit boards.

Our advertising has done a reasonable job of explaining these features to you; however, I know that some of the circuits and components used in the SB-104 are probably new or unfamiliar to you. Therefore, I feel a deeper look into some of these new circuit techniques may be helpful.

To discuss these new techniques, I have asked our design engineers to prepare a series of brief technical papers on the more interesting areas of the circuitry used in the SB-104. These papers will appear in this column each month under the title "Design Notes".

Some of the topics to be covered in the initial issues of the series will be: "How receiver performance is improved without an RF stage", "Techniques and circuitry in broadband solid state amplifier design", "Circuitry and components in digital frequency readout".

Not only will future "Design Notes" be a source of technical information, but they will allow you to meet some of our Design Engineers who were directly involved with the design of the SB-104... a design, I believe, that presents the greatest step forward in amateur radio SSB equipment in over a decade.

I hope that our "Design Notes" column will receive high priority as you read your favorite publication each month.

73, Joe

Send for your **FREE** 1975 Heathkit Catalog

FREE 1975 HEATHKIT CATALOG

HEATH Schlumberger

Heath Company
Dept. 12-12
Benton Harbor, Michigan 49022

☐ Please send my free 1975 Heathkit Catalog.
☐ Enclosed is $_____, plus shipping.
Please send model(s)_____
Name_____
Address_____
City_____ State_____ Zip_____
Prices & specifications subject to change without notice. *Mail order prices; F.O.B. factory. AM-301

HEATHKIT ELECTRONIC CENTERS—
Units of Schlumberger Products Corporation
Retail prices slightly higher.

ARIZ.: Phoenix; CALIF.: Anaheim, El Cerrito, Los Angeles, Pomona, Redwood City, San Diego (La Mesa), Woodland Hills; COLO.: Denver; CONN.: Hartford (Avon); FLA.: Miami (Hialeah), Tampa; GA.: Atlanta; ILL.: Chicago, Downers Grove; IND.: Indianapolis; KANSAS: Kansas City (Mission); KY.: Louisville; LA.: New Orleans (Kenner); MD.: Baltimore, Rockville; MASS.: Boston (Wellesley); MICH.: Detroit; MINN.: Minneapolis (Hopkins); MO.: St. Louis (Bridgeton); NEB.: Omaha; N.J.: Fair Lawn; N.Y.: Buffalo (Amherst), New York City, Jericho (L.I.), Rochester, White Plains; OHIO: Cincinnati (Woodlawn), Cleveland, Columbus; PA.: Philadelphia, Pittsburgh; R.I.: Providence (Warwick); TEXAS: Dallas, Houston; WASH.: Seattle; WIS.: Milwaukee

How to win the fist fight... with CW equipment from HAL.

The economical HAL 1550 keyer.

The easy-to-use 1550 keyer is your answer if you're looking for an electronic keyer that lets you send accurate CW effortlessly. Send from 8 to 60 WPM with conventional, iambic, and dot memory operation. Operates with dual or single lever keys. The optional 1550/ID automatically sends "DE" followed by your station call. For fast, accurate CW, order the HAL 1550/ID or 1550 today.

Price: 1550/ID, $95; 1550, $75; ppd USA. Air shipment, add $3.

ID-1A repeater identifier. Commercial quality, low price.

The HAL ID-1A brings the radio amateur a commercial-quality repeater identifier that complies with FCC ID requirements. It has a unique read-only-memory that you can easily reprogram yourself. Capacity of the ROM is 39 dots, dashes and spaces. TTL IC's assure immunity from noise and temperature. ID intervals available: 3, 6, 12 or 24 min. Specify call.

Price: $115, ppd USA. Air shipment, $3.

Send perfect CW every time with the MKB-1.

A complete Morse keyboard. Code speed variable from 10-60 WPM with variable dot-to-space ratio (weight). All solid-state, featuring computer-grade components. Complete alphanumeric and punctuation keys, plus an optional "DE-call sign" key factory programmed for you. Includes built-in speaker/oscillator monitor.

Price: $290 Assembled, $199 Kit, ppd USA. Without ID, $250 Assembled, $170 Kit. Air shipment, $5.

CW—and RTTY on one keyboard! The HAL DKB-2010.

All solid-state. Type out CW at 8-60 WPM. Adjustable dot-to-space ratio (weight). Complete alphanumeric keys, plus 11 punctuation marks. Five standard two-character keys, 2 shift keys, break-for-tuning key, 2 three-character function keys, and a "DE-call sign" key. We'll program your call right into the DKB-2010. Plus complete RTTY capabilities. Built-in three-character buffer. Optional 64 or 128 key buffer also available.

Price: $425 Assembled, $325 Kit, ppd USA. 64 key buffer $100, 128 key buffer $150. Air shipment, $10.

HAL Communications Corp.
Box 365, Urbana, Illinois 61801
Telephone: (217) 359-7373

Enclosed is $_____ for: ☐ DKB-2010 ☐ MKB-1 ☐ 1550 ☐ ID-1A
Please specify ☐ Assembled ☐ Kit ☐ Options _____
Please send me more information on the following HAL products . . .
☐ DKB-2010 ☐ MKB-1 ☐ 1550/1550 ID ☐ ID-1A
☐ Complete HAL catalog

Name _____ Address _____ Call Sign _____

City/State/Zip _____

Illinois residents add 5% sales tax.

C

DECEMBER, 1974 VOL. 30, NO. 12

CQ The Radio Amateur's Journal

STAFF

EDITORIAL

RICHARD A. ROSS, K2MGA
Editor

ALAN M. DORHOFFER, K2EEK
Managing Editor

WILFRED M. SCHERER, W2AEF
Technical Consultant

MARGUERITE J. FAGELLA
Editorial Assistant

CONTRIBUTORS

FRANK ANZALONE, W1WY
Contest Chairman

FRED CAPOSSELA, W2IWC
Contest Consultant

GEORGE JACOBS, W3ASK
Propagation Editor

A. EDWARD HOPPER, W2GT
USA-CA Director

JERRY HAGEN, WA6GLD
DX Editor

JOHN A. ATTAWAY, K4IIF
Assistant DX Editor

GORDON ELIOT WHITE
Surplus Sidelights

IRWIN MATH, WA2NDM
Math's Notes

COPTHORNE MACDONALD, WØORX
SSTV Editor

BUSINESS

SANFORD R. COWAN
President

RICHARD A. COWAN, WA2LRO
Publisher & Advertising Director

GLORIA FORSYTH
Circulation Manager

PRODUCTION

ALAN M. DORHOFFER, K2EEK
Production Manager

WILLIAM H. TRAVIS
Art Director

MARY ELLEN TAYLOR
Art Assistant

K & S GRAPHICS
Illustrations

FEATURES

DIGITAL SPEED READOUT IN AN ELECTRONIC KEYER
Don C. Gilbert, WA2SKL/WA4SPD 26

RESULTS OF THE 1974 CQ WORLD WIDE WPX SSB CONTEST
Bernie Welch, W8IMZ 33

ANNOUNCING THE QRPp TRANSMITTER DESIGN CONTEST
Adrian Weiss, K8EEG 38

COP'S COLUMN: RFI PROBLEMS AND SOLUTIONS
Copthorne MacDonald, WØORX 40

NOVICE: ELECTRONIC KEYERS
Herbert S. Brier, W9EGQ 43

MATH'S NOTES: LIGHT EMITTING DIODES (LED)
Irwin Math, WA2NDM 45

QRP: ANTENNA SYSTEM EFFICIENCY
Adrian Weiss, K8EEG 46

LOSS IN TRANSMISSION LINE SYSTEMS
William LaHiff, W2IVT 49

ANTENNAS: INVISIBLE ANTENNAS AND ALL BAND DIPOLE
William I. Orr, W6SAI 53

INDEX TO CQ VOLUME 30—1972 90

DEPARTMENTS

DX: USA BICENTENARY SPECIAL CALLS
Jerry Hagen, WA6GLD 57

PROPAGATION: DX CHARTS FOR DEC. 15, THROUGH FEB. 15
George Jacobs, W3ASK 61

CONTEST CALENDAR: CONTESTS FOR DECEMBER
Frank Anzalone, W1WY 64

AWARDS: STORY OF THE MONTH— JAMES K. RAMSEY, WA4ULL
A. Edward Hopper, W2GT 67

SURPLUS SIDELIGHTS: THE AN/ARN-14 NAVIGATION RECEIVER
Gordon Eliot White 68

ANNOUNCEMENTS ..... 10 OUR READERS SAY 9

HAM SHOP ..... 76 ZERO BIAS 7

Offices: 14 Vanderventer Avenue, Port Washington, L.I., N.Y. 11050. Telephone: 516-883-6200.

CQ (Title registered U.S. Post Office) is published monthly by Cowan Publishing Corp. Second Class postage paid at Port Washington, N.Y. and Miami Florida. Subscription Prices one year, $6.00; two years, $11.00; three years, $15.00. Entire contents copyrighted 1974 by Cowan Publishing Corp. CQ does not assume responsibility for unsolicited manuscripts. Allow six weeks for change of address. Printed in the United States of America.

Postmaster: Please send form 3579 to CQ Magazine, 14 Vanderventer Ave., Port Washington, L.I., N.Y. 11050

hy-gain 18AVT/WB vertical antenna!

80 through 10 meters

For true wide-band performance!

The 18AVT/WB gives you unrivaled omnidirectional performance *with 80 meter capability.* Don't settle for second best when you can get true wide-band coverage, superior construction and brilliant performance in one reasonably priced package.

- Automatic switching on all 5 bands using 3 high strength Hy-Q traps with extra large diameter coils for exceptional L/C ratio and high Q.
- All extra heavy duty taper swaged seamless aircraft aluminum with full circumference compression clamps at all joints. So strong, its full 25′ height can be mounted using only a 12″ double grip bracket on 1-5/8″ mast.
- Recessed coax connector in base.
- Hy-Q traps isolate antenna sections for true 1/4 wave resonance on all bands.
- Top loading coil for 80 meters.
- 1 KW CW, 2 KW PEP (maximum power on 80—1 KW PEP), 52 ohms impedance.
- Total performance all the way across the band with just one setting (10-40).
- No dissimilar metals to corrode and cause noise.
- SWR 2:1 or less at band edges (10-40).
- Maximum legal power 10-40 meters, low frequency drift.
- Extremely low radiation angle for easy long haul and DX contacts, roof mounted with radials or ground mounted without radials.
- For roof mounting, use 14RMQ Roof Mount/ Radial Kit.
- Wind survival—80 mph.

Order No. 386

For prices and information, contact your local Hy-Gain distributor or write Hy-Gain.

hy-gain

Hy-Gain Electronics Corporation; 8601 Northeast Highway Six; Lincoln, NE 68507; 402/464-9151; Telex 48-6424.
Branch Office and Warehouse; 6100 Sepulveda Blvd., #322; Van Nuys, CA 91401; 213/785-4532; Telex 65-1359.
Distributed in Canada by Lectron Radio Sales, Ltd.; 211 Hunter Street West; Peterborough, Ontario.

ZERO BIAS

OSCAR 7 Launched Successfully and Working A-OK!

Mark November 15 as another landmark in the history of amateur radio! At exactly 1711 GMT a two stage Delta vehicle lifted slowly off its pad at NASA's western test range near Lompoc, California. Shrouded in a wall of orange-yellow flame and with a tremendous roar, it streaked southward into a cloudless, deep blue sky.

The prime mission of the spacecraft was to launch the fourth operational NOAA weather satellite and INTASAT, a scientific satellite built by Spain. But of greater importance to radio amateurs was the third passenger aboard the giant Delta - AMSAT OSCAR 7, with its two radio amateur repeaters, three telemetry beacons and other communication innovations. It was a textbook launch and all went according to the preflight scenario.

OSCAR-7 was ejected from the parent vehicle at 1828:33 GMT high above Greece, and within seconds its 435.100 MHz telemetry beacon was operating and being received by radio amateurs throughout Europe.

DK2ZF near Hamburg acquired the beacon at 1828:46 GMT and reported the first complete frame of telemetry data. G3IOR, PAØAA, GB2SM, G2BVN, DL3SX, DL9GU and DJ8IM, among others, also reported hearing the satellite from its first beep.

Credit for the first US station to copy the beacon appears to go to K7BBO who acquired it at 1846:37 GMT followed 13 seconds later by K1HCV and just after that by WØPHD.

As planned, the 2-to-10 meter repeater was sucessfully placed into operation along with the 29.50 MHz telemetry beacon an hour after midnight GMT on Nov. 17. The 432 MHz-to-2-meter repeater went into operation as planned on Nov. 18 along with the 145.980 MHz telemetry beacon.

At press time, telemetry readings and the operation of both repeaters indicate that the newest radio amateur satellite is working according to plan. Hundreds of QSO's have been made through both repeaters during the first few days of operation including many trans-Atlantic contacts. The signals relayed through the 432 MHz-to-2-meter repeater have been much stronger than expected and no more than 80 watts ERP should be necessary rather than the 400 watts originally estimated.

OSCAR 7's initial orbit parameters are: Period - 114.99 min.; Longitude Increment-28.748 ; Inclination to Equator - 101.73 . Its orbit is almost exactly circular at 1445 km above the earth's surface. These are very similar to OSCAR 6's orbital parameters, but a half period or 57.5 minutes out of phase.

The 2-to-10 meter repeater will be available for world-wide communication on Sunday, Tuesday and Friday GMT days, and the 432 MHz-to-2-meter repeater on Monday, Thursday and Saturday GMT days. The repeaters are not available for communication on Wednesdays.

Complete details on the OSCAR 6 and OSCAR 7 satellites appeared in the October issue of *CQ* and there will be a more complete report and updated orbital data in next

If You Haven't Used An
ALPHA 374

Then You Don't Know How Easy It Is To Use A
REALLY MODERN COOL KILOWATT!

ALPHA 374 doesn't take up a lot of space — won't break your back *or* your bankbook — eliminates the usual chore of tune-up when changing bands under normal conditions. And **ALPHA 374** is ruggedly built to do the job right . . . in the **ALPHA** tradition!

- A COOL, CONSERVATIVE FULL GALLON — all modes — self-contained in one beautiful cubic foot!
- NO-TUNE-UP INSTANT BANDCHANGE — pretuned bandpass filters do the job for you.
- ADVANCED CONTROL, MONITORING, AND ALC make operation simple.
- PREMIUM COMPONENTS — superb **ALPHA** engineering and craftsmanship.

Every **ALPHA 374** is backed by ETO's full year warranty and traditional service. Contact your dealer today — or if more convenient call ETO direct — for full details and prompt delivery of *your* new **ALPHA 374**.

U.S. Amateur Net Price $1195.

ETO EHRHORN TECHNOLOGICAL OPERATIONS, INC.
BROOKSVILLE, FLORIDA 33512
(904) 596-3711

month's issue. Remember that OSCAR 7's 2m. uplink is between 145.85 and 145.95-MHz, and the 10 m. downlink is between 29.40 and 29.50 MHz with telemetry beacon at 29.50 MHz. The 432 MHz uplink is between 432.125 and432.175 and the downlink is inverted between 145.975 and 145. 925 MHz with beacons at 145.980 and 435. 100 MHz.

In the US the new satellite should be in view for communications up to 4000 miles for at least three successive orbits during the morning hours and three during the evening. It should remain in range for up to 20 minutes on nearly overhead passes.

All of amateur radio can bask in the glory of the OSCAR 7 success. It's another tangible contribution that amateurs have made in advancing the state of the communications art. It should weigh heavy in our defense of our bands when the h.f. spectrum is carved up again at the international frequency conference planned for 1979. For example, the 10 meter band, once almost barren above 29 MHz and looked upon greedily by other services, is now almost solid with amateur signals relayed by OSCAR 6 and OSCAR 7 between 29.40 and 29.55 MHz.

Special credit must go to the talent, sincerity and devotion of the many radio amateurs in the US, Canada, Germany and Australia who participated in the actual design, construction and testing of the satellite, to members of AMSAT, to the ARRL, and to the European members of IARU, all of whose funding and support made OSCAR 7 a reality.

To Jan King, W3GEY, Project Manager of AMSAT-OSCAR 7, our special congratulations and ourapology for not identifying him as the handsome gentleman on the October *CQ* cover.

We here at *CQ* take quiet pride in the seven OSCARs launched to date. It all started in our magazine with an idea put forth by Don Stoner, W6TNS, in 1959 and was followed up partly on the initiative of our Space Communications Editor, George Jacobs, W3ASK, with the formation of the Project OSCAR Association and the sucessful launching of OSCARs 1,2,3, and 4. George also sparked the interest through these pages that led to the establishment of AMSAT and the development of OSCARs 5,6, and 7.

We at *CQ* are eagerly looking forward to a bigger and better OSCAR 8 and you'll be reading about it here in *CQ* in the near future.

Message from the Publisher

Our message from the publisher that appeared on page 5 of the October *CQ* has prompted, as we anticipated, considerable reaction from subscribers. Most reaction was, as we had hoped it would be, comment that *CQ* was well respected, and that even an economized version of *CQ* is still a valuable asset to the operating amateur. We did receive a total of sixteen subscription cancellations (almost all of these indicated that the free classified ad withdrawal was the influencing factor. There will be a replacement program for that announced elsewhere in this issue) and a few phone calls from concientious advertisers offering additional ad support to get *CQ* rolling on a profitable basis.

It also prompted, as expected, an editorial comment in *73* from W2NSD in his inimitable fashion, stating that should *CQ* cease publication he'd be happy to take over our subscriber list, contests, etc. Over the years Mr. Green has hinted many times that *CQ* might disappear from the scene. He never misses an opportunity to get in a dig that might prove embarrassing to a competitor. Bravo, Wayne! You never fail to show your true colors when the chips are down. And as we've said before, the name may be Green but the journalism is inevitably quite yellow.

At any rate, we wish to assure our readers that our retrenchment measures have proven most successful; *CQ* will show a modest profit for the first time in many months with the October issue, and projected business is definitely on the upswing. You need not fear that *CQ* will cease publication. That is not and has never been our intent. We're grateful for the many kind comments from readers and advertisers alike, and we expect that *CQ* columns and contests will be an integral part of amateur radio for many years to come.

Richard A. Cowan, WA2LRO
Publisher, *CQ*

SMALL SIZE

COUNTER DIAL

The No. 10031 Dial is a rugged turns counter dial designed for direct crank-handle drive of multi-turn devices such as vacuum variable capacitors, rotary inductors, multi-turn potentiometers, permeability tuned inductors, etc. It has a 0-99 turn digital readout plus a 0-100 vernier scale. The output coupling is a hub for 1/4" diameter shafts. The design includes a built-in dial lock.

JAMES MILLEN
MANUFACTURING COMPANY, INC.
150 Exchange St., Malden, Mass. 02148 • (617) 324-4108

Announcements

Sandusky, Ohio

The Erie Amateur Radio Society will hold its' Semi-Annual Swap and Auction on Sunday, December 1rst, 1974. Cash Grand Prizes; admission: $1.00. For more information call: Earl L. Carrier K8WLP. Call in on 52/52.

Passaic, New Jersey

The Knight Raiders VHF Club, K2DEL, will sponsor a VHF Activity Week to be held December 23, 1974 thru January 1, 1975. Contact may be made on any band above 50 Mhz. Participants who work the club station and 5 club members will receive a Knight Raiders Award certificate. Those who work at least 10 of the 16 municipalities in Passaic County will receive a Passaic County Award certificate. Stations within Passaic County are eligible for both awards. A one dollar fee must be sent for each certificate for the cost of handling and postage. Send fee and logs to: Knight Raiders VHF Club, P.O. Box 1054, Passaic, New Jersey 07055.

Fort Wayne Indiana

On January 19th 1975, The Allen County Amateur Radio Technical Society will sponsor The Fort Wayne Hamfest. It will take place at Shiloh Hall, ½ mile West of Ind. 3 on Carroll Rd. Tickets are $1.50 and children under 12 years of age are admitted free. For more information write: P.O. Box 342 Fort Wayne, Indiana 46801.

Wheaton, Illinois

The Wheaton Community Radio Amateurs will have their annual mid-winter hamfest on Sunday, February 9th at the DuPage County Fairgrounds in Wheaton, Illinois. For information and advance tickets send a SASE to L.O. Shaw, W9OKI, 433 S. Villa Ave., Villa Park, IL 60181.

Flushing, New York

The following Amateur Radio equipment was stolen from the Hall of Science Radio Club earlier this year: Eico no. 720 CW Transmitter, Eico no. 722 V.F.O., Heathkit HR-20 Receiver, Globe Scout CW Transmitter, Hallicrafters SX99 Receiver, MC-4 Mobile Console Wattmeter, Homebrew Transmatch and CD Ham M Station Console. Anyone who might aid in the recovery of this equipment, please write to: Hall of Science Radio Club, Flushing Meadows - Corona Park, P.O. Box 1032, Flushing New York, 11352.

CQ'S DIAL-A-PROP

For the latest up to the minute propagation forecasts and special contest predictions call 516-883-6223 any time day or night for a recorded message on conditions.

HUSTLER®

4-BTV THRIVES ON COMPARISON!

FOUR BAND—40 THRU 10 METERS FIXED STATION TRAP VERTICAL

Whether you want—

- one setting for total band coverage
- extra weight and high mechanical strength
- easy assembly and installation

—or just plain performance and reliability—

Hustler is the verified choice!

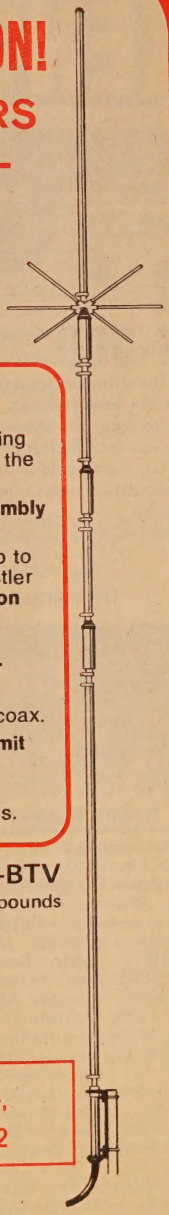

PERFORMANCE AND MECHANICAL SPECIFICATIONS

- **Lowest SWR**—PLUS!
- Bandwidth at its **broadest!** SWR 1.6 to 1 or better at band edges.
- Hustler exclusive trap covers **"Spritz" extruded** to otherwise unattainable close tolerances assuring accurate and permanent trap resonance.
- Solid one inch **fiberglass trap forms** for optimum electrical and mechanical stability.
- Extra heavy duty aluminum mounting bracket with **low loss—high strength** insulators.
- All sections **1¼" heavy wall,** high strength aluminum. Length 21'5".
- **Stainless steel clamps** permitting adjustment without damage to the aluminum tubing.
- Guaranteed to be **easiest assembly** of any multi-band vertical.
- Antenna has ⅜"-24 stud at top to accept RM-75 or RM-75-S Hustler resonator for **75 meter operation** when desired.
- Top loading on 75 meters for broader bandwidth and **higher radiation efficiency!**
- Feed with **any length** 50 ohm coax.
- Power capability—**full legal limit** on SSB and CW.
- Ground mount with or without radials; roof mount with radials.

MODEL 4-BTV
WGT. 15 pounds

Buy Hustler . . . buy the verified choice of thousands!

Available from all distributors who recognize the best!

new-tronics corporation
15800 commerce park drive,
brook park, ohio 44142

Exporter: Roburn Agencies, Inc., New York, N.Y.

Suddenly...the answer is KENWOOD

Today when you ask "How can I modernize my SSB operation?", the answer certainly is KENWOOD. The deluxe TS-900 transceiver, the superb, go-anyplace TS-520 transceiver and the versatile R-599A receiver and T-599A transmitter offer today's amateur advanced design, reliable solid-state performance, contemporary styling. . . and the cost is modest. Now more than ever the answer is KENWOOD.

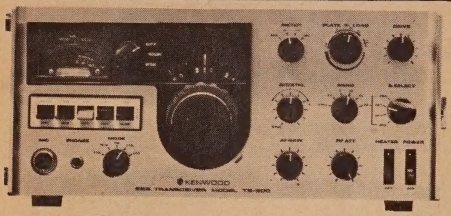

TS-900 Kenwood's superb state-of-the-art SSB transceiver

. . . the ultimate transceiver. The promise of the transistor has been fulfilled. Here is the transceiver you will want to own . . . whatever you have now, get ready to trade up. Its important features are far too numerous to list. Its specifications are superb. The TS-900 is unquestionably the best transceiver of its kind ever offered.
The price $795.00
PS-900 (AC Supply) $120.00, the DS-900 $140.00

TS-520 Kenwood's go every place . . . do everything transceiver

The new TS-520 is the transceiver you have wanted, but could not buy until now. It is a non-compromise, do everything, go everywhere 5 band transceiver for SSB or CW that performs equally well at home, in an automobile, airplane, boat or trailer. The TS-520 features built-in AC power supply, built-in 12 volt DC power supply, built-in VOX with adjustable gain delay and anti-VOX. The price $629.00

The "Twins" by Kenwood

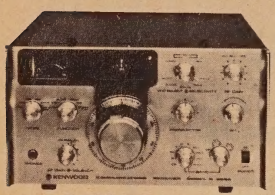

R-599A Receiver

The R-599A is the most complete receiver ever offered. It is solid state, superbly reliable, small and lightweight, covers the full amateur band . . . 10 thru 160 meters, CW, LSB, USB, AM, AM.N and FM.
The price $459.00

The T-599A is mostly solid state . . . only 3 tubes, has built-in power supply, full metering (ALC, Ip. RF output & high voltage), CW-LSB-USB-AM operation.
The price $479.00

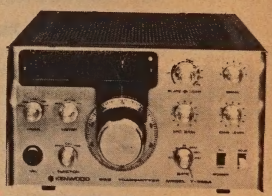

T-599A Transmitter

See the Kenwood line at the following dealers: • **ALABAMA** / L & T Electronic Specialties, Birmingham • **ALASKA** / Service Electric Co., Inc., Ketchikan • **ARIZONA** / Ham Shack, Mesa • Orbit Electronics, Tucson • **CALIFORNIA** / Communications Headquarters, San Diego • Gary Radio, Inc., San Diego • Ham Radio Outlet, Burlingame • Henry Radio, Anaheim • Henry Radio, Los Angeles • Webster Radio, Fresno • **COLORADO** / Radio Communication Company, Arvada • **FLORIDA** / Amateur Electronic Supply, Orlando • Amateur Radio Center Inc., Miami • Amateur Wholesale Electronics, Miami • Grice Electronics Inc., Pensacola • Hollister Electronic Supply, Jacksonville • **GEORGIA** / Clayton Communications, College Park • **IDAHO** / United Electronics Wholesale, Twin Falls • **ILLINOIS** / Klaus Radio, Inc., Peoria • **INDIANA** / Graham Electronics, Indianapolis • Hoosier Electronics, Terre Haute • Radio Distributing Company, South Bend • **IOWA** / Hobby Industry, Council Bluffs • **KANSAS** / Associated Radio Communications, Overland Park • **MAINE** / Down East Ham Shack • **MARYLAND** / Electronic International Service Corp., Wheaton • Professional Electronics, Baltimore • **MICHIGAN** / Electronic Distributors, Muskegon • Radio supply & Engineering Company, Detroit • **MINNESOTA** / Electronic Center, Minneapolis • **MISSOURI** / Ham Radio Center, St. Louis • Henry Radio, Butler • **MONTANA** / Conley Radio Supply, Billings • **NEW MEXICO** / Gene Hansen Company, Corrales • **NEW YORK** / Adirondack Radio, Amsterdam • Harrison Radio Corp., Farmingdale, New York City, Spring Valley • Tom's Radio, Johnson City • **NORTH CAROLINA** / Freck Radio, Asheville • Vickers Electronics, Durham • **OHIO** / Amateur Electronic Supply, Cleveland • Communications World, Cleveland • Queen City Electronics, Cincinnati • Srepco Electronics, Dayton • **OKLAHOMA** / Derrick Electronics, Broken Arrow • Radio, Inc., Tulsa • **OREGON** / Portland Radio Supply, Portland • **PENNSYLVANIA** / Electronic Exchange, North Wales • JRS Distributors, York • Kass Electronics, Drexel Hill • **SOUTH CAROLINA** / Accutek, Inc., Greenville • **SOUTH DAKOTA** / Burghardt Amateur Center, Watertown • **TEXAS** / Douglas Electronics, Corpus Christi • Electronics Center, Inc., Dallas • Ed Juge Electronics, Inc., Fort Worth • Madison Electronics, Houston • **UTAH** / Manwill Supply Company, Salt Lake City • **WASHINGTON** / Amateur Radio Supply Company, Seattle • **WISCONSIN** / Amateur Electronic Supply, Milwaukee •

Prices subject to change without notice.

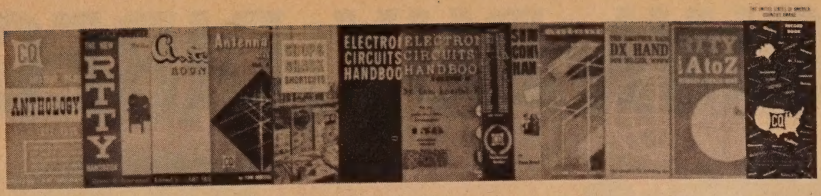

CQ BOOK SHOP

CQ Binders

Convenient and economical are the words for CQ's beautiful maroon and gold binders. Individual issues can be removed quickly and easily without damage to the magazine. Save precious time as reference copies are within immediate reach in this handy binder. $5.00

The New RTTY Handbook

A treasury of vital and "hard-to-get" information, this book is loaded with valuable equipment schematics, adjustment procedures, etc. A boon to beginner and pro. A special section on getting started, written by Byron Kretzman, W2JTP, a well-known authority in the field. $3.95

Antenna Roundup I

Edited by Art Seidman, a 160 page mass of antenna information directed at answering a multitude of questions surrounding the mysterious antenna. $3.00

Antenna Roundup II

Ten big theory articles backed up by 82 detailed and illustrated construction projects from VLF to microwave, long wires to 17 element beams and Sterba Curtain arrays. $4.00

Shop & Shack Shortcuts

A volume packed with hundreds of hints & shortcuts collected by Don Stoner, this will help anyone to dress up his shack, improve shop techniques and increase efficiency and equipment. $3.95

Antenna Handbook I

All new information on transmission line theory, Attenuation, Impedance, Standing waves, Resonant and nonresonant lines, current distribution, free space 3 dimensional patterns of long wires of all practical length and much, much more by Ken Glanzer. $4.00

The New DX Handbook

Don Miller's 200 pages of valuable technical information and operating aids, most of which has never been published before and can be found in no other volume contains Great Circle Bearing Charts. $5.00

CQ Anthology II

1952-1959 250 pages of more recent but still hard-to-get important articles from glorious yestervear. $3.00

Surplus Conversion Handbook

Compiled by Tom Kneitel, WB2AAI, this contains 192 pages of conversion articles, covering almost every piece of surplus gear worth the effort to convert to ham use. $4.50

Electronic Circuit Handbook I

Written by Tom Kneitel, WB2AAI, this details 150 of the most often needed circuits in 11 great chapters. Invaluable for beginners and old-timers alike. $3.00

Electronic Circuit Handbook II

Tom Kneitel's own sequel to Vol 1, this volume delivers 159 additional circuits that will appeal to all amateurs. Each circuit is fully described in text with complete schematics. $3.00

RTTY From A To Z

This new RTTY Classic has been produced to fill the gaps in RTTY knowledge among amateurs and professionals alike. 16 chapters and 224 pages. This book is a must in your technical library. $5.00

USA-CA Record Book

The official application and Record book for the coveted United States of America Counties Award issued by CQ. Contains room for simple entry of all data required to apply, plus rules and endorsement application. Two copies recommended: one for application, one for your records.Per copy price: $1.00.

DX Country Chart

Handsome wall-size chart (25" x 31") listing every amateur radio country in the world alphabetically by prefix, and giving continent, form of government, area, population, zone and class of country. A must for every active amateur and a bargain at $1.25.

- ☐ CQ Anthology II $3.00
- ☐ CQ Binders $5.00
- ☐ New RTTY Handbook $3.95
- ☐ Antenna Roundup I $3.00
- ☐ Antenna Roundup II $4.00
- ☐ USA-CA Record Book $1.00
- ☐ DX Country Chart $1.25
- ☐ Shop & Shack Shortcuts $3.95
- ☐ Electronic Circuits Handbook I $3.00
- ☐ Electronic Circuits Handbook II $3.00
- ☐ Surplus Conversion Handbook $4.50
- ☐ Antenna Handbook I $4.00
- ☐ New DX Handbook $5.00
- ☐ RTTY From A To Z $5.00

NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____

New York City and State residents must add sales tax applicable to your area.

COWAN PUBLISHING CORP. Book Div.
14 Vanderventer Avenue • Port Washington, L.I., N.Y: 11050

NOW! BUY DIRECT

WHAT DOES THIS MEAN?

It means that GENAVE'S outstanding line of Amateur radios is now available to you at new, inflation-beating prices. A glance at the new prices confirms that the dealer's discount has been entirely eliminated, to your benefit. The same fine radios that you've seen in his shop may now be ordered on a Factory-Direct basis. **You** pocket the savings. Warranty policies remain the same: if your new GTX fails within three months of purchase, send it back. We'll fix it or replace it, **fast.**

Order TODAY—Orders will be processed as they are received!

Standard crystal frequencies in stock @ $3.75 each:

1¼ Meter		2 Meter		6 Meter	
TX	RX	TX	RX	TX	RX
222.30	223.50	146.01	146.34	52.25	52.38
222.34	223.90	146.10	146.52	52.525	52.525
222.38	223.94	146.12	146.61	52.70	52.60
223.14	223.98	146.16	146.70	52.76	52.64
223.26	224.74	146.19	146.72	52.82	52.68
223.30	224.86	146.22	146.76	52.88	52.72
223.34	224.90	146.25	146.79	52.92	52.79
223.50	224.94	146.28	146.82	52.96	52.80
		146.34	146.85	53.15	53.05
		146.52	146.88	53.25	53.08
		146.94	146.94	53.68	53.16

Contact factory for prices on other crystal frequencies.

Made In U.S.A.

Genave®

USE THIS HANDY ORDER FORM TO HELP YOURSELF TO GIANT SAVINGS!

General Aviation Electronics, Inc., 4141 Kingman Drive, Indianapolis, Indiana 46226—Area 317-546-1111

for GIANT SAVINGS!

Look at These UNBEATABLE PRICES!

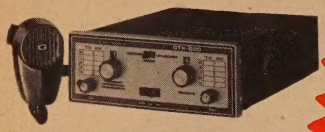

GTX-600 6-Meter FM
100 channels, 35 watts
WAS $309.95
NOW
$219.95
(Incl. 52.525 MHz)

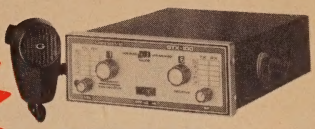

GTX-100 1¼-Meter FM
100 channels, 12 watts
WAS $309.95
NOW
$219.95
(Incl. 223.5 MHz)

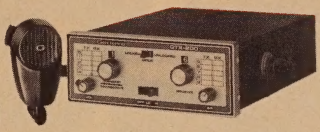

GTX-200 2-Meter FM
100 channels, 30 watts
WAS $299.95
NOW
$199.95
(Incl. 146.94 MHz)

GTX-2 2-Meter FM
10 channels, 30 watts
WAS $299.95
NOW
$189.95
(Incl. 146.94 MHz)

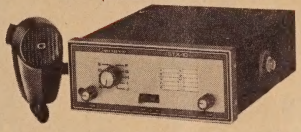

GTX-10 2-Meter FM
10 channels, 10 watts
WAS $239.95
NOW
$169.95
(Incl. 146.94 MHz)

CLIP OUT AND ORDER NOW!

CQ

GENAVE, 4141 Kingman Dr., Indianapolis, IN 46226
HEY, GENAVE! Thanks for the nice prices! Please send me:

☐ **GTX-600** @ $219.95 $_____
☐ **GTX-200** @ $199.95 $_____
☐ **GTX-100** @ $219.95 $_____
☐ **GTX-2** @ $189.95 $_____
☐ **GTX-10** @ $169.95 $_____

☐ **Lambda/30 2-M Base Antenna** @ $59.95 $_____
☐ **Lambda/6 2-M Trunk Antenna** @ $29.95 $_____
☐ **TE-1 Tone Encoder Pad** @ $59.95 $_____
☐ **PSI-9 Port. Power Package** (less batteries) @ $29.95 $_____
☐ **PS-1 AC Power Supply** @ $49.95 $_____

and the following **standard** crystals @ $3.75 each:_____
_____. $_____

Sub-Total $_____ Ind. residents add 4% sales tax:
Cal. residents add 6% sales tax:_____ **TOTAL:** $_____

All orders shipped post-paid within continental U.S. For C.O.D., Include 20% Down.

NAME _____ AMATEUR CALL _____

ADDRESS _____ CITY _____ STATE & ZIP _____

Payment by: ☐ Certified Check/Money Order ☐ Personal Check ☐ C.O.D.
Note: Orders accompanied by personal checks will require about two weeks to process.

☐ 20% Down Payment Enclosed. Charge Balance To:

☐ BankAmericard #_____ Expires _____

☐ Master Charge #_____ Expires _____ Interbank #_____

Prices and specifications subject to change without notice.

The Eitels comment on our *Triton*

William Eitel—WA7LRU/W6UF/W6AY
Laneil Eitel—WA7LUN/WB6MRW

Whatever your Amateur interests are on the HF bands, the TRITON will give you new operating convenience and pleasure. Fully solid state with the latest semi-conductor technology. Instant band change, high articulation SSB and a host of new and exciting features. Write for details.

William Eitel
Laneil Eitel

Sutro Ranch and Laboratory
DAYTON, NEVADA 89403
(702) 882-4187

August 24, 1974

Mr. Al Ka.
Ten Tec, Inc.
Sevierville, Tenn 37862

Dear Al:

I have been using a Triton II for about four months and I would like to comment on some of its features. As you know, my major interest on the HF bands is in high speed CW. After studying the features of the equipment available to serious CW operators, I decided the Triton II might meet my requirements. I had the opportunity to try a Triton II at the SAROC Convention in Las Vegas last January and I was indeed amazed at its performance on both SSB and CW. The Triton has better break-in performance than any separate receiver transmitter combination I have used and seems better than most of the stations I work. In a high speed roundtable, the first dot from the station wishing to break will usually break me. The CW filters are excellent and provide the selectivity necessary for practical CW operation. The offset tuning allows accurate zero beat with the station I wish to work. Yes, I am talking about a transceiver and not a receiver transmitter combination.

The XYL WA7LUN-WB6MRW is also a CW operator and she uses the Triton II at our summer location. She has decided to trade her present popular equipment for a Triton II. I am also considering replacing my home station exciter with a Triton. This will free my receiver for use for other purposes. I have used my receiver with the Triton II and the receiving antenna provision in the Triton is excellent and provides a very practical method of using a separate receiver to monitor other frequencies.

I would recommend the Triton to anyone interested in MODERN CW operation.

73,
Bill
Bill
WA7LRU/W6UF

WWE/eh

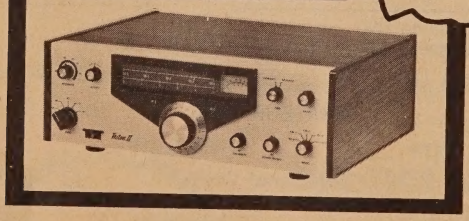

TRITON I 100 watts input $579.00
TRITON II 200 watts input 669.00

TEN-TEC, INC.
SEVIERVILLE, TENNESSEE 37862

PHOTO ETCH™ PRINTED CIRCUIT KIT

MAKES PRINTED CIRCUITS THREE WAYS!

1 FULL SCALE ARTWORK MASTER

2 MAGAZINE ART ILLUSTRATION → FILM POSITIVE → NEGATIVE → DEVELOPED PHOTO RESIST IMAGE ON COPPER CLAD CIRCUIT BOARD → ETCHED CIRCUIT BOARD

3 DIRECT ETCH DRY TRANSFERS APPLIED TO COPPER CLAD BOARD

NO CAMERA
DARKROOM
FILM CUTTING
TRACING

USES DATAK'S POS-NEG PROCESS
The revolutionary photographic way that makes PERFECT printed circuits from original art or a printed page.

KIT CONTAINS: 5" x 6" steel printing frame, 4 sheets 5" x 6" photocopy film, yellow filter, chemicals for 1 pint film developer and 1 pint film fixer, 5" x 6" copper clad board, 3" x 4½" copper clad board, spray can of photo etch resist, 1 pint resist developer, 2 sheets 8½" x 11" layout film, 1 roll 1/16" printed circuit tape, 1 roll 1/32" printed circuit tape, 8 sheets dry transfer direct etch PC patterns including pads, transistors, round can and flat pack ICs, DIP ICs, edge card connectors, lines, circles, jogs, etc., ¼ lb anhydrous ferric chloride to make 1 pint etchant, instructions.

ER-4 COMPLETE PHOTO ETCH SET . . . . . postpaid $24.95
AT YOUR DISTRIBUTOR OR DIRECT (N. J. residents add sales tax)

The DATAK corp. • 65 71st St. • Guttenberg, N. J. 07093

HP: THE STANDARD OF COMPARISON IN TEST EQUIPMENT

Know your frequency...precisely.

$249* 10 Hz to 80 MHz.

Professional caliber gear with the precision of a seven digit LED readout at an unusually low price. The HP 5381A features a high-stability internal time base, 25 mV sensitivity, a three-position attenuator switch, external oscillator input and ratio measurement capability. All packed in a rugged metal, dust-free case.

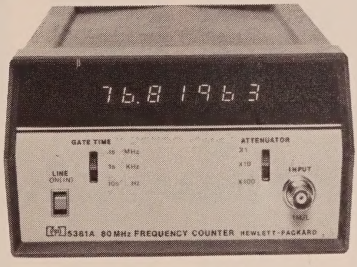

$450* 10 Hz to 225 MHz.

HP's 5382A Counter. All the features of the 5381 to 225 MHz. Plus an *eight* digit readout. Also, available with a temperature compensated crystal oscillator ($100*). Both instruments are backed by the full HP guarantee.

*Domestic USA prices only 02402

☐ Please mail me complete information on your new low-cost precision counters. (No salesman will call.)
☐ Please have a sales engineer telephone me.

Name _____
Address _____
City _____ State _____
Zip _____ Phone _____

HEWLETT hp PACKARD

Sales and service from 172 offices in 65 countries.
1501 Page Mill Road, Palo Alto, California 94304

SSB-ers:

increase talk power, cut "splatter"

Our *444 base station microphone* not only gives you increased talk power, but cuts "splatter" (and QRM complaints) to an absolute minimum! It has superbly tailored response, with sharp cutoffs below 300 and above 3,000 Hz and a rising response characteristic for maximum intelligibility. The 444's rugged, reliable Controlled Magnetic element has been proved in safety communications, and other tough professional communications applications. It delivers a clean signal to the transmitter at levels as high as crystal units! (And, unlike crystal and ceramic units, the element is totally immune to the effects of temperature and humidity.) The 444 also features an adjustable height stand that makes for comfortable "ragchewing" sessions, an optional-locking bar for push-to-talk or VOX operation, and a practically indestructible Armo-Dur® case. Write:

Shure Brothers Inc.,
222 Hartrey Ave., Evanston, Ill. 60204

SHURE

It's here...full line
HF SSB/ISB

OFF-THE-SHELF SERVICE

Whether for defense or commercial, Scientific Radio Systems is your best single-source for all HF SSB/ISB applications. Why? Because SRS engineers can and will customize your HF SSB/ISB communication system from their off-the-shelf full-line inventory.

That kind of service keeps your cost lower than you would expect. And it also keeps us number one for reliable trouble-free HF SSB/ISB systems being used the world over. Write to us now about HF SSB/ISB for:

- ☐ Point-To-Point
- ☐ Ground-To-Air
- ☐ Area Broadcast

FEATURES

- ☐ Up to 10 Channels (Frequencies)
- ☐ Telephone and Cable Remote Controls
- ☐ Simultaneous Voice and Data
- ☐ 1.6-30 MHz, 150W/1KW/10KW
- ☐ Multichannel TTY (±35, ±42.5, ±85, ±425)

Users include: U.S. ARMY, NAVY, AIR FORCE, COAST GUARD, ATOMIC ENERGY COMMISSION, NATIONAL WEATHER SERVICE, NASA, FAA, FCC, etc.

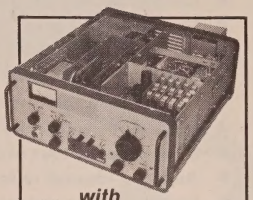

. . . with plug-in modular construction!

SR SYSTEMS

Take your pick.

☐ THIS EQUIPMENT IS ON THE GSA FEDERAL SUPPLY SCHEDULE

☐ MILITARY NOMENCLATURE & FSN'S EXIST FOR OUR ENTIRE LINE

Scientific Radio Systems

367 ORCHARD STREET
ROCHESTER, N.Y. 14606

CABLE SIRAD
TELEX 978-368
PHONE (716) 458-3733

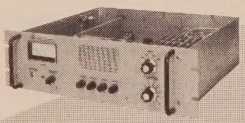

SSB RECEIVER
FSN 5820-971-8531

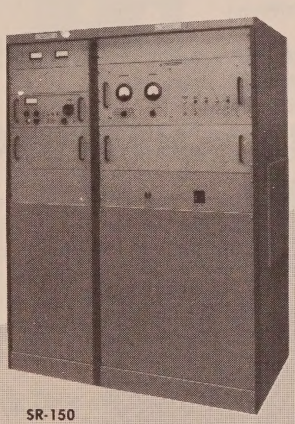

SR-150
10KW SSB/ISB
TRANSMITTER

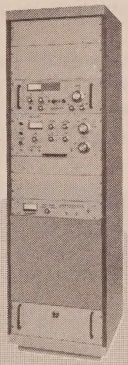

AN/URC-79
1KW SSB
TRANSCEIVER

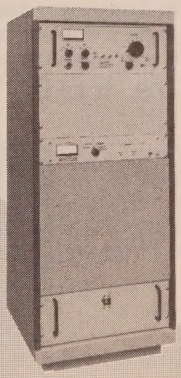

AN/FRT-91
1KW ISB TRANSMITTER

SR-808
SELECTIVE CALL

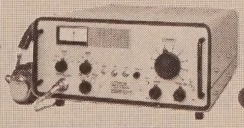

R-1883/URR ISB RECEIVER

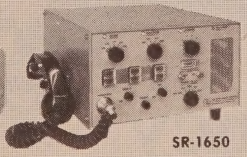

SR-1650
DIGITAL TELEPHONE LINE
REMOTE CONTROL

AN/URC-77
150W SSB TRANSCEIVER

The Ultimate F.M. Transceiver

Here it is, the FMer's dream, a fully synthesized transceiver that'll cover the entire two meter band, PLUS a built-in scanning receiver that'll locate any repeater frequency in your area that's in use.

And get a load of these other features that make the "Dream Machine" the ultimate rig:

- Operates on FM, AM or Modulated CW
- Built-in DC and AC power supplies
- Frequency Range of 143.5 to 148.5 MHz in 5 KHz increments
- Autoscan in 5 KHz steps across entire band, with adjustable speed and frequency limits.
- Synthesizer flexibility that offers choice of 600 KHz up or down, 1 Meg up or down, simplex, frequency split, or any nonstandard split (programmable) all from a single function switch.
- Receiver Sensitivity of 0.35 Mv for 12 db SINAD on FM
- Dual power output of 20 watts or 5 watts across entire band
- Adjacent channel rejection (30 KHz) 100 db minimum
- Image spurious and intermodulation (EIA) 80 db minimum
- 10 pole, 13 KHz crystal filter
- Receiver Superhet, single conversion
- Frequency stability of 0.0005%
- Built-in tone burst and PL encoders and decoders
- Built-in touch tone pad
- Full LED Digital readout
- Built-in S Meter also serves as VSWR bridge, power output meter, battery indicator, deviation indicator and discriminator meter.
- Audio output 4 watts @ 10% THD
- Speaker built-in to left side of cabinet for maximum mobile reception
- Headphone jack for noise-free mobile operation
- Independent selectable priority channel
- Built-in Auto CQ
- Temperature range from -20^{o} to 170^{o} Fahrenheit
- Size: 4" H x 8" W x 10" D Weight: 10 pounds
- One million channels (1000 Rec. x 1000 Trans.)

The EBC-144 "DREAM MACHINE"

$1495.00

A $150 deposit will insure early delivery and guarantee price

AMATEUR PRODUCTS DIVISION

emergency beacon corp.

15-RR River Street
New Rochelle, N.Y. 10801
(914) 235-9400

Is this the Atlas-180?

Well, not exactly. It's the SouthCom AN/URC-87(V) Man-Pack Military Radio. The URC-87 is a completely solid state portable man-pack and vehicular HF-SSB radio set for military, police, survey, and point-to-point communications throughout the world. It is today's and tomorrow's outstanding portable radio set.

So what does this have to do with the Atlas-180?

THE URC-87 and the Atlas-180 are what you might call 'first cousins.' Atlas Radio is licensed by SouthCom International, and thus has access to the advanced state-of-the-art circuit designs by Les Earnshaw, President of SouthCom. Les is widely recognized as one of the foremost solid state radio engineers in the world, and the URC-87 is an outstanding example of his work.

The Atlas-180 uses the same basic circuitry as the URC-87. There are some differences of course, such as a tuneable VFO in place of the frequency synthesizer, and we can't guarantee underwater operation. But the outstanding receiver and transmitter performance is there, and accomplished with far fewer components than any comparable equipment. Together the URC-87 and the Atlas-180 enjoy a reputation for performance and reliability that make them truly superior transceivers, the envy of competitors.

There are now over 1000 Atlas-180's on the air all over the world. Their growing reputation for excellent quality, receiver sensitivity, selectivity, and transmitter punch, all ties back to the URC-87. Immunity to overload and cross modulation from strong adjacent channel stations is nothing short of fantastic. Selectivity is provided by a new 8 pole ladder designed super filter, with shape factor and ultimate rejection superior to practically any other receiver or transceiver! And the front end design permits full utilization of the filter's capabilities.

The one area where we have an edge over the URC-87 is in transmit power, and that's because the Atlas-180 doesn't have to operate on self contained batteries. The 100 watts of output speaks out with real authority!

Modular construction with plug in circuit boards permits easy servicing, when required. However, built to top commercial specs, this isn't very often. But when service is needed, Atlas Radio backs every set with a service policy second to none. Your satisfaction is guaranteed.

73
Herb Johnson, W6QKI

Season's Greetings from all the Gang at Atlas Radio.

ATLAS RADIO INC.

490 Via Del Norte Phone (714) 433-1983
Oceanside, California 92054

See your Atlas dealer for complete details, or drop us a card and we'll be pleased to mail you a brochure and dealer list.

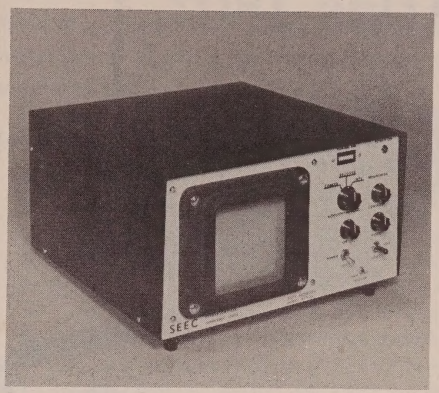

HCV /

Now from the designer of the world famous HCV-SSTV equipment, Dr. James Thomas, WB4HCV, is proud to announce the new and improved HCV-1B SSTV Camera and HCV-2A SSTV Monitor. Both are similar to those produced by Thomas Electronics, only much improved. The special features

SPECIFICATIONS – HCV-2A SSTV MONITOR

6.25" Diagonal Screen.
Removable Picture Tube Filter for added viewing flexibility.
Manual Vertical Trigger Pushbutton allows re-start of scan at any time.
Tuning Meter, instead of LED, to aid tuning of SSTV signal.
Noise immunity circuits and special filtering to allow for excellent "closed circuit" pictures under high noise conditions. Copy pictures with 3db or less signal strength.
The only SSTV Monitor with Transistors, ICs and Op Amps mounted in plug-in sockets on a G-10 glass epoxy gold flashed printed circuit board.
Built in 115/230 V 50/60Hz Power Supply. Fully shielded power transformer.
CRT (Picture Tube) burn protection and sweep failure protection. 11-14 KV adjustable anode voltage power supply provides very bright, sharp picture. Special CRT phosphur mix allows for black and white picture, with neutral density filter installed, instead of the usual yellow. Optional yellow/amber filter also provided.
29 Transistors, 11 ICs, 30 Diodes, Special Phosphor Mix CRT.
Optional Built In Fast Scan Viewfinder allows viewing of HCV-1B Camera or similar SSTV Camera fast scan sampling rate on the same CRT used for SSTV. By viewing the picture in real time, the camera can be focused and set-up instantly. Eliminates the need of a separate fast scan viewfinder monitor. Add $95.00., to basic HCV-2A price for this optional feature factory installed or purchase the HCV-70FSVFK modification kit for $69.95., and install it yourself.
Built to rigid industrial specifications for long trouble-free service. Full 1 year warranty-90 days on CRT. Printed circuit board exchange program and complete service department available if ever needed. 24 hour telephone answering service to better serve our customers.
Fully meets or exceeds all currently accepted SSTV standards-World-wide.
Size: 15½" deep, 14" wide, 8¼" high. Weight 26 lbs.
Color: Black and White or optional 2 tone gray when specified - no extra charge. Aluminum Cabinet.

HCV-2A SSTV MONITOR PRICES

Regular Price $425.00. Special Introductory Cash With Order Price $398.00. (Note: Credit Cards pay regular price $425.) F.O.B. Hendersonville, Tennessee. 5 ways to purchase: Cash, C.O.D., Mastercharge, Bank Americard, SEEC financing plan (up to 36 months). HCV-2A Monitor with built-in fast scan viewfinder $493.00. Regular Price $520.00.

MONITOR ACCESSORY LIST

Sony TC110A Cassette Tape Recorder
$134.95

Grey Scale Calibration Tape
$5.00 Cassette. $4.00 Reel

Pre-Recorded, Call Sign, etc. - Specify
$8.00 Cassette. $7.00 Reel

Blank Scotch Brand Tape:

	Cassette	Reel
45 minute	$2.00	$3.75 5" Rl
60 minute	$3.00	$4.25 7" Rl
90 minute	$4.00	$6.00 "
120 minute	$5.75	$8.50 "

HCV70FSVFK Fast Scan Viewfinder
Kit HCV-2A **$69.95**
Spare Printed Circuit Board
HCV-2A **$175.00**

If you need something not listed please call or write for price and delivery information.

SSTV

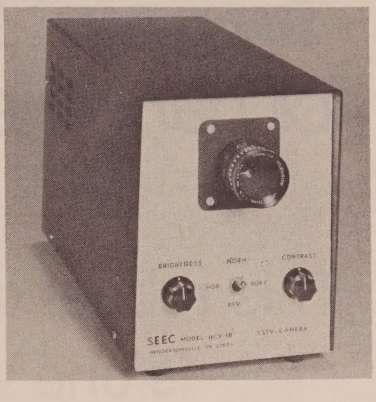

have now been patented and carry U.S. Patent numbers DD-033468 (Monitor) and DD-033471 (Camera). Watch for our new HCV-3KB SSTV keyboard and our Hard Copy machine, available soon. Call or write for complete specifications on all HCV equipment. We have 24 hour telephone answering service for your convenience.

SPECIFICATIONS-HCV-1B SSTV CAMERA

¼-½-3/4 Frame Rate Selector.
Positive/Negative (Black or White Background Color Reversal.
Normal-Reverse Horizontal Deflection Coil Switch (Mirror Image Reading).
The Only SSTV Camera With Transistors, ICs and Op Amps mounted in plug-in sockets on a G-10 glass epoxy gold flashed printed circuit board.
The Only SSTV Camera commercially made with a built-in power supply for 115/230 V 50/60 Hz, which does not produce 50/60 Hz hum bars in the slow scan picture.
F1.9-22 25MM Cosmicar TV Lens Supplied.
Fast Scan (sampling rate-5Khz horizontal, 15/30Hz vertical) R.F. or Video output for viewing fast scan on standard TV set-Channels 2-8 or on a video monitor to aid as a focusing aid only in camera set-up, etc. Fast scan sampling rates also available for connection to HCV-2A equipped with fast scan viewfinder modification, which displays fast scan in the same format as on slow scan, except in real time, to allow for instant focus and set-up of scene.
ALC Option. Automatic Light Control may be added if desired. This optional feature allows the operator to leave the iris of the lens at one F setting (all the way open if desired), as the camera will adjust itself to light changes automatically. The light can then be varied on the scene, thus eliminating adjustment of the lens opening or the camera Contrast control. Auto/Manual switch which allows the operator to return the camera to normal operation when ALC is not being used. Add $40.00 to basic HCV-1B price for this optional feature.
Fully meets or exceeds all currently accepted SSTV standards World-wide.
Built to rigid industrial specifications for long trouble-free service. Full 1 year warranty-90 days on Vidicon Tube. Printed Circuit Board exchange program and complete service department available if ever needed.
A separate lab facility is also available which is involved in making improvements and testing our new designs prior to production. Modifications, improvements, etc., are sent out as they are made. 24 hour telephone answering service to better serve our customers. Size: 6" wide, 8" high, 13¼" long. Weight: 12 lbs. (with lens). Color: Black & White or Optional 2 tone Gray - No extra charge. Aluminum Cabinet.
48 Transistors, 14 ICs, 26 Diodes. Industrial Grade 7735A Vidicon.

CAMERA ACCESSORY LIST

Heavy Duty Tripod		**$34.95**
Lenses: Cosmicar TV		
2514	**25mm F1.4-22 C-Mount**	**$40.00**
2519	**25mm F1.9-22 " " Std.**	**$35.00**
1219	**12.5mm F1.9-22 " " Wide Angle**	**$60.00**
Z-9015	**22.5-90mm F1.5 C-Mount Zoom Lens**	**$375.00**
504	**75mm F1.4 C-Mount Telephoto**	**$136.95**
2514DH	**25mm F1.4-22 C-Mount Macro Close up**	**$62.95**
EX-C6	**Extension Tube (Close-up) Kit C Mount**	**$15.95**
Close Up Lens for 2514 and 2519-Specify		**$14.95**
MC-1	**Microscope Adapter C-Mount**	**$6.95**
Spare P.C. Board for HCV1B		**$195.00**

If you need something not listed please call or write for price and delivery information.

HCV-1B SSTV CAMERA PRICES

Regular Price $75.00. Special Introductory Cash With Order Price $452.00. (Note: Credit Cards pay regular price $475.) F.O.B. Hendersonville, Tennessee. 5 ways to purchase: Cash, C.O.D., Mastercharge, Bank Americard, SEEC Financing Plan (up to 36 months). HCV-1B Camera with built-in ALC (Automatic Light Control)-Special Cash Price $492.00., Regular Price $515.00.

Sumner Electronics & Engr. Co. inc.

P.O. Box 572
Hendersonville, Tennessee 37075
Telephone: 615-824-3235

hy-gain 2-meter antenna for hand-held transceivers

144-148 MHz

This rubber duckie is one tough antenna!

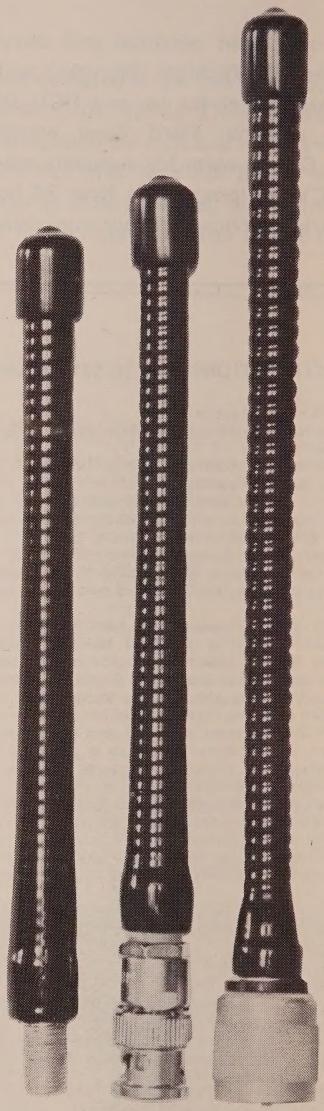

When the going gets tough, Hy-Gain's flexible 2-meter antenna is the one to have. So short, it goes where whips can't. Continuously loaded for optimum performance and completely insulated with a special vinyl coating, it won't crack or break, no matter how you bend it. Cannot be shorted out accidentally! Designed with the same care and excellence in engineering that produces our superb commercial and mobile antennas. Whether your 2-meter hand-held is one of the fine commercially available units or a beauty you built yourself, this is the antenna that can go where you go!

Available with three connector types and tuned for optimum performance:

Order No. 274 BNC or 'snap' fitting, fits Tempo, Wilson, Ken Product, Klegg and other popular hand-held 2-meter transceivers.

Order No. 275 Accepts SO-239 connector, fits Drake and Motorola.

Order No. 269 Male screw 5/6 x 32, fits Motorola, GE, Johnson, RCA and CommCo.

For information on the complete line of fine Hy-Gain Amateur products, see your Hy-Gain distributor or write:

hy-gain

Hy-Gain Electronics Corporation; 8601 Northeast Highway Six; Lincoln, NE 68507; 402/464-9151; Telex 48-6424
Branch Office and Warehouse; 6100 Sepulveda Blvd., #322; Van Nuys, CA 91401; 213/785-4532; Telex 65-1359.
Distributed in Canada by Lectron Radio Sales, Ltd.; 211 Hunter Street West; Peterborough, Ontario.

HENRY

ONE NAME GROWS STRONGER YEAR BY YEAR

When you buy a Henry Linear Amplifier, you buy quality, performance, reliability.. all the features that have made Henry amplifiers world famous. But most of all you buy the integrity of the Henry name.

Other brands have disappeared from the amateur scene...names that were familiar to all amateurs. Now those companies are gone and their equipment is orphaned.

But one name has grown steadily throughout the years. Today Henry amplifiers stand preeminent throughout the entire amateur world...symbols of the finest equipment you can buy.

Join the great family of happy Henry amplifier owners. Treat yourself to the best.

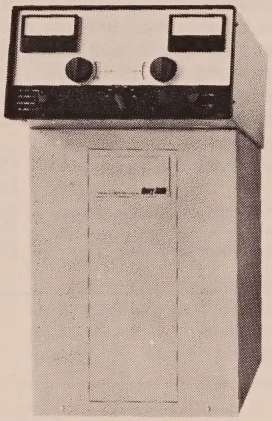

2K-4 . . .
THE "WORKHORSE"

The 2K-4 linear amplifier offers engineering, construction and features second to none, and at a price that makes it the best amplifier value ever offered to the amateur. Constructed with a ruggedness guaranteed to provide a long life of reliable service, its heavy duty components allow it to loaf along even at full legal power. If you want to put that strong clear signal on the air that you've probably heard from other 2K users, now is the time. Move up to the 2K-4. Floor console or desk model... $895.00

2K-ULTRA Small, rugged and reliable. Loafs along at full legal power without even the sound of a blower. Uses the best components available, including a pair of Eimac 8873 tubes. $895.00

TEMPO/2001 Small, reliable and inexpensive. Two Eimac 8874 grounded grid triodes, full kilowatt of output for SSB, built-in solid state power supply, antenna relay, internal blower, relative RF power indicator and full amateur band coverage from 80-10 meters. $595.00

3K-A Superior quality linear amplifier for commercial and military use. Two Eimac 3-500Z grounded grid triodes, three kilowatts PEP input on SSB with efficiencies in the range of 60%. PEP output in excess of 2000 watts. Provides a power supply capable of furnishing 2000 watts of continuous duty input for RTTY or CW with 1200 watts output. $1150.00

Henry offers a line of superb commercial high frequency amplifiers including the 4K-Ultra and 1K-4A Channelized Amplifier. Also solid-state Vhf and Uhf amplifiers up to 120 Watts.

Please call or write for full technical specifications. Henry Amplifiers are also available at select dealers throughout the U.S.
Export inquiries invited

Henry Radio

11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127

Prices subject to change without notice.

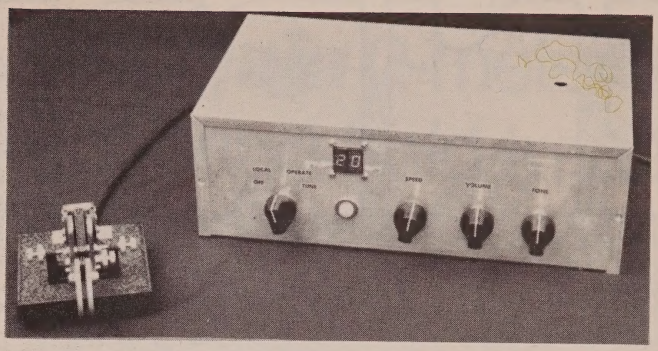

Front view of the prototype digital readout keyer showing control locations and functions. In use, the keyer displays the keying speed which the operator is sending at that time, and is updated every 1.2 seconds if the operator should increase or decrease his sending speed.

Digital Speed Readout In An Electronic Keyer

BY DON C. GILBERT,* WA2SKL/WA4SPD

HAVE you ever wondered exactly what speed you were sending? For instance, when preparing for the General exam you knew you could copy someone and send just as fast as him but you didn't know whether that speed was 15 or 10. This electronic keyer solves the problem because it provides a constant digital measurement of the speed you are sending, in words per minute. The measurement circuit can be adapted to other keyers, too.

Referring to fig. 1, the block diagram, we see that the basic keyer is Frank Van Cleef's "ICKEY,"[1] with automatic letter spacing.[2] This circuit has been redone for this keyer using the newer TTL logic, which is cheaper and more reliable than the old RTL. This circuit was chosen because of the dot and dash memories, which are both convenient and allow a free-

*10 Russet Rd., RD 1, Poughkeepsie, NY 12601

[1]Van Cleef, "ICKEY — An Integrated Circuit Electronic Keyer with Dot and Dash Memories," *QST*, Nov. '68.
[2]Van Cleef, "Automatic Letter Spacing for ICKEY," *QST*, Feb. '69.

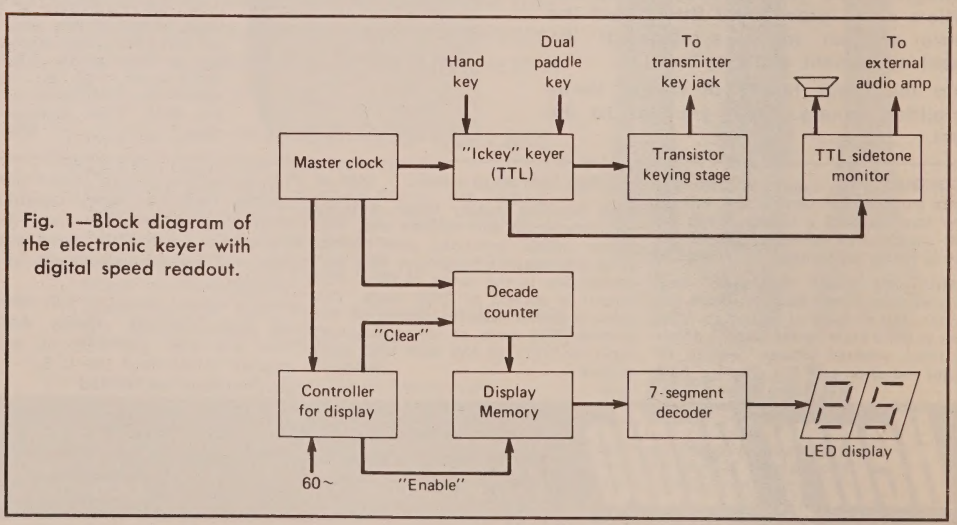

Fig. 1—Block diagram of the electronic keyer with digital speed readout.

running clock, which is necessary for the digital measurement. The master clock is really the heart of the whole circuit, because it not only drives the keyer but also is input to the digital measurement circuit. The clock is similar to the one used in the HAL 1550 keyer.[3] The output of the keyer is used to drive a sidetone monitor and a high voltage transistor keying stage, both also from the HAL 1550.

The digital measurement circuit is based on the formula from *The Radio Amateur's Handbook:*

$$\text{Speed (w.p.m.)} = \frac{\text{dots/min.}}{25}$$

This formula is based on standard values for "correct" c.w.: one unit pulse per dot, one unit pulse per space, three unit pulses per dash, and three unit pulses between letters. The ICKEY keyer will allow no other values, except a longer time between letters. Assuming that the operator is not waiting a long period between letters and words, the formula can be restated,

Speed (w.p.m.) = *Number of dots in 2.4 seconds.*

Since the master clock is running at twice the speed of the dots, (each master clock pulse is a "unit pulse" referred to above) all we have to do is count how many clock pulses appear in the space of 1.2 seconds and that number will be the speed in w.p.m. the keyer is sending. The digital measurement circuit does this by letting a decade counter count the pulses from the master clock for exactly 1.2 seconds (this period is obtained by counting, with another counter, 72 cycles from the 60 Hz line voltage), and then displaying that value. The display memory shown in the block diagram is necessary so that while the decade counter is counting, a constant number can be displayed. The output of the display memory is in binary coded decimal (BCD), required by the light-emitting diode (LED) readout. The result is a two digit display of the keying speed, which is changed every 1.2 seconds if the keying speed changes and otherwise stays constant.

[3]"HAL 1550 Electronic Keyer Instruction Manual," HAL Communications Corp., Box 365, Urbana, Illinois 61801.

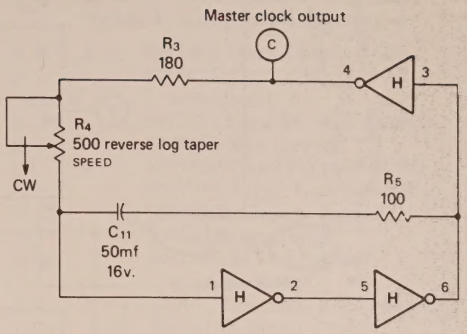

Fig. 2—Circuit of the keyer master clock (similar to that in the HAL 1550 keyer).

Master Clock

The master clock shown in fig. 2 produces square pulses which are "high" (over 3 volts) about half of each cycle and "low" (around ground) the rest of the cycle. Potentiometer R_4 varies the period of each cycle from about 20 milliseconds, or 60 w.p.m. to about 200 milliseconds, or 6 w.p.m. The value of R_3 may be adjusted to change the lowest and highest speeds. R_4 is reverse log taper to make the speed adjustment more linear.

Power Supply

The power supply shown in fig. 3 is designed to provide three voltages to the rest of circuit: 5.0 volts regulated for Vcc in all integrated circuits plus the LED's, a "logic high" voltage for connection to all gate inputs which must always remain in the high state, and a 120 Hz square wave which drives the "controller" for the display. The 5 volt regulated is formed with

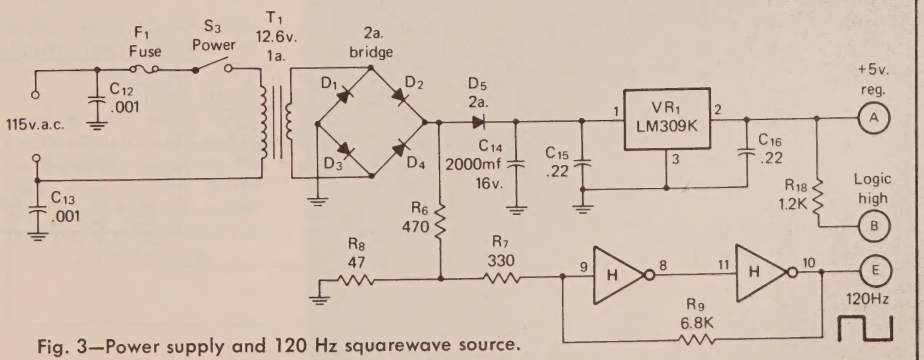

Fig. 3—Power supply and 120 Hz squarewave source.

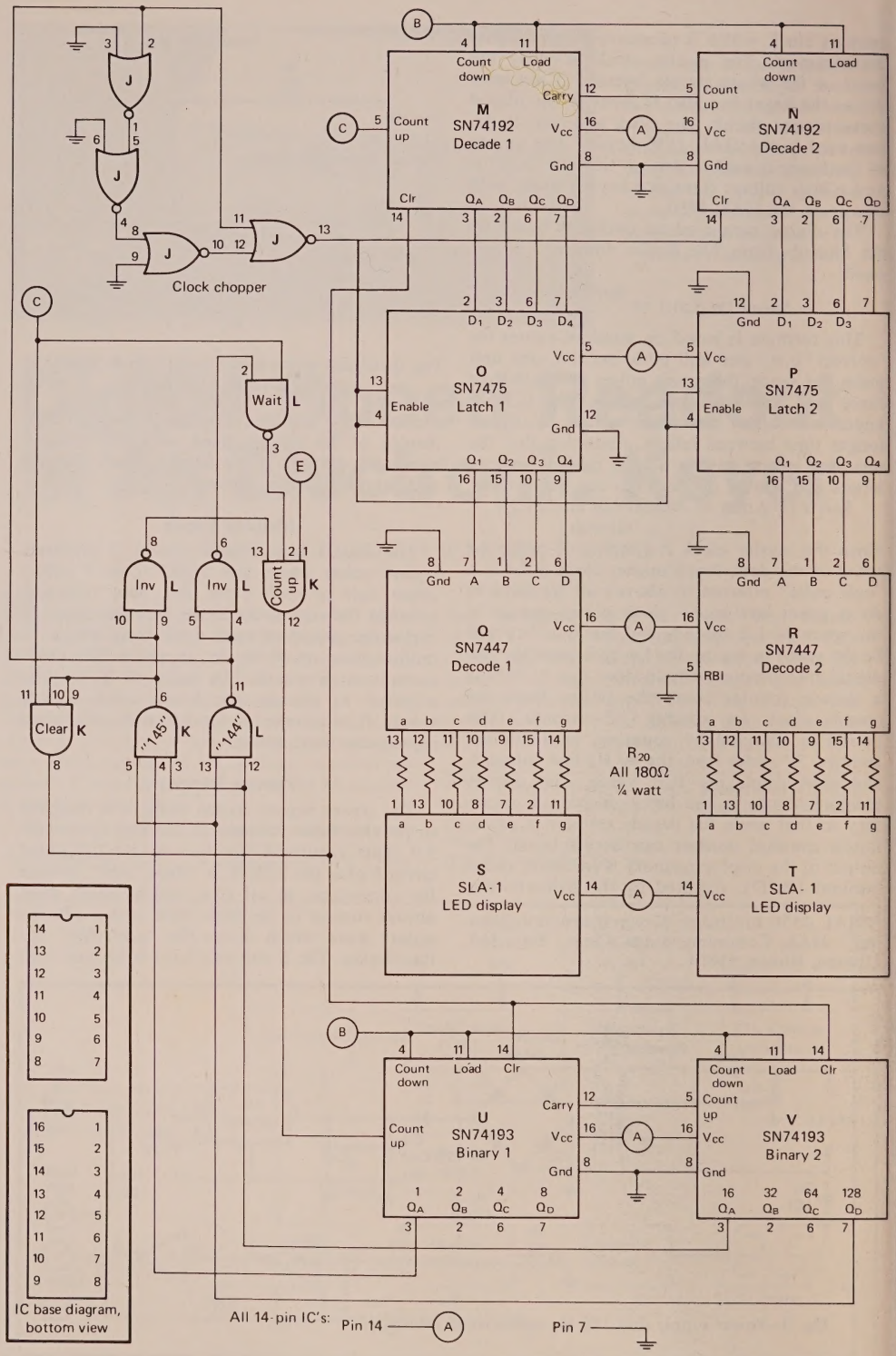
Clock chopper
M
SN74192
Decade 1
N
SN74192
Decade 2
O
SN7475
Latch 1
P
SN7475
Latch 2
Q
SN7447
Decode 1
R
SN7447
Decode 2
S
SLA-1
LED display
T
SLA-1
LED display
U
SN74193
Binary 1
V
SN74193
Binary 2
Wait
Inv
Count up
Clear
"145"
"144"
R20
All 180Ω
¼ watt
IC base diagram,
bottom view
All 14-pin IC's:
Pin 14
Pin 7

Fig. 4—Display controller circuit. Circled letters in this and other diagrams refer to interconnections between circuit elements in figs. 2 through 6.

Table I—Integrated Circuits

A, B, C, E, J, D	SN7402 Quad 2-input NOR. SN7425 Dual 4-input NOR with strobe.
E, G	SN7476 Dual JK M/S flip flop.
H	SN7404 Hex inverter.
I, L	SN7400 Quad 2-input NAND.
K	SN7411 Triple 3-input AND.
M, N	SN74192 Decode counter.
O, P	SN7475 Quad latch.
Q, R	SN7447 BCD-7 segment decoder/driver.
S, T	SLA-1 7-segment LED readout.
U, V	SN74193 Binary counter.
VR[1]	LM309K 5 v. 1 a. voltage regulator.

a 12 volt 1 amp transformer, a bridge rectifier and a filter, and an LM309K voltage regulator. Capacitors C_{15} and C_{16} are needed by the VR for transient protection. The "logic high" voltage is taken through a 1.2K resistor, R_{18}, connected to the regulated voltage. The 120 Hz square wave is formed by the "Schmitt trigger" circuit of R_6 through R_9, and the two inverters H. Diode D_5 is needed to isolate the Schmitt trigger from the power supply filter.

Digital Display

Referring to fig. 4, we see that the decade counter which counts the clock pulses is composed of the two IC's M and N. Each time a clock pulse changes from low to high, M counts to the next higher number. When it gets to 9, its "carry" line propagates the count to N. As long as the "clear" line (pin 14 on both M and N) is low, counting takes place on each clock pulse. When the "clear" line goes high, the count returns to zero. It is the function of the "controller" section, (J, K, L, U, V) to let the counter count and reset (clear) it at the proper times. The display memory is formed by IC's O and P: each contains four "latches" or memory elements. When the "enable" line (pins 13 and 4 on both O and P) is high, the outputs are the same as the inputs. But when the enable line goes low, the outputs stay as they are regardless of how the inputs change. This fact is used to provide a constant display: while M and N are counting, the enable line is held low so that the last speed is still displayed. But when the new 1.2 second count is complete, the enable line is brought high which lets the new speed show. If the new speed is the same as the old (which is always the case unless the operator is changing the speed pot) the display never changes.

Q and R are BCD to 7-segment decoders which convert the count from the display memory into the 7-segment enable lines a-g on each IC. When a certain segment is supposed to be lit, the corresponding line for that segment goes to ground potential, so Vcc conducts through the LED and current-limiting resistor to ground, lighting the segment. Opcoa SLA-1 LED readouts were chosen for this circuit because of their large size (.334" character size) and relative cheapness, but other LED's could be used by changing the values for the current-limiting

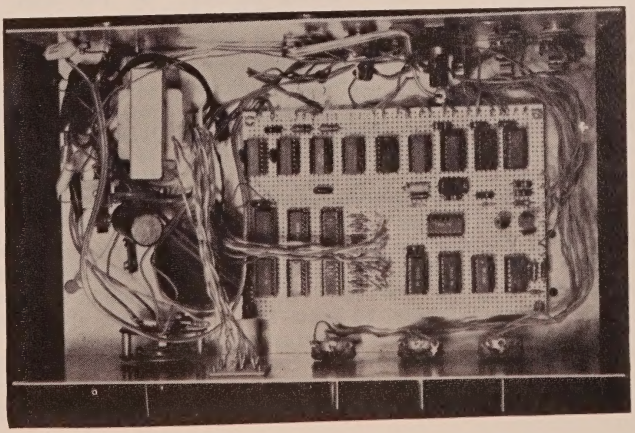

Interior view of the keyer showing parts placement. With the exception of the power supply, the entire keyer is built on a single piece of perfboard. Along the top of the board are the keyer and sidetone generator IC's while the master clock and display control IC's are at the bottom.

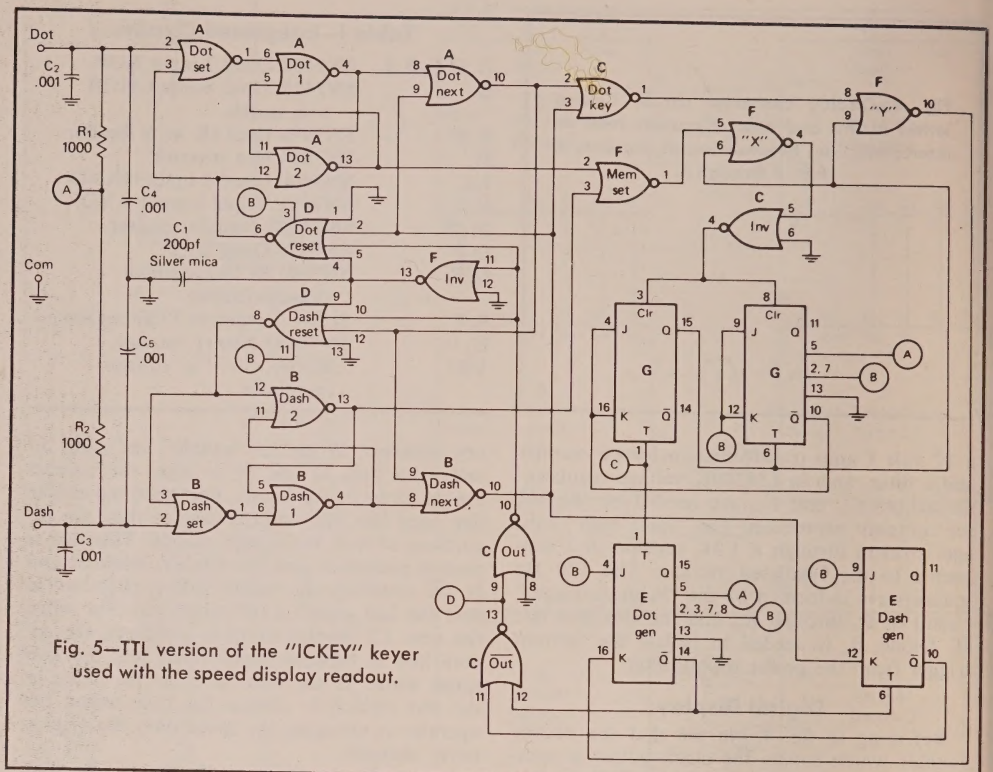

Fig. 5—TTL version of the "ICKEY" keyer used with the speed display readout.

resistors R_{20}.

The "controller" section shown in fig. 4 is the key to the operation of the digital display. Since it operates directly from the 60 Hz line voltage, it is usually very accurate and never needs adjustment. This means that even if the digital display is used with a keyer whose speed drifts considerably, the display will always show the exact speed at which the keyer is running.

Normally, pins 2 and 13 of COUNT UP are high, allowing the 120 Hz square wave to count the binary counters U and V. During this time, pin 8 of CLEAR is low allowing the decade counters M and N to count the clock pulses, and pin 13 of J is also low, keeping the changing count from affecting the value displayed from the memory O and P. When pin 3 of V *and* pin 7 of V go high, indicating that a count of 144 120-Hz pulses, or 1.2 seconds, has been reached, pin 11 of "144" goes low, which does two things. First, this low is inverted to a high on pin 2 of WAIT, which inhibits COUNT UP from letting the 120 Hz square wave through to count up U until the clock pulse is in a *low* state. Second, the low from "144" causes pin 13 of J to go high, letting the count from the decade counters M and N go into the memory O and P and be displayed. If this enable were left high too long, the decade counters would continue counting and the display would change. So the "clock chopping" circuit on IC J is used to turn the high on pin 13 of J back off after about 30 nanoseconds, just enough time for the count to get through the memories O and P. This circuit is really a 30 ns monostable multivibrator.

Once the clock goes into a low state, the COUNT UP gate lets the 120 Hz through and U and V count one more pulse, up to a count of 145. But at this point, pin 3 of U and pins 3 and 7 of V all become high which drives pin 6 of "145" high. This causes pin 13 of COUNT UP to go low, inhibiting any more counting in the binary counters, and also brings high pins 9 and 10 of CLEAR. The circuit was not allowed to count to 145 until the clock pulse was in a low state, so at this point the circuit waits until the clock pulse becomes high again. When it does, pin 8 of CLEAR goes high, clearing both the decade counters M and N and the binary counters U and V. This in turn makes pin 6 of "145" go low again, and all counters start counting from zero.

The critical feature in the design is that because of the gates WAIT and CLEAR, the controller always starts both counters (binary and decade) at the very moment the clock pulse goes from low to high, and never at any other point within the period of the clock pulse. This means that the 1.2 second period always counts

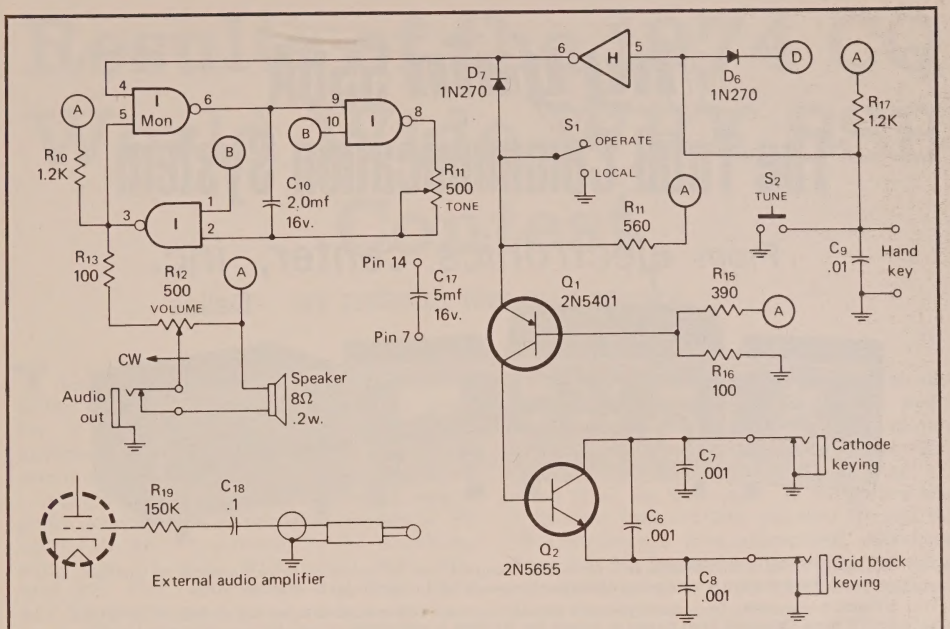

Fig. 6—Sidetone oscillator and keying output circuits.

the same number and last digit "jitter" is eliminated.

Keyer

As shown in fig. 5, the keyer circuit is the same as Van Cleef's ICKEY, except that the logic used is TTL. A comparison with the original circuit will show that the flip flops (G and E) are connected differently. This is due to a difference in function between the RTL IC's (which toggled, or reversed states, when both J and K were low) and the TTL (which toggles when J and K are high). The bypassing here and in the other circuits is necessary to prevent r.f. interference.

Sidetone Monitor

Referring to fig. 6 we see that the sidetone monitor oscillator, I, is similar to the master clock, except that it is turned on and off by gate MON. Pot R_{11} controls the frequency of oscillation. The speaker is driven directly by the IC, so capacitor C_{17} is connected directly from Vcc to ground on I to improve regulation. An external audio amplifier may also be driven, such as the audio stage in a receiver, but coupling capacitor C_{18} should be used if one is not already present in the circuit, and R_{19} should be used for isolation.

Keying Stage

The keying stage is also shown in fig. 6. Diode D_6 and resistor R_{17} allow a hand key and the tune switch to be connected to drive the output. The diode D_6 isolates the hand key from the keyer circuit. Resistor R_{17} allows pin 5 of H to follow the level of pin 13 of OUT, but keeps from shorting Vcc to ground when the hand key is closed.

Switch S_1 defeats the output stage in the "local" position, allowing the operator to practice with the keyer while it is connected to the transmitter without keying the transmitter. In the "operate" position, Q_1 acts as a common-base amplifier to drive Q_2 from non-conduction into conduction. Q_2 can key either (but not both) a positive voltage to ground, like a cathode-keyed transmitter, at a maximum of 250 volts, 100 ma, or a negative voltage to ground, like a grid-block keyed transmitter, at a maximum of −150 volts, 100 ma. If the transmitter to be keyed has a shaping capacitor across the keyed line, a resistor should be selected which does not affect the keying of the transmitter and put in series with the keying line.

Construction

The entire keyer, except power supply, fits nicely on Vector 64P44-062EP 6.5″ × 4.5″ prepunched board. IC sockets were used for convenience in experimentation, but are not necessary. Vector Zip terminals (T42-1) proved convenient in making connections on the board as well as connections to points off the board.

[*Continued on page 71*]

hy-gain 550A

The Total Communication System

From electronics center, inc.

Dallas

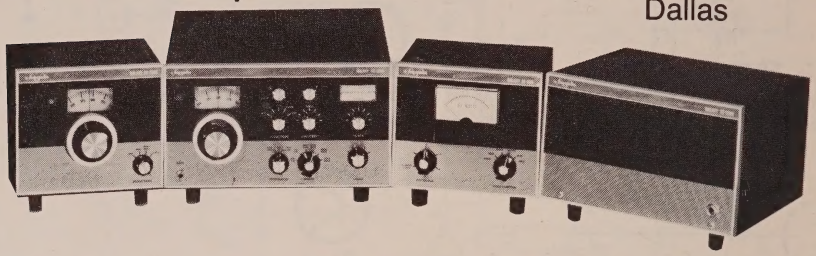

The Hy-Gain 550A is the complete amateur system. Designed from the ground up to work together for total performance. Each element is matched to the system, for simple, plug-in expansion of your capabilities.

GT-550A Transceiver The matchless heart of the 550A System. No other transceiver can give you this performance for the price. Operating fixed station or mobile, the GT-550A is guaranteed to have top frequency stability after warm-up. A graph showing stability during final check-out is included with each unit. 25 KHz calibrator and VOX, optional.

Frequency Coverage – 3.5-4.0, 7.0-7.5, 14.0-14.5, 21.0-21.5, 28.0-29.0 MHz crystals supplied. Other 10 meter coverage optional. Power Output – 300 watts PEP (nominal) on SSB, 180 watts on CW and RTTY, into 50 ohm resistive load.

Harmonic and Spurious Radiation – Carrier suppression in excess of 45 db down, unwanted side bands minus 55 db oscillator feed through and mixer spurious products down 50 db. Second harmonic minus 40 db and third order distortion in excess of minus 45 db.

Noise Level – In excess of 40 db below single tone carrier.

Audio Frequency Response – Minus 6 db approximately 300/2400 Hz determined by side band filter.

RF Compression Characteristics – Up to 10 db RF compression without distortion.

Receiver Sensitivity – Better than .5 uv for 10 db S+N/n ratio.

Receiver Selectivity – 2.1 KHz with 1.8 shape factor for SSB or 300 Hz sharp selectivity with optional CW filter.

Receiver Spurious Response – Image rejection better than 40 db down. Internal spurious below 1 uv equivalent input.

Frequency Calibration – Interpolation to 1 KHz in 5 KHz increments.

Frequency Stability – Within 10 Hz during any 30 minute warm-up period, less than 100 Hz in any 15 minute warm-up period, not more than 100 Hz with a plus or minus 10% line voltage variation.

Calibration Accuracy – Interpolation to 1 KHz after calibration.

Back Lash – Not more than 50 Hz.

Output Impedance – Variable 50 ohms nominal capable of matching up to 2-1 SWR (30-100 Ohms).

Automatic Volume Control – Fast attack, slow release on all receiver modes.

Order No. 855

RF550A contains high accuracy watt meter; calibrated in 400 and 4,000 watt scales; switch for forward or selected power; switch to select 5 antennas or dummy load. Order No. 857

RV550A is a solid state VFO. Function switch selects the remote unit to control Receive-Transceive-Transmit frequency independently. Order No. 856

SC550A Speaker Console with headphone jack. AC400 power supply will mount inside. Order No. 858

AC400 Power Supply is heavy duty solid state to operate GT-550A at full power, on SSB or CW, and with switch selection of 115/230 VAC, 50/60 Hz input voltages. Order No. 801

G-1000 12V D C Mobile power supply with cables. Order No. 802

Electronics Center carries complete lines of Ham equipment, accessories and antennas. Write or call Walt, W5ZYA or Al, W5PXH for your HAM needs.

electronics center, inc.

2929 N. Haskell • Dallas, TX 75204 • 214/526-2023

Home of the world's largest Electronic Flea Market. It's free! First Saturday of each month.

Results of the 1974 CQ World Wide WPX SSB Contest

BY BERNIE WELCH,* W8IMZ

THIS was a good one—providing the measurability of "good" is based upon the total number of logs received. The eighteen percent increase over last year's number of logs would certainly justify this.

Activity by a considerable number of unique prefix goodies, such as the large number of PS and PT1's thru 9's, provided by the Brazilians, along with U5, HG8, VX1, and 2, WS7, PI1, FPØ, EI1, CV2, VA6, WM5, 4JØ, CQ6, LH2, RI8, XX6, RB5 and LAØ helped make this contest a success, even though band conditions continued to deteriorate. Many stations missed taking the extra multiplier for WA2KGY/4X, which counts as 4XØ for WPX.

Around the clock pile-ups were attributed to semi-rare DX stations XU1, A51, PJ9, 5B4, ZB2, JD1, VP5, HV3, 9M2, OD5, CR4, CR5 and EA6, 5Z4 and CN8.

PJ9JR came through with the high score of the contest and won top world honors in the multi-operator, single xmitter category. Jack, W3ZKH and Ray, WA3IAQ DXpeditioned to Curacoa, Netherlands Antilles especially for this contest. Jack commented, "had plenty of everything except sunspots. Conditions were marginal at best, but enjoyed every QSO." Some of the other expedition stations were: VP2EEC, VP2GGG, FPØBG, 5Z4OY/A, JD1YAH, and VP5CW. We expect to have a special trophy award made available starting with the '75 contest for the top scoring station in this category (multi or single transmitter) provided there is increased participation and three or more groups continue to submit their logs.

K6UA is the winner of the single-operator all band W4OPM Memorial Award. Dale did an excellent job of racking up 665,808 points from California. In keeping with *CQ* policy of not awarding a major trophy to the same station two years in succession, W2PV will be awarded a special *CQ* Award for USA high score.

The only 160 meter entry was WB8APH. Wallace is congratulated for his efforts. Wish we had more WPX activity on this band.

*7735 Redbank Ln., Dayton, Ohio 45424

W6ONV operated by WA9UCE is an all-time high 14 mHz score for California, under the current WPX contest rules, and second only to W3AU in this year's stateside competition. Thanks for all the extra activity and logs received from the west coast. In fact, there was an increase from the 2nd, 4th thru 7th and 9th US Districts and it is appreciated. Also how about that big increase in the number of world wide multi-operator, single transmitter stations? Could this indicate a trend?

Before we became engulfed in a stack of mail questioning the listing of UK6APA I feel clarification is in order. The log clearly states that they operated on the top of an 1100 ft. mountain, near the Black Sea within Asiatic Russia. Most stations did not take the correct number of points for this one since USSR normally assigns a call like this to Europe.

LU5HFI operated by F5QQ is probably the final contest activity for that station. Ron indicates he may be operating from an exotic African location in next year's event.

The 10 meter score of CE6EZ was limited only by the amount of activity on that band because according to Ralf, the band was wide

This is Kohsaku, JD1AJD/JA7KAC operating JD1-YAH, who along with 5 other Japan DX Association ops made Ogasawara Island and the rare JD prefix available with over 2700 completed contest QSOs.

TROPHY WINNERS

WORLD—Single Operator, Single Band. Jack Reichert, W3ZKH Trophy. Won by: **Club Station YU2CDS.** (Opr. Davor Milosevic, YU2RNC, 14mHz).

WORLD—Single Operator, All Band. Don Murray, K4FMA Trophy. Won by: **Victor Manuel Ramos Pereira, CQ6LF.**

WORLD—Multi-operator, Single Xmtr. Ted Thorpe, ZL2AWJ Memorial, awarded by Don Miller, W9WNV. Won by: **Station PJ9JR.** (Oprs. W3ZKH, and WA3IAQ.)

WORLD—Multi-operator, Multi Xmtr. Chuck Swain, K7LMU Memorial awarded by Don Miller, W9WNV. Won by **Station CV2T.** (Oprs. CX1BBL, CX3BH, CX4AAC, CX4CR, CX8BBH, CX9BT.)

CANADA—Single Operator, Single Band. Gene Krehbiel, VE7DKS Trophy. Won by: **Station VX2AS.** (Opr. Stan L. Parsons, VO2AS, 14 mHz.)

U.S.A.—Single Operator, All Band. Charles "Joe" Hiller, W4OPM Memorial, awarded by Jerry Hagen, WA6GLD. Won by: **Dale Hoppe, K6UA.**

U.S.A. — Single Operator, Single Band. Charles "Joe" Hiller, W4OPM Memorial, awarded by The Virginia Century Club. Won by: **Station W3AU.** (Opr. Robert G. Cox, K3ES1, 14 mHz.)

SPECIAL CQ AWARD—Station W2PV

open. G3JUL indicates this was his first appearance on the contest scene for over ten years. I'm sure happy he picked the WPX to get back in the action, as did Gordon, VK2OW, an old timer on c.w. who acquired an s.s.b. rig just in time to work his very first phone contest.

Brother Ed, HV3SJ had planned a multi-operator weekend, but due to circumstances, went it alone and gave many a new and much sought after prefix. Is it possible that the HV1 prefix could be activated for the next one?

The North Florida DX Association's VP5CW operations stirred up a lot of activity for stations seeking new countries. That was a FB effort and I'm sure all WPXers appreciate it.

The VA6 prefix used by the Wizard Lake DX Club station VA6WDX was assigned to celebrate 100 years of RCMP in Alberta. Here in the USA, the special WM5BIL call was assigned to celebrate the 275th anniversary of the founding of the city of Biloxi, Mississippi and was operated by the Mississippi Coast Amateur Radio Association, and thanks to K5YIN for supplying the information. WS7MVM was a special event operation by the Boeing Employees Amateur Radio Society to mark man's first two planet missions, the Venus and Mercury encounters. The call ZB2WPX did not just happen. It was only through the efforts of Jimmy ZB2BL, assisted by ZB2CX that this special call was activated for the contest period.

I imagine that some of you who have made suggestions for changes in rules, dates, etc., feel that they are given low priority. However, I assure you each suggestion is carefully considered by the committee. In a world-wide event the rules must be as fair as possible for all areas of the world and stability of dates is most necessary. It takes a few years to determine if changes are in the best interest of all contestants.

Now is the time to make your plans for the

[*Text continued on page 70*]

TOP SCORES

SINGLE OPERATOR ALL BANDS

CQ6LF	**1,936,938**	LU8AJG	1,072,500
CN8BO	1,907,880	KS6DH	1,046,446
LU5HFI	1,780,600	5Z4OY/A	958,353
YV6AW	1,673,660	**W2PV**	**878,738**
KH6RS	1,235,208	VP2GGG	836,565
CX1JM	1,216,212	DK8FZ	822,617

SINGLE OPERATOR SINGLE BAND

28 mHz		21 mHz	
CQ6OR	424,815	CR6OZ	661,680
CE6EZ	266,668	KH6IJ	270,060
YV4YC	73,260	K6SDR	231,150
JR1INZ	43,733	WB6EJV	158,130
4X4QG	41,736	WA6QFY	153,153
K6SVL	24,278	PY1BDU	148,035

14 mHz			
YU2CDS	**845,568**	K6OVJ	247,866
W3AU	**724,822**	I4BMJ	180,958
DK1FW	510,402	K5PFL	171,520
UJ8JGJ	509,787	W6RTT	135,044
KH6GMP	477,246	**3.8 mHz**	
SM1CNS	455,445	YU4EBL	244,818
7 mHz		I3MAU	215,940
OH2KI	259,440	DL8PC	208,278
W6PAA	253,946	YV4TI	176,064
		OH1XX	170,624
		HA4KXC	143,040

MULTI-OPERATOR

Single Transmitter

PJ9JR	**4,543,618**	PS7BDX	2,519,700
PY2CAB	3,647,904	UK6APA	2,094,666
4X4NJ	2,845,905	VP5CW	2,000,985
UK9ABA	2,530,098	YU1BCD	1,613,920

Multi Transmitter

CV2T	**2,859,213**	SK5AL	1,031,916
SV1GA/5B4	2,819,945	JD1YAH	678,679

U.S.A. TOP SCORES

Single Operator

All Band	W2PV	878,738
28 mHz	K6SVL	24,278
21 mHz	K6SDR	231,150
14 mHz	W3AU	724,822
7 mHz	W6PAA	253,946
3.8 mHz	W7YTN	85,888
1.8 mHz	WB8APH	504

Multi Operator

Single Xmtr.	WA6GLD	137,250
Multi Xmtr.	W5NOP/5	279,720

Number groups after call leter denotes: Band, Score, QSO's and Prefixes. Bold listings are certificate winners.

SINGLE OPERATOR

North America

United States

K1CSJ	**A**	**509,694**	**765**	**263**
WA1STN	"	74,448	230	132
W1MDO	"	12,608	83	64
W1GYE	14	630	17	15
W1WY	**7**	**2,244**	**34**	**33**
W2PV	**A**	**878,738**	**956**	**322**
		(Opr. WB2SQN)		
WA2EAH	"	228,684	428	204
W2LEJ	"	43,320	144	114
WB2JJN	"	38,658	154	102
K2BQO	**14**	**325,945**	**546**	**235**
WA2ECC	"	32,103	135	87
K2KUR	"	3,840	45	40
K2LWR	**3.8**	**66,608**	**237**	**92**
W2NIN	"	63,518	210	91
WB2FGA	"	4,320	62	40
W3HVM	**A**	**12,871**	**86**	**61**
W3YHR	"	2,988	43	36
W3AZD	**28**	**11,715**	**90**	**55**
WA3HRV	**21**	**75,190**	**218**	**146**
W3AU	**14**	**724,822**	**823**	**322**
		(Opr. K3EST)		
WA3VUC	"	79,497	256	121
K3ZOL	"	78,952	214	139
W3CRE	**7**	**10,560**	**122**	**55**
W4WRY	**A**	**177,300**	**265**	**170**
K4YFQ	"	81,420	238	138
WB4SIJ	"	46,560	157	120
WB4TBO	"	43,641	159	117
K4OD	"	24,645	123	93
K4ADT	"	17,352	104	72
K4ZA	"	13,561	90	71
W4UYC	"	8,320	67	52
W4KMS	"	6,528	63	51
WB4RUA	"	455	16	13
W4OZF	**28**	**4,738**	**73**	**46**
W4WSF	**21**	**67,536**	**216**	**134**
W4CYC	"	20,501	107	83
K4EKJ	**14**	**51,062**	**164**	**121**
K4SGL	"	50,173	170	131
WB4TPU	"	17,025	89	75
W4EEO	"	1,725	25	25
W4JUK	"	176	8	8
WA4APG	**7**	**9,100**	**57**	**50**
WA5STI	**A**	**67,564**	**259**	**133**
W5BE	"	50,941	212	121
WA5ZWC	"	25,920	140	96
W5LPO	"	25,480	139	98
W5OB	"	3,616	41	32
WB5KWU	"	2,898	67	46
K5DEC	"	1,908	41	36
WB5GYF	28	102	6	6
W5RTQ	**21**	**33,633**	**152**	**101**
WB5FKX	"	11,160	80	62
K5FKD	"	1,440	26	24
WA5LES	**14**	**111,687**	**322**	**177**
K5PFL	**7**	**171,520**	**348**	**128**
WA5LUM	"	15,000	139	75
WA5VDH	**3.8**	**13,600**	**120**	**68**
K6UA	**A**	**665,808**	**1007**	**208**
W6UFJ	"	225,318	516	141
W6BJB	"	106,560	364	111
WA6MWG	"	51,290	168	115
W6KYA	"	28,475	148	67
WA6WUJ	"	22,344	122	98
WA6NBY	"	21,128	110	76
WA6TKT	"	14,896	117	76
W6YVK	"	10,948	81	68
W6SC	"	10,797	73	61
W6CLM	"	7,304	64	44
K6SVL	**28**	**24,278**	**150**	**61**
K6SDR	**21**	**231,150**	**678**	**115**
WB6EJV	"	158,130	530	105
WA6QFY	"	153,153	474	119
W6ONV	**14**	**406,087**	**749**	**209**
		(Opr. WA9UCE)		
W6AM	"	27	3	3
W6PAA	**7**	**253,946**	**473**	**119**
K6OVJ	"	247,866	495	109
		(Opr. WB6VZI)		
W6RTT	"	135,044	326	98
WA6UFY/6	"	88	11	11
VE63DXV/W6				
	3.8	**50,736**	**171**	**84**
WA7MEO	**A**	**392,570**	**751**	**185**
W7JUO	"	10,374	70	57
K7IDX	**"**	**28,390**	**45**	**13**
W7EXM	"	15	9	5
K7RSC	**14**	**284,410**	**664**	**170**
VE7ZZ/W7				
	"	214,970	514	166
WS7MVM	"	71,478	501	114
W7AYY	"	27,058	148	83
W7YTN	**3.8**	**85,888**	**262**	**88**
W8IMZ	A	38,098	158	101
K8PYD	"	60	5	5
W8KOD	**21**	**4,212**	**51**	**39**
WA8TBQ	**14**	**249,075**	**433**	**225**
W8CNL	"	58,646	178	142
WA8VMQ	**7**	**50,400**	**190**	**100**
WA8LXJ	"	19,760	96	76
WB8HLI	"	832	66	32
K8DVV	**3.8**	**36,792**	**302**	**73**
W8FJS	"	4,128	57	43
WB8APH	**1.8**	**504**	**60**	**21**
W9LT	**A**	**227,880**	**427**	**216**
WB9EBO	"	30,870	114	98
K9CLO	"	19,872	119	92
K9EGA	**21**	**10,850**	**86**	**62**
K9TZH	**14**	**254,421**	**413**	**243**
W9IY	"	222,444	405	222
W9YRA	"	66,360	200	140
WA9HEU	**7**	**13,728**	**95**	**66**
WB9HAD	"	10,303	119	59
WB9IND	"	1,140	38	30
WAØVPN	**A**	**20,672**	**121**	**76**
KØPMZ	**7**	**14,400**	**135**	**72**
WA2WMT/Ø				
	"	13,640	77	62
WAØEMS	"	7,080	114	60

Anguilla

VP2EEC	**A**	**93,522**	**347**	**109**
		(Opr. K2FJ)		

Bermuda

VP9AD	**A**	**155,700**	**314**	**150**
VP9GO	**14**	**425,220**	**734**	**228**

Canada

VE1RQ	**14**	**72,485**	**225**	**133**
VX1AW	**A**	**106,492**	**248**	**158**
VX2AS	**14**	**281,060**	**662**	**188**
VE3GCO	**A**	**45,156**	**169**	**106**
VE3BBH	**14**	**232,988**	**469**	**212**
VE3FLE	"	173,106	384	177
VE3CBY	"	86,319	245	139
VE3GFY	**7**	**34,902**	**141**	**63**
VE3BBN	**3.8**	**33,642**	**148**	**63**
VE4RP	**A**	**41,230**	**156**	**95**
VE4ZP	**14**	**56,499**	**234**	**111**
VE6AGV	**A**	**69,700**	**266**	**100**
VE6SB	"	41,943	198	93
VE6MP	**14**	**59,055**	**293**	**93**
VE6MC	3.8	1,188	23	18
VE7IQ	**A**	**10,824**	**121**	**33**
VE8OO	**14**	**37,582**	**195**	**86**
KZ5BC	**A**	**697,632**	**1267**	**208**
KZ5NG	**"**	**615,020**	**1260**	**191**
		(Opr. KZ5BP)		

Costa Rica

TI2SW	**14**	**58,604**	**270**	**98**

Dominican Republic

HI8XAW	**A**	**251,370**	**755**	**147**
HI8LC	**14**	**110,433**	**360**	**131**

Grenada

VP2GGG	**A**	**836,565**	**1333**	**215**
		(Opr. W5QBM)		

Mexico

XE1LLS	**7**	**41,072**	**141**	**68**

San Andres Is.

HKØBKX	**A**	**277,200**	**722**	**150**

Saint Pierre Is.

FPØBG	**14**	**9,163**	**65**	**49**
		(Opr. VE1AIH)		

Africa

Angola

CQ6LF	**A**	**1,936,938**	**2065**	**318**
XX6SM	"	251,870	525	178
CQ6OR	**28**	**424,815**	**653**	**223**
CR6OZ	**21**	**661,680**	**933**	**240**
XX6CC	"	464,175	698	225

Kenya

5Z4OY/A	**A**	**958,353**	**1270**	**257**
		(Opr. OH2BCP)		

Liberia

EL4D	14	19,894	136	49

Morocco

CN8BO	**A**	**1,907,880**	**1933**	**312**

Mozambique

CR7DB	**A**	**24,090**	**121**	**73**

Rhodesia

ZE1BL	A	6,120	51	40

Sao Thome Is.

CR5AJ	**14**	**52,503**	**167**	**111**

Asia

Bhutan

A51PN	**A**	**39,449**	**217**	**103**

India

VU2DK	**14**	**296,097**	**530**	**229**

Iran

EP2NH	**A**	**67,465**	**281**	**131**

Israel

4X4QG	**28**	**41,736**	**152**	**94**
WA2KGY/4X				
	21	**135,675**	**410**	**135**

Japan

JA1OCA	**A**	**208,075**	**461**	**175**
JH1EIG	**A**	**135,470**	**334**	**155**
JR1FNZ	"	67,500	236	100
JA6CNL	"	63,308	216	133
JA2HUN	"	35,956	168	89
JA2INS	"	32,769	126	99
JA2MGE	"	18,796	113	74
JH1GTQ	"	11,277	73	63
JA1BUI	"	2,133	35	27
JA7HLO	"	1,595	34	29
JA7ARW	"	1,533	30	21
JH2IRN	"	884	28	26
JA2AIR	"	780	15	12
JA1EL	"	225	11	9
JA8IBU	"	154	9	7
JA1LDJ	"	84	6	6
JA3BBG	"	70	6	5
JR1INZ	**28**	**43,733**	**265**	**101**
JR1PZN	"	7,353	81	57
JH3GCN	"	5,192	73	44
JA1XZF	"	4,462	60	46
JA1RUJ	"	3,520	66	44
JA6BSM	**21**	**77,928**	**257**	**136**
JH2BIM	"	44,388	184	108
JH2MYN	"	37,125	180	99
JH2IRC	"	28,391	140	89
JA3ERG	"	24,920	161	89
JA3BUB	"	12,238	95	58
JA8WY	"	11,682	136	66
JA3CMD	"	10,472	86	56
JF1KXN	"	5,029	69	47
JH3FYW	"	4,033	67	37
JA6EFT	"	3,740	46	34
JR2BGE	"	2,436	37	28
JA3ELU	"	972	20	18
JA3YJQ	"	648	23	18
JA9AG	**14**	**235,119**	**504**	**181**
JA1PCY	"	45,594	180	102
JA7KTY	"	41,385	184	93
JA3IBU	"	37,184	170	83
JAØPZJ	"	15,678	107	67
JAØSC	"	14,006	117	47
JA8AIP	"	7,261	66	53
JAØAIE	"	6,825	67	39
JA1AAT	"	6,216	61	42
JA3VOV	"	4,480	51	40
JA5CEK/3	"	3,456	51	36
JA6YY	"	1,980	37	30
JA5COE	"	1,820	31	26

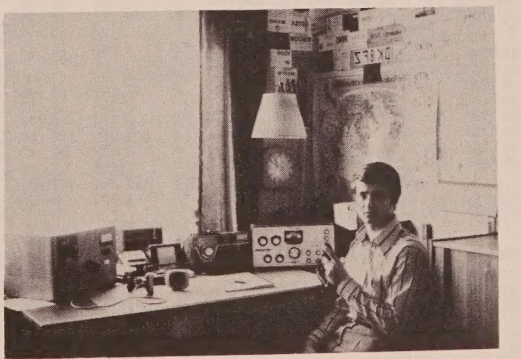

A young and eager contestant for a number of years, Egon, DK8FZ almost doubled his all-band single op score this year and took top honors for the Federal Republic of Germany. How about making it a million points in the next one?

This is Irene—the gal who for the past couple of years has managed to get the WPX winner certificate awards to you at the earliest possible date.

JH3BJN	"	512	16	16
JA7KM	"	114	8	6
JA2BAY	**7**	**82,626**	**211**	**94**
JA2BET	"	50,516	149	73
JA7HYS	"	1,470	19	15
JF1EEK	"	768	19	16
JA1SHY	"	640	13	10
JA3BCT	"	500	20	5
KA2PJ	**14**	**84,608**	**250**	**128**
KA7MS	"	16,320	105	68

Khmer Republic

XU1DX	**A**	**514,609**	**1533**	**227**
		(Opr. K7CBZ)		

Lebanon

OD5BA	**A**	**715,407**	**943**	**231**
OD5HJ	**14**	**8,154**	**116**	**54**

U.S.S.R.

Asiatic

UA9TS	**A**	**526,608**	**948**	**216**
UA9IF	**14**	**86,710**	**326**	**130**
UA9OS	"	18,113	158	59
UA9MT	"	12,597	70	57
UA9MQ	"	6,280	59	40
UA9UBH	**3.5**	**7,672**	**66**	**28**
4JØDI	**A**	**447,975**	**1300**	**165**
UAØCAH	"	55,380	731	60
UAØJBD	**28**	**5,304**	**119**	**34**
UAØAAL	**3.5**	**14,112**	**78**	**36**

Armenia

UG6JJ	**14**	**44,844**	**165**	**101**

Azerbaijan

UD6DHW	**14**	**59,360**	**205**	**106**
UD6DKM	"	7,245	59	45

Kazakh

UL7FM	**A**	**387,748**	**792**	**212**
UL7DAF	"	262,095	694	173
UL7GAZ	"	244,968	700	177
UL7LAW	"	96,280	225	116
UL7YP	"	1,944	27	24
UL7YR	"	588	15	14
UL7TA	**28**	**3,930**	**111**	**30**
UL7JG	**14**	**237,413**	**502**	**191**

Tadjik

UJ8JGJ	**14**	**509,787**	**840**	**237**
UJ8JJJ	**7**	**6,930**	**56**	**33**

Turkoman

UH8BO	**14**	**80,693**	**225**	**137**

Uzbek

RI8LAX	**28**	**1,560**	**51**	**24**
UI8LAG	**3.5**	**108,100**	**210**	**94**

Europe

Austria

DK5AD/OE2				
	A	**249,400**	**600**	**200**

Balearic Is.

EA6CK	**A**	**113,457**	**473**	**177**

Bulgaria

LZ2RF	**A**	**152,342**	**449**	**211**
LZ1MH	"	124,998	500	166
LZ2EE	"	12,730	86	67
LZ1QH	**21**	**17,280**	**127**	**54**
LZ2KSB	14	1,960	50	35
LZ2JF	**3.5**	**114,686**	**361**	**143**

Czechoslovakia

OK3YCE	**A**	**323,520**	**637**	**240**
OK3EA	"	190,347	462	201
OK1KZ	"	72,485	326	133
OK1AGN	"	71,336	254	148
OK1AHV	"	52,540	237	148
OK1TA	"	28,987	132	101
OK1KVK	"	26,772	150	92
OK2BEF	"	13,760	107	64
OK2BKI	"	13,580	120	70
OK2QX	"	13,056	107	64
OK2PEQ	"	7,020	72	60
OK1WT	"	6,400	69	50
OK2SMO	"	1,922	34	31
OK1ATE	**14**	**120,276**	**379**	**156**
OK1MPP	"	86,652	258	174
OK3LU	"	53,170	227	130
OK1AVU	"	45,320	204	103
OK1AJN	"	17,775	167	75
OK2BBJ	"	16,985	155	79
OK1DVK	"	4,560	48	48
OK2PBG	"	2,916	65	36
OK1MP	**7**	**27,492**	**141**	**87**
OK2KR	"	22,100	131	85
OK2BNK	"	450	17	15
OK2BIQ	**3.5**	**113,778**	**400**	**147**
OK1AHI	"	68,094	295	117
OK2BKH	"	51,450	234	105
OK1EP	"	21,450	152	75
OK1FBV	"	16,724	120	74
OK1AAE	"	9,912	83	59
OK3TBG	"	5,590	71	43
OK1UY	"	5,208	66	42
OK2PEL	"	2,772	45	33
OK1MJL	"	756	23	18
OK3ARP	"	392	14	14

Denmark

OZ6XR	**A**	**42,552**	**212**	**108**
OZ1XO	"	5,356	70	52
OZ4HW	"	4,773	82	37
OZ6PI	**14**	**101,680**	**385**	**164**
OZ8KU	**7**	**4,452**	**56**	**42**
OZ8XZ	"	1,856	38	29
OZ5EV	**3.5**	**122,008**	**400**	**151**
OZ9XM	"	1,000	25	20

England

G3HTA	**A**	**306,138**	**622**	**222**
G4AYA	"	87,291	369	159
G4CLA	"	66,220	324	140
G3YBH	"	60,047	215	149
G8VF	"	46,482	248	122
G2AJB	"	23,280	148	97
G3NRQ	"	1,239	44	21
G4AYL/A	**14**	**397,544**	**776**	**229**
G4CKL	"	54,806	262	134
G4ACQ	**7**	**55,454**	**217**	**119**
G3JUL	**3.5**	**33,578**	**171**	**103**

Finland

OH3YI	**A**	**537,285**	**924**	**301**
OH1IJ	"	313,470	682	243
OH1LW	"	268,424	674	232
OH5YF	"	8,832	70	69
OH2BMG	"	4,136	64	47
OH7TO	"	3,913	66	43
OH7NW	"	2,400	53	32
OH5RZ	"	2,072	42	37
OH2BO	"	1,846	34	26
OH8OR	"	147	7	7
OH3WN	**21**	**1,700**	**26**	**25**
OH3WW	**21**	**1,700**	**26**	**25**
OH1UR	"	60	6	5
OH1VR	**14**	**299,172**	**835**	**233**
OH1IG	**"**	**38,220**	**344**	**105**
OH6MM	"	36,685	287	115
OH4SM	"	15,552	162	81
OH7SC	"	7,006	77	62
OH2EQ	"	6,580	84	47
OH7PB	"	6,096	70	48
OH1PG	"	264	16	12
OH7TV	"	105	7	7
OH2KI	**7**	**259,440**	**456**	**188**
OH6ZH	"	51,304	208	106
OH1XX	**3.5**	**170,624**	**518**	**172**
OH2DN	"	16,660	120	70

France

F9MD	**A**	**293,480**	**535**	**232**
F6AXO	"	58,362	247	137
F6BJA	"	37,210	153	122
F3IJ	"	18,252	119	78
F2QQ	**14**	**449,320**	**825**	**235**

Germany (East)

DM2DUK	**A**	**762,128**	**1200**	**304**
DM6TAH	"	60,420	300	106
DM4YEL	"	49,184	229	116
DM2AJH	"	38,266	180	106
DM3XLB	"	14,280	109	68
DM2BPB	"	9,676	101	59
DM2DGO	**14**	**13,952**	**94**	**64**
DM4GM	"	121	11	11
DM3BB	"	120	8	6
DM3CF	"	60	6	6
DM2BOO	7	60	6	5
DM5IG	**3.5**	**9,130**	**83**	**55**
DM3WB	"	242	11	11

Germany West

DK8FZ	**A**	**822,617**	**1113**	**337**
DK5GX	"	24,196	138	92
DL6OX	"	13,600	97	68
DL7AN	"	12,084	106	76
DJ7HL	"	1,632	40	34
DL1YA	"	230	10	10
DL1ED	**28**	**2,673**	**36**	**27**
DL2JO	**21**	**3,780**	**53**	**35**
DK1FW	**14**	**510,402**	**808**	**257**
DJØEW	"	193,888	545	146
DK7ZJ	"	10,980	142	61
DJØUJ	**7**	**96,944**	**330**	**146**
DL8PC	**3.5**	**208,278**	**605**	**189**
DK4OO	"	104,976	342	162
DK4EX	"	9,372	84	71
DK5OL	"	6,834	76	51
DA1CT	**14**	**87,032**	**292**	**172**
DA1YH	**3.5**	**5,428**	**60**	**46**

Greece

SVØWGG	**AA**	**461,805**	**1262**	**255**

Hungary

HA5KFN	**A**	**29,205**	**167**	**99**
HA5CI	"	20,210	126	94
HA7LF	**14**	**258,930**	**663**	**210**
HA5DG	"	7,676	76	76
HA7SQ	"	4,928	73	44
HA7PQ	**7**	**16,330**	**119**	**71**
HA4KXC	**3.5**	**143,040**	**517**	**160**
HA4XX	"	30,616	179	89

Iceland

TF3SB	**A**	**11,534**	**129**	**73**

Italy

I3PRK	**A**	**665,577**	**933**	**301**
I1ANP	"	183,141	611	189
I6VDB	"	85,284	368	138
I4CSP	"	75,692	279	149
I2AT	**28**	**5,640**	**53**	**40**
I4BNR	**21**	**90,640**	**328**	**103**
I8KBT	"	67,056	246	132
I5FCK	**14**	**339,416**	**719**	**203**
I3GNX	"	66,062	302	134
I5PLS	"	62,906	309	142
I5XRR	"	44,195	180	127
I4BMJ	**7**	**180,958**	**497**	**173**
I3BBZ	"	81,388	292	126
I3MAU	**3.5**	**215,940**	**569**	**177**

Luxembourg

LX1RK	**A**	**14,378**	**116**	**79**

Netherlands

PAØHBO	**A**	**605,730**	**919**	**305**
PAØVB	"	2,278	44	34
PAØYN	"	2,133	52	27
PAØLVK	**14**	**5,040**	**58**	**45**
PAØTO	"	912	34	24

Norway

LA5QK	**A**	**76,437**	**308**	**149**
LAØAR	"	54,929	315	133
LA5JS	"	42,408	229	114
LA6HL	"	4,082	53	26
LA3WQ	21	128	10	8
LA3BG	**14**	**89,125**	**362**	**155**
LA3UQ	"	27,072	203	96
LA5KO	"	6,324	64	51
LH2A	"	162	9	9

Poland

SP9AI	**A**	**158,260**	**477**	**193**
SP5BB	"	113,150	385	155
SP5XM	"	60,382	262	133
SP9EHP	"	40,837	220	97
SP9ZD	"	33,158	158	118
SP5KGT	"	32,476	161	92
SP2BBD	"	25,414	148	97
SP2GNB	"	16,704	140	87
SP7ETG	"	15,366	115	78
SP9YP	"	12,654	109	74
SP5ZBL	"	9,828	91	63
SP3GEM	"	7,227	113	33
SP6AGK	"	4,687	62	43
SP6AEG	"	2,079	34	27
SP9PT	"	1,890	31	30
SP9EHW	"	1,890	30	27
SP3DOI	**21**	**4,407**	**42**	**39**
SP8AWL	"	1,575	28	21
SP4CLX	**14**	**73,414**	**356**	**142**
SP7ASZ	"	25,753	157	91
SP9ABU	"	24,990	176	98
SP9ADU	"	14,700	115	75
SP5AMX	"	2,465	50	29
SP8AOV	"	1,000	28	20
SP3CTC	"	260	10	10
SP6ECA	"	160	14	10
SP6TQ	**7**	**47,586**	**215**	**103**
SP5DZI	**3.5**	**98,914**	**339**	**137**
SP3BLG	"	75,504	307	121
SP2CMB	"	27,468	185	84
SP6AGD	"	24,734	151	83
SP6AFO	"	16,614	133	71
SP9PEW	"	11,748	104	66
SP9ETK	"	1,716	34	26
SP9DH	"	1,056	28	24
SP9PBZ	"	4	2	2

Portugal

CA1MZ	**A**	**4,354**	**45**	**39**

Romania

YO7DL	**A**	**87,745**	**418**	**161**
YO6KAF	"	64,170	251	138
		(Opr. YO6AWR)		
YO3AC	"	22,780	106	85
YO7AWN	"	19,832	134	74
YO3JW	**3.5**	**105,080**	**356**	**142**
YO7AQE	"	480	21	12

Scotland

GM5BCV	**A**	**191,967**	**634**	**183**

Spain

EA5HM	**A**	**68,391**	**350**	**149**
EA2JD	**14**	**88,616**	**389**	**152**

Sweden

SM5BNX	**A**	**31,860**	**209**	**108**
SM5RE	"	19,264	152	86
SM7AIO	"	18,382	101	101
SM7TV	"	13,260	116	68
SMØCGO	"	11,682	95	66
SM5ARL	"	7,452	85	69
SK1AQ	"	4,128	48	43
		(Opr. SMICXE)		
SM2EQT	"	3,081	50	39
SM7ECX/M				
	"	1,248	26	24
SM4AZD	"	1,170	28	26
SM1CNS	**14**	**455,445**	**822**	**261**
SM7DMN	"	31,200	240	104
SMØATN	"	9,864	73	72
SMØBPZ	"	5,355	61	51
SM7CRW				
	3.5	**36,248**	**201**	**92**

Switzerland

HB9AWM	**A**	**200,070**	**495**	**190**
HB9UD	"	3,135	40	33

Vatican

HV3SJ	**A**	**60,478**	**325**	**139**

OH2MM, Vilho, along with Marty, OH2BH; Pierre, OD5HC; and Aris, SV1GA stirred up a beehive of activity from Cyprus as SV1GA/5B4. Vilho's photo was taken at Joe's, OD5BA on a stopover from Cyprus. Bet there was a lot of WPX contest rag-chewing?

Wales

GW4AES	14	62,424	364	136
GW4BLE	7	114,608	312	152

Yugoslavia

YU1OCV	**A**	**144,375**	**457**	**165**
YU2RAM	"	42,368	196	128
YU2RKC	**28**	**12,320**	**79**	**55**
YU2ROZ	**21**	**72,220**	**239**	**115**
YU2CDS	**14**	**845,568**	**1340**	**288**
YU3TKT	"	10,010	126	65
YU5XDX	"	4,200	74	50
YU2OB	**7**	**72,570**	**266**	**123**
YU1AJE	"	1,782	40	27
YU4EBL	**3.5**	**244,818**	**590**	**201**
		(Opr. YU4VFF)		
YU1DVW	"	49,220	276	107
YU1AGU	"	14,490	114	63

U.S.S.R.

European

UW6MT	**A**	**368,461**	**778**	**229**
UV3DN	"	155,340	513	180
UA3ST	"	137,175	471	177
UA4SR	"	56,140	236	140
UV3TQ	"	26,132	166	94
UA3DAO	"	23,352	150	84
UA3XP	"	23,220	147	86
UA3WZ	"	21,204	151	76
UA6LWI	"	20,111	151	91
UA6HAC	"	3,706	47	34
UA1WAA	"	2,030	41	35
UA6JAD	**28**	**714**	**17**	**14**
UA6HYL	"	216	9	8
UW6CV	**21**	**66,712**	**316**	**124**
UA4CZ	"	65,201	288	113
UA6BV	"	27,621	155	99
UW3RR	"	5,916	98	51
UW6CW	"	1,272	31	24
UW4NP	**14**	**266,500**	**660**	**205**
UZ3TC	"	160,362	611	177
UA3GM	"	92,253	336	161
UW3CX	"	71,910	290	141
UW6LC	"	70,328	331	149
UA1MU	"	25,654	142	101
UA1GBE	"	4,800	74	50
UA6HY	"	3,220	57	46
UA3IE	"	450	23	18
UA3QAQ	**3.5**	**48,672**	**238**	**104**
UA3ERD	"	46,848	218	96
UA3EAT	"	15,080	112	58
UA4UAZ	"	13,356	112	53
UA4YAW	"	11,792	90	44
UA1ALN	"	9,633	114	57
UA6HBU	"	3,392	54	32

Kaliningrad

UA2EC	**A**	**155,040**	**407**	**170**

Latvia

UQ2DV	**A**	**98,100**	**348**	**150**
UQ2MU	"	65,024	345	128
UQ2CR	"	52,210	246	115
UQ2AS	**3.5**	**37,856**	**197**	**91**
UQ2GBU	"	37,410	207	87
UQ2GCN	"	21,754	141	73

Lithuania

UP2OU	**A**	**373,302**	**817**	**223**
UP2BAS	**21**	**968**	**24**	**22**
UP2FA	**3.5**	**20,700**	**143**	**69**

Moldavia

UO5BZ	**A**	**33,712**	**180**	**112**

Ukraine

UT5RT	**A**	**596,882**	**1172**	**286**
UB5LU	"	32,996	217	113
UY5ZT	"	1,302	32	31
UB5VAZ	**28**	**1,679**	**28**	**23**
RB5VAC	"	216	9	8
RB5ABX	"	75	6	5
UY5OO	**21**	**65,835**	**271**	**99**
UB5AAF	"	6,204	59	47
UB5CI	**14**	**219,960**	**667**	**234**
UB5OD	"	38,985	237	113
UB5XY	**7**	**2,880**	**50**	**30**
UB5WF	**3.5**	**88,844**	**317**	**133**
UB5EDU	"	77,736	271	123
UB5QCQ	"	55,414	236	103
UB5VAL	"	42,780	217	93
UB5VAN	"	29,928	170	86
UB5QBG	"	10,560	101	44

White Russia

UC2WP	**A**	**38,232**	**288**	**108**
UC2BF	"	1,825	28	25
UK2AAB	**7**	**11,600**	**106**	**58**

Oceania

Australia

VK1AOP	**A**	**111,006**	**335**	**126**
VK2OW	**A**	**8,358**	**71**	**42**
VK4VU	**A**	**274,247**	**642**	**139**
VK4FH	"	182,932	536	116
VK4AK	"	21,375	110	75
VK5NO	**A**	**351,770**	**838**	**145**
VK5MF	"	74,980	283	92
VK2XT	**21**	**31,977**	**323**	**33**
VK3SM	**21**	**23,779**	**193**	**43**
VK4PJ	"	714	19	14
VK2APK	**14**	**229,824**	**479**	**171**
VK6LK	**14**	**99,975**	**281**	**129**

Guam

KG6JAR	**14**	**32,214**	**200**	**59**

Hawaii

KH6RS	**A**	**1,235,208**	**2466**	**156**
		(Opr. K2SIL)		
KH6IJ	**21**	**270,060**	**1291**	**70**
KH6GMP	**14**	**477,246**	**1072**	**154**

Marshall Is.

KX6LM	**A**	**126,290**	**600**	**73**

New Zealand

ZL1BKX	**A**	**183,352**	**345**	**164**
ZL1AMM	"	68,355	225	105
ZL1AAS	**14**	**90,060**	**272**	**114**
ZL4BO	**7**	**58,824**	**152**	**76**

Samoa (American)

KS6DH	**A**	**1,046,446**	**1758**	**193**

Western Samoa

5W1AN	**14**	**65,764**	**277**	**82**

South America

Argentina

LU5HFI	**A**	**1,780,600**	**1885**	**307**
		(Opr. F5QQ)		
LU8AJG	**A**	**1,072,500**	**1369**	**275**
LU2DEK	**21**	**20,097**	**114**	**63**

Bolivia

CP3BY/1	**A**	**38,364**	**162**	**92**

Brazil

PS4KL	**A**	**513,280**	**663**	**256**
PS7ARM	"	352,429	601	199
PS8JO	"	297,666	521	207
PS6AM	"	280,596	501	201
PS2JB	"	242,332	463	188
PY2AQG	"	29,646	128	81
PY3CKL	"	26,800	143	67
PT1AA	"	24,300	117	81
		(Opr. PT2GBZ)		
PY1CHP	"	5,375	46	43
PS4BTK	"	512	16	16
PY1BOL	**28**	**11,564**	**74**	**59**
PY1BDU	**21**	**148,035**	**364**	**139**
PY1DBE	**14**	**154,305**	**397**	**135**
PS1CCK	"	825	31	25
PY2ELZ	**7**	**19,910**	**70**	**55**
PY3CGP	"	4,482	38	27
PS2FIZ	3.5	140	9	7
PY2FOT	"	112	7	7

Chile

CE6EZ	**28**	**266,668**	**575**	**163**

Colombia

WA6TLJ/HK6				
	A	**47,286**	**153**	**74**

Ecuador

HC1WW	**A**	**7,434**	**62**	**42**

Peru

OAN4ANR	**7**	**4,480**	**40**	**32**

Uruguay

CX1JM	**A**	**1,216,212**	**1534**	**258**
CX7BQ	"	124,950	313	147

Venezuela

YV6AW	**A**	**1,673,660**	**1744**	**268**
YV1TO	"	533,168	814	188
YV3CL	"	141,984	300	153
YV4YC	**28**	**73,260**	**296**	**90**
YV4OW/7	**7**	**132,210**	**201**	**117**
YV4TI	**3.5**	**176,064**	**316**	**96**

MULTI-OPERATOR
Single Transmitter

United States

WA6GLD		**137,250**	**340**	**122**
WØEEE		**109,585**	**341**	**155**
K3IVO		**94,710**	**247**	**154**
WB8IAY		**60,588**	**212**	**132**
WM5BIL		**39,550**	**604**	**89**
W6VPZ		28,137	149	83
WAØCGV		1,914	38	33

North America

VP5CW		**2,000,985**	**2444**	**285**
VA6WDX		**133,945**	**576**	**89**

Africa

CR4BC		**1,262,533**	**1332**	**281**

Asia

4X4NJ		**2,845,905**	**2506**	**339**
9M2CX		**449,838**	**1628**	**201**
JH1YDT		**166,980**	**390**	**165**
JA6YTU		151,060	457	166
JA1YFG		59,267	216	97

Europe

YU1BCD		**1,613,920**	**1889**	**352**
I6FLD		**1,377,720**	**1694**	**356**
G4DAA		**1,063,535**	**1563**	**305**
SP5PWK		**952,380**	**1217**	**333**
HG8U		**767,529**	**1392**	**279**
DJØEK		**681,884**	**1050**	**294**
HA9KOB		679,481	1291	277
G3RCV		580,350	1006	265
DK4OV		576,160	919	277
SK6BA		**518,940**	**832**	**270**
SP6PZB		502,000	990	251
EI1AA		**480,636**	**1065**	**234**
YU2CBM		429,408	901	252
OH3AM		**421,751**	**1003**	**253**
DKØSD		394,389	758	243
ZB2WPX		**383,280**	**1019**	**240**
I3BKT		370,403	720	223
HA5AIR		338,549	701	233
LZ2KPD		**311,831**	**906**	**221**
SP9KRT		280,704	887	192
HA5KKB		262,353	652	217
HA2KRL		258,543	650	207
G4BUE		228,437	539	209
OH8RC		209,979	489	189
HA7KLG		201,798	487	202
OH5WJ		165,615	545	183
LA1K		**159,216**	**649**	**186**
HA5KKW		147,028	480	178
OK1KPU		**141,432**	**460**	**166**
SP3KGJ		136,950	446	165
HA7KLF		134,640	416	180
HA5KAS		124,041	394	173
HA7KLC		116,154	426	162
OH4RH		112,391	401	167
PI1ARS		**96,924**	**332**	**164**
HA2KMR		84,960	329	144
HA5KMB		83,475	301	159
OK3KGI		78,120	360	126
SP9ZAF		74,746	313	133
OK3KTR		66,640	277	136
OK1KUR		55,876	263	122
YU2CDO		35,350	268	101
SK4EN		33,000	180	100
SP6KDA		30,749	173	97
OK1KUO		18,396	126	77
OK2KWL		17,608	121	71
SP5KOH		11,904	100	62
SP3ZAH		10,521	87	63
OK3KAP		2,592	43	36

Oceania

ZL2HV		**54,560**	**228**	**88**

South America

PJ9JR		**4,543,618**	**3631**	**347**
PY2CAB		**3,647,904**	**3101**	**416**
PS7BDX		2,519,700	2335	370
PS7NS		883,500	1168	250

U.S.S.R.
Club Stations

Asia

UK9ABA		**2,530,098**	**1980**	**367**
UK6APA		**2,094.666**	**1908**	**371**
UK9CAE		908.295	1120	285
UKØAAB		**590.180**	**1246**	**230**
UK9OAZ		428.358	1060	217
UK9FFR		327.128	549	206
UK6FAF		**276.344**	**489**	**169**
UK6GAA		**207.701**	**405**	**169**
UK9OBI		108.772	323	142
UKØCAX		100.470	779	85
UKØSAL		80.400	358	120
UK9OAW		56.462	241	109
UK7PAL		**17,006**	**138**	**58**

Europe

UK2GKW		**1,391.712**	**1848**	**336**
UK6LEZ		**1,194.165**	**1557**	**315**
UK5IAZ		**1,037.162**	**1694**	**322**
UK3AAC		790.560	1383	305
UK3SAB		611.000	1277	235
UK3DBG		424.964	942	262
UK3QAA		418.396	954	257
UK2RAE		**375.375**	**1000**	**231**
UK5ATFK		335.160	797	190
UK4WAB		335.025	744	225
UK2PAF		**315.545**	**735**	**223**
UK4WAC		313.124	754	212
UK3ARO		298.584	692	234
UK5MAG		285.824	750	203
UK5EAQ		253,344	708	208

[Continued on page 70]

Announcing The QRPp Transmitter Design Contest

BY ADRIAN WEISS,* K8EEG

THERE can be no doubt about it—operating with very low power offers something that can't be found in other facets of amateur radio. The thousands of converts to the QRPp "alternate life style" attest to this fact. However, both newcomer and veteran alike face a common difficulty when the time comes for upgrading their stations.

Most of us start out with a simple, single-band, crystal controlled transmitter used in conjunction with the sophisticated all-band station receiver and antenna system. Once one gets the hang of QRPp operation and the attendant skills, such a transmitter becomes a real obstacle. To make the best use of our knowledge of propagation, a band switching capability is essential, as is the flexibility of v.f.o. control. Unfortunately, the only commercially produced QRPp rig providing this degree of flexibility is the superb Argonaut. But many QRPp'ers don't see any sense in laying out the cash for an extra receiver just to get a transmitter. Home-brewers are no better off. With one exception[1] which is outdated, I know of no published design for an all-band, v.f.o. controlled QRPp transmitter. What the QRPp movement needs most desperately at this stage, then, is a flexible transmitter that can serve adequately with the all-band receiver and antenna system.

CQ's policy of encouraging QRPp continues in its present sponsorship of this "QRPp Transmitter Design Contest." The contest is intended to produce the badly needed design for an all-band, v.f.o. QRPp transmitter.

By offering instant fame and recognition (publication of the winning design—and perhaps the runner-ups), riches (payment for published articles), tangible rewards (a TenTec 215 receiver for the winner, a Curtis Electro Devices 8043-1 "Keyer on a chip" for each of two runners up, and satisfaction (the knowledge that hundreds and perhaps thousands will be duplicating your design), we at *CQ* hope that we can motivate many of you to try your hand in the contest. At the very worst, you will end up with a unique QRPp rig that you can use with pride and satisfaction.

I want to emphasize the point that this is not intended to be a contest for graduate engineers —although they can compete. What we are looking for is a good, all-around design that works—we are *not* looking for an original work of genius, although that certainly would be nice. So, design from scratch, or pick a circuit from here, another from there, put it all together, and if it works well, it may win! The following comments are intended as suggested specifications for the winning design.

V.F.O.

The v.f.o. should permit coverage of at least 100 kHz of the 80, 40, 20, and 15 meter bands; 10 meters may be included if desired. Any v.f.o. system is acceptable—separate tanks for each band, a frequency multiplication scheme, heterodyne scheme, or whatever—so long as a reasonable degree of electrical, thermal and mechanical stability is inherent in the design. In addition, the v.f.o. should be adequately isolated from later r.f. stages to avoid possible r.f. feedback and excessive "pulling" during key-down periods.

R.F. Stages

The r.f. section should feature coverage of the four bands mentioned above, and be capable of at least four watts r.f. output power. Either discrete or broadband tuning of the r.f. stages is acceptable, so long as harmonics are down 30 dB from fundamental. Interstage and output circuits should be designed so that spurious tuned spots will not occur within the range of the components specified.

The transmitter should be operable with B+ supplies of 12-13.6 volts. We strongly recommend that a modern "ballasted emitter" or mismatch protected" r.f. device be used in the final amplifier. Types such as the 2N5590, 2N5995 are recommended, and devices specifically intended for broadband service would be wise choices if the designer chooses to take the broadband route. Keying of the B+ except through a properly designed solid state switch should be avoided. Reliability is an important factor. If it takes an extra r.f. stage to guarantee the required output power, use the extra stage rather than depending upon very critical peaking of a single stage.

*213 Forest Ave., Vermillion, SD 57069

[1]Weiss, A., K8EEG, "A Multiband FET V.F.O. QRPp Transmitter," *ham radio,* (July, 1972), p. 39. The TenTec r.f. module is no longer in production.

General

One key criteria to be applied in judging submitted designs is the ease of duplication. This doesn't mean that the transmitter must be simple. Even a complex circuit can be duplicated by a beginner if the designer makes the rationale of the circuit clear, uses readily available parts, and provides a clear p.c. board design if that form of construction is chosen. Miniaturization is *not* one of our criteria.

Submitted designs may be as complex or as simple as desired. The winner will be chosen entirely on the basis of the design and performance of the c.w. r.f. section of the entry. For example, an entry may be a complete s.s.b./c.w. transmitter with s.w.r./wattmeter, keyer, sidetone, etc.—we'll judge only the c.w. r.f. performance of the design.

While attractive cabinetry can obviously be a source of pride to a designer, we will not take housing into consideration in selecting the winner.

If it is necessary to use exotic parts, a source for such parts should be indicated.

Entries

Deadline for entries is June 1, 1975. The initial entry should include the circuit itself, parts specified on the schematic, or on a separate sheet with a listing of sources for any unusual parts. The above must be accompanied by a supporting explanation of the rationale of the circuit, preferably with a block diagram, with commentary on any unusual features of the circuit. These notes are only intended for the assistance of the judges. A snapshot will be sufficient evidence of the existence of the unit, for preliminary entries.

The finalists will be selected from these initial entries. We reserve the right to request and test actual working models of the finalist designs in order to choose the winner.

Ten finalists will be selected from the initial entries by a screening panel composed of *CQ* staff. Selection of the winner and two runners up will be made by a panel consisting of: Wilfred M. Scherer, W2AEF, *CQ* Technical Consultant; Dan Tomcik, K4HYF, V.P. TenTec, and Jack Birchfield, K4DCD, Executive V.P. TenTec; and Bob Fernau, W8NDG of Heathkit, design engineer of the HW-7. Decisions of the panel will be reported in the QRPp column in *CQ*.

So gang, there it is! We're confident that many of you will take up the gauntlet in the service of QRPp'ers everywhere and that your efforts will result in a reliable, flexible QRPp transmitter that will be as important to the QRPp movement in years to come as the old Heath AT-1 was to a generation of Novices in the 'fifties. So, dig into the books and come up with a winner! We'll all be winners in this one! ■

CQ to Change Abbreviation Style

In response to reader requests and the pressure of the technical writing field, *CQ* will adopt a number of minor changes in its basic style of technical abbreviation beginning with the January 1975 issue.

The following units, abbreviations and prefixes will be used in *CQ*. In many cases the abbreviations are identical to those used all along, but a few significant changes have been made to eliminate ambiguities in prefixes. While not all the unit abbreviations coincide with the recommendations of the International Electrotechnical Commission, the American Standards Association or the IEEE, we feel that our readers will find them to be unambiguous and unconfusing. The abbreviations represent the most convenient and stylistically sound approach for our publications.

Units		Prefixes	
Ampere	- a	M = mega	$= 10^6$
Decibel	- db	k = kilo	$= 10^3$
Farad	- f	m = milli	$= 10^{-3}$
Henry	- h	μ = micro	$= 10^{-6}$
Hertz	- Hz	n = nano*	$= 10^{-9}$
Meter	- m	p = pico	$= 10^{-12}$
Ohm	- ohm or Ω		
Volt	- v		
Watt	- w		

Using these basic elements, the most common units will become: MHz = megahertz, Mw = megawatt, kw = kilowatt, kv = kilovolt, kHz = kilohertz, ma =milliampere, mh = millihenry, mm = millimeter, mv = millivolt, mw = milliwatt, μa = microampere, μf = microfarad, μh = microhenry, μv = microvolt, μw = microwatt, pf = picofarad (.001 mf).

* Not normally used except in relation to seconds.

COP's COLUMN

BY COPTHORNE MACDONALD,* WØORX

On-The-Air "Futures Hamfest"

What do you have planned for the weekend of March 8-9? How about taking part in the very first on-the-air "Futures Hamfest" which will be held that weekend? Suggested originally by Ron Wilbur, K6ZEZ, the idea of sharing a weekend of fun and enlightenment on the ham bands has excited a number of us. There will be some talks on the ham gear of the future, of course, and certificates for those stations who work to help make the weekend happen. But there will also be sessions on Economics, Alternative Energy Sources, Women's Issues, Education, the Environment Decentralized Living, Ham Radio's Future, and other concerns we share. One of the basic ideas is to open up our shacks and share this ham radio weekend with others. Some sessions will use s.s.b.-only, and some RTTY, but many of the sessions will utilize SSTV to permit speakers to illustrate their talks. This will be a real opportunity for SSTVers to declare a weekend "open house" to the local ham club members, and maybe even to the whole town as well. It will be perfect chance to show off what SSTV can d and to demonstrate a serious use of ham radi (Don't forget to invite the local newspaper an TV photographers too.) There will be som *very* knowledgeable speakers, with question an answer sessions in most cases so that you ar I can ask those questions which have been bu ging us. Look for more details in this colum and elsewhere as the time draws nearer, b right now volunteers are needed to work c preparations. Stations that get out well a needed for Moderator duty, and to host gue speakers (either in the shack or via phon patch). Slow-scanners willing to convert spea er's slides and photos into SSTV tapes a needed too. Finally, if you know one or mo "doing" people working toward a better futu in some field or other, see if he or she wo volunteer as a speaker. The heroic Chairm and coordinator of this effort is Randy Brin WA7BKR. If you'd like to lend a hand, co tact him on 3898 kHz Sunday, Tuesday, a Thursday nights at 8 P.M. PST, or Sunday afte noons on 14253 at Noon PST. (If ham rad fails you, his address is RFD 2, Box 301- Port Orchard, Washington 98366).

*P.O. Box 483, Rochester, MN 55901.

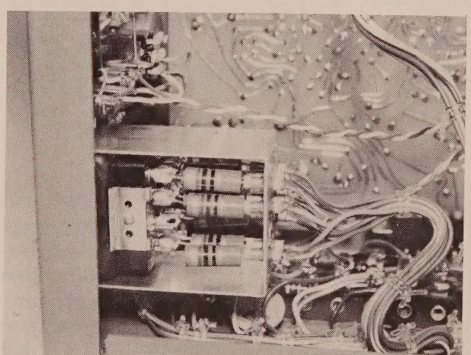

Fig. 1—10 μh inductors and .001 mf feedthrough capacitors in this Robot camera provide RFI filtering of each wire in the camera cable.

R.F. Pickup On Cables

In last month's column we looked at w "r.f. in the shack" causes problems, and so of the ways to minimize the difficulties grounding units together and filtering the a line. R.f. can also enter a unit by way of interconnecting cables. Speaker wires, aud patch cables, camera cables, mike cables, f or TV antenna lead-in wires, and even hea phones can be culprits. Using shielded ca having an overall braided (not spiral-wrappe shield is a good idea, and is often sufficient the units at each end of the cable are w shielded. With unshielded cables (and ev shielded cables if high r.f. currents flow in t braid) the r.f. picked up must be filtered o Sometimes bypassing each lead to the chas will suffice. Sometimes an *R-C* or *L-C* filter each lead is required. Table I gives the re tance of some common *L*'s and *C*'s at varic frequencies. The basic idea is to put some

Absolute Value of Reactance in Ohms				
Part Value	3 kHz	20 kHz	3.5 mHz	30 m
.01 mf	5.3K	800	4.5	<1
.001 mf	53K	8K	45	5.3
100 pf	530K	80K	450	53
10 μh	<1	1.3	220	1.9
100 μh	1.9	13	2.2K	*

*Depends upon distributed winding capacita

Table I—Reactance of some common RFI fi components at several frequencies of interest

ductive reactance or resistance in series with the lead entering the unit before bypassing it to chassis ground with a capacitor. Figure 1 shows the scheme that Robot uses in their SSTV camera. In series with each lead entering the camera is a 10 μh inductor followed by a .001 mf feedthrough capacitor to ground. In high impedance circuits, series resistors can be used instead of inductors. Table I plus common sense can help to pick suitable values in different situations. For example, in filtering a power supply lead, select an inductor with a d.c. resistance low enough to give an acceptably low voltage drop, yet presenting a reasonably high reactance at r.f. frequencies. Good values of bypass capacitance for power leads are .01 and .02 mf. When filtering audio or slow-scan video leads you must consider both the frequency response you want to preserve, and the impedance level. At the maximum audio frequency desired, the series impedance should be low, and the capacitive reactance high, compared to the parallel combination of source and load resistance. Thus, for a 600 ohm audio line carrying speech or SSTV, a .01 or .02 mf bypass would be fine. The "auxiliary" input of a Hi-Fi amplifier may involve an impedance to ground of 10K or so. Therefore, if the full 20 kHz frequency response is desired, the shunt *C* should not exceed 330 or 470 pf. A 330 pf capacitor is not an ideal bypass in the 3 to 30 mHz range. To optimize the filtering you might want to select a series choke that is self-resonant near the highest frequency at which your rig causes RFI. A second possibility in a case like this would be to use a multi-stage filter as shown in fig. 2(D), or settle for some reduction of audio frequency response.

A caution regarding inductors: they don't act like inductors above their self-resonant frequencies, so going to high values of inductance can actually *reduce* attenuation at high frequencies. A choke which is effective throughout the v.h.f. and u.h.f. range can be made by slipping two or three ferrite beads on a piece of bare wire. Type 43-101 ferrite beads are suitable, and are available from Amidon Associates, 12033 Otsego Street, North Hollywood, Calif. 91607.

Coax antenna lead-ins do not generally bring much stray r.f. into a ham receiver because the shield is grounded to the chassis, and the input stage is generally very close to the input connector. TV and f.m. receivers are usually designed for a balanced 300 ohm input and do have problems. The best approach is installing a good high pass filter such as the R. L. Drake TV-300HP-R.

Last Ditch Efforts

Sometimes, even if the a.c. line has been filtered as described in last month's column, and interconnecting leads coming into the unit

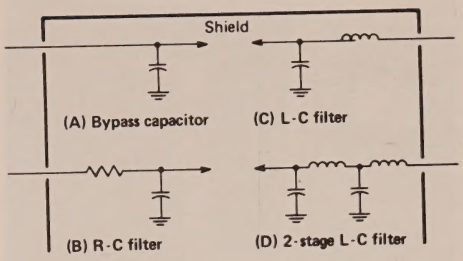

Fig. 2—Four common ways of filtering interconnecting cable leads for RFI.

have been filtered as described above, the interference will still persist. If this happens in a well-shielded unit it generally means that the filtering of the a.c. line and other leads going into the unit is still not adequate. If the unit is a tape recorder, stereo amp, or TV set in a wood or plastic cabinet, the remaining interference is probably related to the lack of shielding.

There are two ways to attack the problem. The first is to shield the cabinet by carefully gluing aluminum foil to the inside cabinet walls. Do not cover ventilation holes with foil, and if the unit generates a lot of heat, spray the foil with black paint so there is no shiny surface to reflect the heat back toward the chassis. Make sure that the chassis makes good electrical contact with bare foil in several places.

Sometimes shielding is not practical at all. In other situations it is not possible to shield a unit completely. In these cases one can resort to r.f. filtering right at the individual transistors. The preamp stages are the place to start. One filtering scheme is shown in fig. 3. Here the transistor base lead is cut, and a 4.7K ¼ watt resistor is soldered in series with the base lead. Then a .001 mf capacitor with short leads is soldered directly from base to emitter. Using this approach it is not necessary to cut any PC board conductors, and the filtering is done right at the transistor.

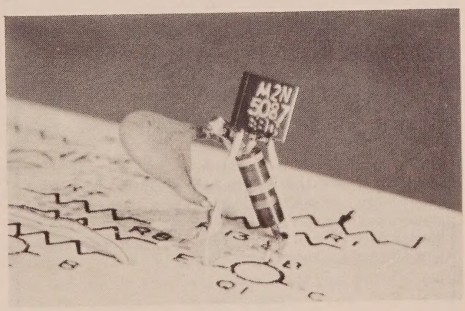

Fig. 3—When it is impossible to keep r.f. out of an audio amplifier, a simple *R-C* filter right at the transistor will often eliminate RFI.

Fig. 4—RFI in this cassette recorder was eliminated by keeping the interconnecting cable short, and powering the recorder with internal batteries.

Eliminating RFI is generally a step-by-step process. We've looked at several of these steps:

1. Chassis-to-chassis bonding of nearby units.
2. Filtering the a.c. input.
3. Filtering interconnecting cables.
4. Shielding.
5. R.f. filtering at individual transistor stages.

The order given is the order in which I would usually attack the problem, but there is nothing sacred about it. Sometimes going right to step 5 would be simplest. It's important to remember that the RFI may be coming into the unit via several routes simultaneously. Often you will notice a reduction in interference only when several corrective measures are taken *at the same time.* For example, if half of the interference comes via the a.c. line, and half via an interconnecting cable, eliminating either source will give only a slight reduction in the observed interference level. All r.f. highways into the unit must be blocked at the same time. As you work down the list, leave each modification installed even if it doesn't seem to help much. When the problem is finally solved you can go back and try removing the modifications one-by-one if you wish.

Some RFI Case Histories

A bad case of RFI in a reel-to-reel tape recorder housed in a wooden case was cured by filtering the a.c. line, filtering the input and output leads right at the connectors, and filtering the preamps right at the transistors. Shielding was not attempted.

The small cassette recorder shown in fig. 4 had interference problems when the a.c. adapter was plugged in and when long interconnecting cables were used. By using internal batteries and a very short cable to the rig, the interference was eliminated as long as the operator does not touch the recorder. (Yes, our bodies can be antennas too!)

A slow-scan monitor in a steel cabinet was cured of RFI by r.f. filtering the a.c. line, and by filtering the SSTV audio inputs right at the connectors.

RFI problems in a well-shielded slow-scan camera were solved simply by bypassing each lead of the camera cable to the camera case with .01 mf disc ceramics.

An f.m. receiver/stereo amp in a wooden case responded to a.c. line filtering, and bypassing each speaker lead to ground with .02 mf disc ceramics.

The toughest case was a solid-state color TV set where the RFI affected the video stages as well as the audio. The final solution required a good high pass filter, a.c. line filtering, and covering the inside of the plastic cabinet with aluminum foil.

'Til next time. Vy 73, Cop, WØORX

WANT TO BUY OLD LIONEL TRAINS

My classified ads in CQ have been very productive in helping me acquire several new additions to my electric train collection.

There are still many Lionel models that I want quite badly, and I'll pay good cash or swap radios for just about any Lionel train in good condition.

The models I'm looking for particularly are as follows:

Twin Diesels -- Canadian Pacific No. 2373
Rio Grande No. 2379
B & O No. 2358
GG-1's (Pennsy Electrics) Nos. 2330, 2332, 2340, 2352, 2360.
Steam Locomotives Nos. 700E, 773, 763, 5344, 726.

Am also interested in any Lionel Standard Gauge equipment, as well as 0 gauge box cars, freights, passengers, etc. Your old trains in the attic or garage may be worth good money. Don't be bashful. Drop me a line and find out.

Dick Cowan
CQ Magazine
14 Vanderventer Ave.
Port Washington, NY 11050

WANT TO BUY -- USED HAM GEAR

We pay cash for used gear: FM, SSB, AM, etc. Working or as is -- makes no difference. Call or write today! Al, W2SRW or Mel, WA2NET.

RAMCO ELECTRONICS
365 Canal Street, New York, NY 10013
Phone: **(212)966-6056**

NOVICE SHACK

BY HERBERT S. BRIER,* W9EGQ

If anything is better calculated to give a new c.w. operator an irresistible urge to retire his "straight" key in favor of an electronic keyer than observing an expert operate such a keyer, we cannot think of what it is. The operator of a straight key has to pound out each code character, dot by dot, and dash by dash. In contrast, the operator of the electronic keyer nonchalantly wiggles his hand a few millimeters from side to side a few times to send the same message. And it is almost as effortless as it looks for the expert. But Novices, do not throw away your straight keys yet. There are a couple of catches to using an electronic keyer, especially if your code is a little shaky. Before going into them, however, let us describe in elementary fashion how an electronic keyer works.

The keyer contains a "clock" that generates square waves at the highest speed at which it is desired to send dots. The clock feeds a keying transistor or relay through the dot contact of the control paddle. The clock also feeds a "frequency divider" which makes dashes three times as long as the dots but keeps the spacing between both the same. The divider feeds the keying circuit through the dash contact on the control paddle. A speed control varies the speed of the dots, dashes, and spaces all in the same ratio.

Pushing the paddle to the right generates a continuous stream of dots; pushing it to the left generates a stream of dashes. Thus, all the operator has to do to send perfect code is to swing the paddle, left and right, to mix the dots and dashes in the proper proportions. The timing must be precise, however. The importance of timing in sending dot characters is obvious, but it is equally important in characters containing both dots and dashes, because of the limited time in a character to reverse the position of the paddle. The problem is lessened by adjusting the lever for minimum spacing between contacts. Twin paddles, one for the dots and the other for the dashes, may also be used to halve the time required to change from sending dots to sending dashes and vice versa.

Twin-paddle electronic keyers equipped with self-completing circuits and built-in "memories" *(which insure that once a dot or dash is started, it will be completed and a unit space will elapse before another dot or dash can be sent)* will send alternate dot and dashes or dashes and dots (depending on which paddle is pressed first) as long as both paddles are squeezed. By alternately pressing and releasing them in the correct sequence, all the code characters can be sent with a minimum of wasted motion. We emphasize again that precise timing is the first requirement in mastering any electronic keyer, however it is used. A built-in keying monitor or other means of listening to your own sending is only slightly less important.

The delicate touch required to control an electronic keyer can be achieved with practice. In the meantime, however, your ability to send good code on a straight key deteriorates at least temporarily.

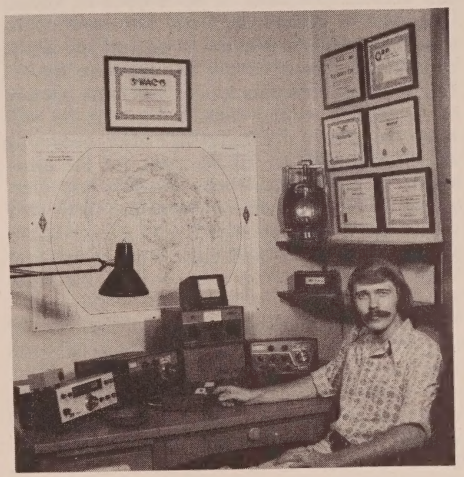

Peter Sils, WN8PJR, 15103 Clifton Blvd., #2, Lakewood, Ohio 44107, wins a 1-year subscription for CQ for submitting this picture. Peter uses a Drake T-4XC transmitter cranked down to 75 watts and a Drake R-4B receiver, and a Ten-Tec Argonaut transceiver usually operated at two watts input. His antennas are a Mosley TA-33JR, 10, 15, 20-meter rotary beam, 40 feet high and separate 80 and 40-meter inverted V's. The Worked-All-Continents (WAC) certificate and 40 countries worked speak for themselves. The 2-watter worked Hawaii and England on 15 meters in September. If you would like to try for the free 1-year subscription we award to the sender of photograph we choose as the best picture of the month, send a sharp photograph (preferably black and white) of you at the controls of your station and some details about your amateur career to: CQ Novice Shack Photo Contest, c/o Herbert S. Brier, W9-EGQ, 385 Johnson St., Gary, Ind. 46402.

*385 Johnson St., Gary, Ind. 46402.

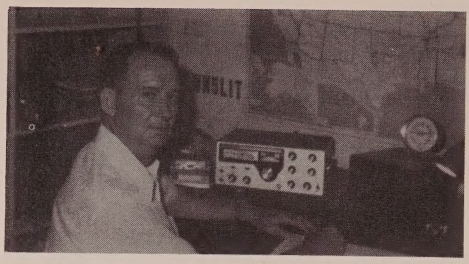

Ken Anderson, WN5LIT, had an unusual "breaker" in a recent contact. Details in "News And Views."

What happens when the operator goes back to a straight key after a session with an electronic keyer is that the multi-dot and multi-dash combinations come out as long dashes as he waits for the key to do the work, instead of pumping it manually. Of course, an operator can become proficient on both types of keying machines by diligent practice. The question is, though, whether a Novice is wise to spend the time that he could devote to preparing for his General-class examination to learn to operate an electronic keyer, considering that he will have the rest of his radio life after becoming a General to devote to the task. On the other hand, we know that many Novices use electronic keyers, and some of them use them very well, indeed. Incidentally, the FCC will allow you to carry your own battery-powered keyer with you into the FCC office to take the sending test on.

Many electronic keyers are advertised in *CQ* and other magazines in kit and finished form from approximately $10 to well over $100. The lowest priced ones are not always the cheapest, by the way. Some of them are sold without the paddle mechanism, which can add $20.00 or more to the total cost. A very acceptable twin-paddle mechanism can be constructed, however, by mounting two standard straight keys, back-to-back, on their sides on a rectangle of metal heavy enough to prevent the device from walking across the operating table in use.

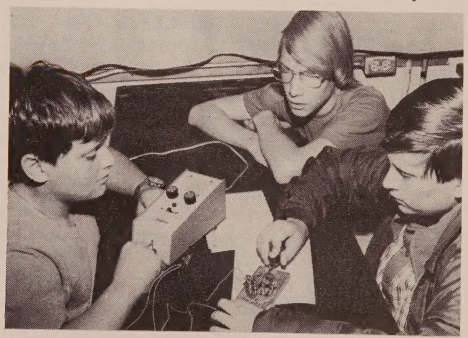

Members of the First Ave. School Amateur Radio Club, Arcadia, Calif., 91006, comparing a Heathkit electronic keyer with a straight key. The knobs on the keyer are its speed control and the volume control for the built-in keying monitor.

Sources of Electronic Keyers

Curtis Electro Devices, Inc., Box 4090, Mountain View, Ca. 94040. $140-300.
Data Engineering, Inc., 5554 Park Royal Rd., Springfield, Va. 22151.
Hal Communications Corp., Box 365, Urbana, Il. 61801. $75. less paddle.
Heathkit, Benton Harbor, Mich. Kit, $40.
Matric, Box 185, Franklin, Pa. 16323. Keyer, $35. Paddle, $10.
MF-J Enterprises, P.O. Box 494, Mississippi State, Mississippi. $35, Four penlight cells extra.
Ten-Tec, Inc., Sevierville, Tn. 37862. Three models with paddles, $38-100.
Vibroplex Co., Inc., 833 Broadway, N.Y., N.Y. 10003. Paddles $28 and $33.

Operating Events of Novice Interest

10-Meter Contest, 1200 GMT Dec. 14, to 2359 GMT, Dec. 15. Everybody works everybody in this event. U.S. and Canadian amateurs send signal reports and names of states and provinces. DX send reports and serial number. Scoring: Two points for complete exchanges. Novices worked four points. Total score is sum of contact points multiplied by sum of states, VE call areas, ITU regions (Non land based stations), and different countries woked. Suggested frequencies for Novice, 28.1-28.15 mHz. Scores go to ARRL, Newington, Cn. 06111.

Straight-Key Night, 0100-0600 GMT, Jan. 1, 1975. No contest. Just amateurs working each other using straight keys and exchanging signal reports preceded by "SKN." Send list of station worked and your vote for best "fist" heard to ARRL, Newington. Cn. 06111. Most Novice activity will probably be in the lower 10 kHz of the 3.7 and 7.1-mHz Novice bands.

News And Views

After the local amateur radio club showed a decided lack of interest in holding classes for prospective amateurs, **Ted Herrman, KZ5VV,** Panama Canal Zone, did the job himself. Between February and July, he turned out 13 new Novices, KZ5CZN, JAN, LBN, MON, ASN, DXN, QXN, RBN, XQN, XYN, RSN, BJN, and XGN. A couple of them have already earned their General tickets but still work the Novice bands. As **Jake Meyer, KZ5JA,** P.O. Box 415, Balboa Heights, C.Z., said, "It will be better

[*Continued on page 74*]

MATH'S NOTES

BY IRWIN MATH,* WA2NDM

OVER the past several months we have received several letters from readers of this column asking for a "practical review" in the application of light emitting diodes. As a result, we will devote this months column to the "care and feeding" of these devices.

The light emitting diode (or LED as it is commonly called) is electrically, nothing more than a specially fabricated diode and therefore exhibits all diode characteristics. Where it differs from a conventional diode however, is when it is forward biased. At this time, it emits light which, with todays units can be either red, green, yellow or invisible (to the eye) infra-red depending on the semiconductor materials used in the fabrication of the particular device. The general design procedure for the use of any of the four varieties is the same however.

Fig. 1 is a schematic of the basic LED circuit. Because of the fact that the LED is a forward biased diode, a resistor is necessary to limit current flow to a safe value.

Brightness is proportional to the current flowing through the LED but, like a conventional diode, too much current can damage the device. A little simple arithmetic is all that is necessary however to determine the value of the current limiting resistor. All of the necessary parameters for the formula in fig. 1 (maximum current and diode forward voltage drop) can be obtained from the data sheet for the particular LED to be used. Typical figures incidentaly are 1.5 volts for the diode forward drop and 20-30 milliamperes for the maximum current. When used as a pilot light indicator therefore, it is easy to see that the total power required for a LED and resistor (Vsupply × Idiode) is much less than that required for a conventional pilot lamp. As an example of this

*5 Melville Lane, Great Neck, N.Y. 10023.

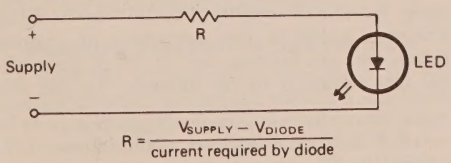

Fig. 1—A typical LED hookup.

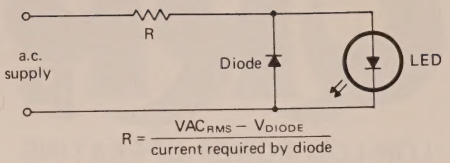

Fig. 2—Using an LED with a.c.

consider the case of the popular #47 lamp which requires 150 milliamperes at 6.3 volts, almost 1 watt. An LED used for this purpose, operating from the same 6.3 volts, would only require 20 milliamperes—a power of .126 watts or roughly 10 times less. Also, since the LED is a semiconductor device, its ruggedness and life will be many times that of the pilot lamp. In fact the only drawback is the amount of light output from the device which is less, but still completely adequate for almost all indicator requirements.

One can also use a LED with a.c. in the same circuit as fig. 1. Here, the positive half cycle of the a.c. will act as the forward biasing voltage while the negative half cycle will simply reverse bias the diode and cut it off. The resulting 60 Hz flicker is not noticeable by the eye and the final result seems the same. Care must be taken in this application however, to assure that the reverse voltage breakdown level, which is quite low in many LED's is not exceeded. In case this is a problem, it is only necessary to add a low cost diode in parallel with the LED as shown in fig. 2. This diode will conduct in the reverse direction of the LED thereby limiting its reverse voltage. Note that the RMS value of the a.c. is used for the resistor calculation in this application.

The low current and polarity sensitive features of light emitting diodes offers many interesting and unique possibilities for the experimenter. Fig. 3 is an example of a typical circuit made possible by these characteristics. Here the LED is used in several ways. The first, exactly as shown, is as a simple polarity indicator. Depending on the input polarity the diode that is forward biased will light and the other will remain off. Putting a.c. into this circuit will cause both diodes to light, therefore it can be used as an a.c./d.c. detector. If the circuit is connected to the output of a communications receiver however, it will serve as a zero-beat detector when adjusting the internal

[*Continued on page 72*]

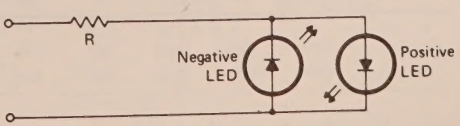

Fig. 3—The LED circuit described in the text.

QRPp

LOW-LOW POWER OPERATING

BY ADRIAN WEISS,* K8EEG

Efficiency In The Antenna System

As anyone who has had to copy a weak QRPp signal in the QRM will verify, a one dB difference in signal level often can make the difference between copy and no-copy. I know that for a fact also. During the August QRP Contest, I worked a string of about 17 stations on 80 meter c.w. with some pretty bad QRN problems. All contacts were eventually completed, but oftentimes taking about 15 minutes to get across the simple exchange information. I often wished that the other guys had been able to squeeze just another dB output during those couple of really tough hours of copy. That would have made all the difference in the world! So, let's review the ways and means of making certain that you aren't wasting that dB of signal that could make the difference in a rough QSO.

Mechanical Losses and Their Cure

Before we even start to consider the esoteric theory on s.w.r. and its effect upon antenna system losses, we have to clear up the simple sources of signal loss. The first of these, and a very common source, is the poor solder connection. When an antenna is buffeted by winds and rain and snow, plus all the pollutants floating around in the atmosphere these days, the solder connecting the feedline to the antenna itself is bound to corrode and introduce some real resistance between feedline and antenna.

*213 Forest Ave., Vermillion SD 57069.

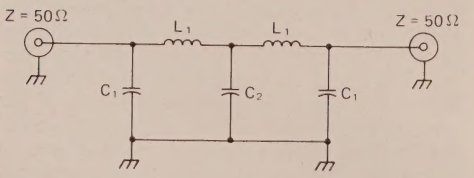

F (mHz)	3.5	7	14	21	28
L_1 (μh)	2	1	.55	.35	.17
C_1 (pf)	820	470	220	180	110
C_2 (pf)	1500	1000	470	390	220

Fig. 1—A half-wave filter.

This connection should be inspected periodically for corrosion, but it is likely to be there. The best way to avoid the problem is not to rely merely on solder. Best to use a screw, nut, and washers combo to pressure clamp the feedline to the antenna, then solder the wires together, and finally, weatherproof them with a healthy wrapping of good plastic tape or a glob of plastic insulating material. Similarly, every connection that is made along the feedline-antenna path should be checked—solder connections resoldered periodically, coax receptacles and plugs steel-wooled clean, the ground connections between coax receptcales and chassis cleaned and tightened. Likewise, the ground wire-cold water pipe connection should be cleaned. If a transmatch or antenna tuner is used, check it thoroughly.

Feedline Loss

An old, frazzled piece of coax used as a feedline can burn up more r.f. energy than you would expect. Coax should be replaced if any noticeable signs of deterioration can be spotted. After several cold winters in the open, the coax dialectric can deteriorate also. When checking the coax, don't forget the solder connections to the coax plug—these can wear loose in time. One easy test that should turn up any serious defect in the r.f. handling capability of the coax is to first measure the r.f. voltage across a dummy load, and then connect the dummy load to the far end of the coax without touching the transmitter tuning; any noticeable difference in power delivered to the load is an indication that the coax has deteriorated.[1]

Choice of coax for feedline is important. Depending on construction, size of inner conductor, and spacing, a feedline will exhibit real resistance which dissipates r.f. energy fed through it. To give you the picture, Table I lists the attenuation per hundred feet of four types of feedline—RG-58U and RG-8U coax, and 300ohm open line with seven strands of #21, and solid #16 copperweld lines. Deviation from 100 ft. lengths is linear.

Loss in dB per 100 ft. at Frequency

Type	3.5 mHz	7 mHz	14 mHz	21 mHz	28 mHz
RG-58U	0.69	1.1	1.5	1.95	2.35
RG-8U	0.31	0.45	0.65	0.82	0.95
7/21 open	0.2	0.28	0.42	0.52	0.62
#16 solid	0.12	0.17	0.25	0.32	0.39

A glance at this table tells the tale. If you are using brand-new quality RG-58U at 7 mHz, and need a 100 ft. run, regardless of antenna match you are burning up 1.1 db of your signal just getting it to the antenna. To put this

[1] See also the technique suggested in *The A.R.R.L. Antenna Book* (Newington, CT, 1968), p. 85.

into realistic terms, if you are putting 1 watt into the feedline, only about 750 milliwatts gets to the antenna. For RG-8U, it comes out about 910 miliwatts. For the #16, about 970 miliwatts. You're in the wrong ball park if you are using that miniature RG-174U. If you are, I'll let you look it up for yourself.

SWR and Line Loss

A common myth that has been floating around since the introduction of coax is that *reflected power* is somehow *wasted power*. That is, if the s.w.r. meter reads 10 watts forward and three watts reflected, then the antenna is only radiating the difference, or seven watts. Not so. The actual loss caused by s.w.r. varies with the line attenuation referred to above and is quite negligible when a low loss line is used. To cite some examples, let me refer to the *A.R.R.L. Antenna Book*, Fig. 3-18, p. 77. If the feedline attenuation when perfectly matched to a load of its characteristic impedance is 1 db, an s.w.r. of 2:1 will add 0.21 db additional loss; 3:1 will add 0.5 db additional loss; 5:1 will add 1.2 db additional loss. To return to our RG-58U at 7 mHz again, the total loss for 100 ft. with a 3:1 s.w.r. will be 1.1 db line loss plus 0.53 db additional loss, or 1.63 db. However, if we use RG-8U in the same case, it comes out to line loss of 0.45 db plus 0.25 db additional s.w.r. induced loss, or 0.8 db total loss. So, operating with 100 ft. of RG-8U at a 3:1 s.w.r. is clearly better than operating with perfectly matched RG-58U. Of course, with the # 16 solid open line, the figure is 0.17 db line loss, plus 0.2 db s.w.r. induced, or 0.37 db total. Take your choice. To reiterate, s.w.r. of itself causes very negligible signal loss.

SWR and Harmonics

Inaccurate s.w.r. readings are often caused by the presence of harmonic energy in the output signal. If your antenna is cut to frequency either with an r.f. bridge or according to handbook formulas (which come out very close in practice), and you have a 2.5:1 s.w.r. or higher there is a good chance that the reflected reading is actually caused by harmonics. There is no sense in putting a signal into the feedline that is 60% fundamental and 40% harmonic. Strive for signal purity. Insertion of a simple half-wave filter in the feedline will usually drop harmonics about 25 dB or better. See fig. 1 for details. Of course, the filters should be shielded so that no harmonic leakage occurs.

Matching Transmitter and Feedline

Unless the characteristic impedance of the feedline exactly matches the radiation resistance of the antenna, there will always be an s.w.r. of above 1:1. It is not absolutely necessary to have a perfect match between feedline and antenna, and such is well-nigh impossible to

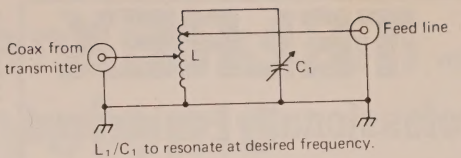

Fig. 2—A simple transmatch.

achieve, because the radiation resistance of the antenna is affected by many factors, such as height above ground, proximity to surrounding objects etc. Furthermore, the antenna will eventually radiate all power fed into the feedline (minus line losses) regardless of s.w.r. The reflected waves eventually recombine with the forward waves to be radiated. The problem point to be dealt with, then, is the match between transmitter and feedline, because power can be wasted there. If your antenna has an s.w.r. of somewhere around 3:1 or worse, and your rig just won't load up into the antenna, you need some sort of matching device, such as a transmatch or antenna tuner. A simple transmatch which will match your transmitter output to a coax or open feedline is shown in fig. 2. The input and output taps are varied until a good match is obtained. You can take a chance and adjust the match for lowest s.w.r., read between the transmitter and transmatch, but that can be deceptive at times. It is best to insert a #49 or #47 bulb in series with the output lead and tune for highest indication of r.f. current. Or, a field-strength meter can be used to monitor radiation from the antenna during tune-up. By juggling the taps, you should be able to get a very low s.w.r. and high output indication at the same time.

When using open wire feedline, it is best to

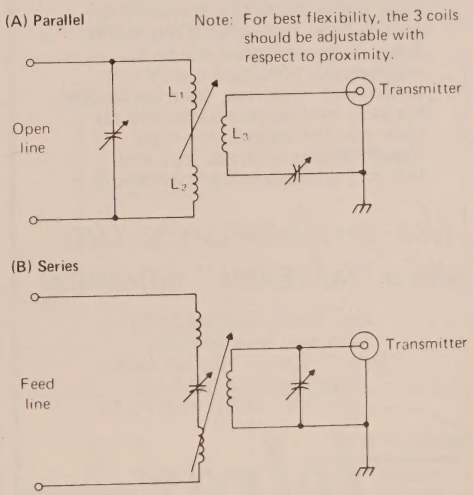

Fig. 3—A lumped constant transmatch for open line feeder.

with **TELREX**

Professionally Engineered

"BEAMED-POWER"

"BALANCED-PATTERN"

"PERFECT-MATCH"

Antenna Systems

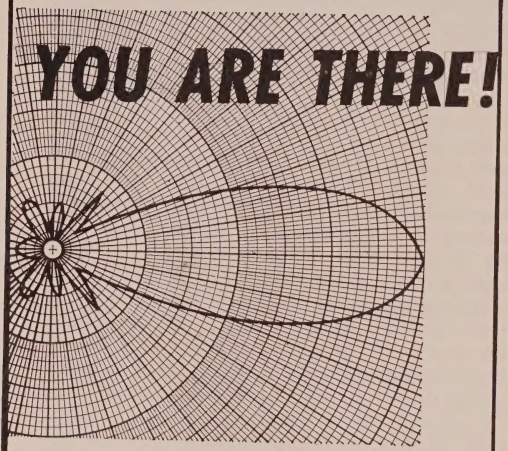

The design, craftsmanship and technical excellence of Telrex — Communication Antennas.

have made them the standard of comparison throughout the world! Every Telrex antenna model is engineered, precision machined, tuned and matched, then calibrated for easy and correct assembly at your site for repetition of our specifications without 'cut and try' and endless experimentation.

"the-performance-line"

with a "MATERIAL" difference!

Also: Rotator-Selsyn-Indicator Systems, Inverted-V-Kits, "Baluns," Towers, "Bertha" Masts, 12-Conductor Control Cable and Co-ax. SEND FOR PL-73

COMMUNICATION SYSTEMS SINCE 1921 **telrex** Laboratories

ASBURY PARK, NEW JERSEY 07712, U.S.A.

connect the feedline across a lumped capacitance/inductance. In many of the transmatches published in the literature which used tapped coils and dual-capacitors, it is possible to achieve a perfect 1:1 s.w.r. with no r.f. power going to the antenna—the transmatch itself is dissipating all the energy! So, again, small bulbs in the feedline is the only way of getting a positive indication that a low s.w.r. is an actual indication of power going to the antenna. See fig. 3 for parallel and series tuned lumped constant circuits. Best results are obtained if the link coil is adjustable with respect to its positioning in the main coil.

Ultimately, all of the above procedures will result in improvements if anything is wrong with your system. The one true and trustworthy way of determining whether your system is working, or is being improved by some adjustment, is the laborious route of positioning a field-strength meter a wavelength or so from the antenna in question, and monitor the signal strength after each adjustment is made without retuning the rig. If the F/S reading goes up, the juice is getting into the ionosphere where it should be!

Milliwatt Research Group

We are still looking for QRPp operators interested in an organized experimentation with very low power levels on the order of 200 milliwatts and below. Tests will run until the end of the good season in late spring or so. This will be basically an individual effort with published results at the end. If interested, drop me a card.

WB9MBH is interested in doing some serious scientific experimentation with 10 milliwatts and under. He is looking for individuals with the capability of sophisticated weak signal reception techniques. If you fit, and want to join in the effort, drop me a card.

Don't forget the DL/AG QRPp DX Contest coming up in January. See elsewhere for announcement and details.

Transatlantic QRPp DX Tests

We are in the process of setting up transatlantic QRPp DX tests for several weekends in February and March. The choice of times and frequencies is still to be determined. What we need is a group of QRPp'rs on both sides of the Atlantic who will show up at the selected times and attempt to establish contact across the pond. Similar to W1BB's 160 DX tests. Foreign hams should write to Gus Taylor, G8PG, 37 Pickerall Rd., Greasby, Upton, Wirral, Cheshire, England. Others drop me a card.

That's it for this month. It's time again to start collecting QRPp WAS and DXCC standings. Drop me a card with your standings pronto.

73, Ade, K8EEG/Ø

Loss In Transmission Line Systems

BY WILLIAM J. LaHIFF,* W2IVT

It was so good back in the old days. A transmitter was usually a simple oscillator-amplifier type (fig. 1) with the antenna tuning circuit coupled to the tank coil. It was merely necessary to connect the open wire feeders to L_1, C_1 and tune for maximum antenna current. We knew nothing about s.w.r., the 1934 ARRL *Handbook* mentions only a "standing wave" once and states that variations of voltage along the non-resonant line are not good. The transmitter was complete. Only a single wire antenna or an antenna with open wire feeders was required to put a signal on the air. Also, the choice of antenna and feed line was simple, one of three: a straight wire (tapped on the tank coil), a single wire fed dipole (Windom), or an open wire line feeding a dipole at the end (Zepp) or the center, known as current feed.

The overall efficiency was excellent. The curbstone engineering was that from the plate of the vacuum tube an approximate loss of 20 percent (no decibels, either) would occur in the tank coil, the coupling coil and the open wire feeder. This combination would match almost any antenna system and external matching devices, with the attendant losses were not required. A transmitter rated at 100 watts output would deliver full power to the antenna at any frequency.

*3489 Fort Independence St., Bronx, NY 10463

Birth of a Problem

Somewhere along the line things became complicated, maybe sometime following War 2. The radio manufacturing companies required a peacetime market and some elected to sell amateur radio transmitters. Perhaps a non-ham radio engineer who had designed fixed frequency transmitters during the war designed out the pre-war wide range output circuit and designed in a circuit suitable only for coaxial cable. He did not know much about antennas and his company had 4650 Type N, 50 ohm coaxial connectors in stock. As a result the 50 ohm transmitter output was born.

The Antenna Problem

As shown in the chart (fig. 2) only a very low (physically) center fed dipole has a feed point resistance of 50 ohms and the majority of antennas supported at reasonable heights above ground show a resistance of

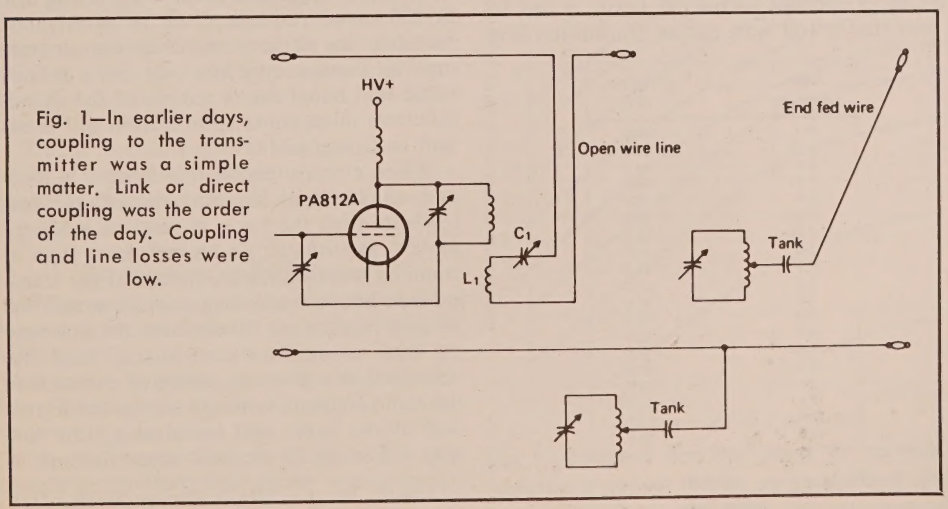

Fig. 1—In earlier days, coupling to the transmitter was a simple matter. Link or direct coupling was the order of the day. Coupling and line losses were low.

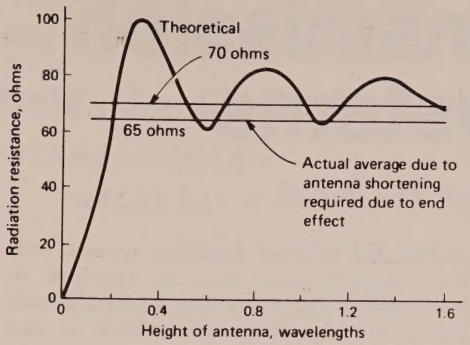

Fig. 2—Radiation resistance variation of a dipole antenna as a function of height above ground.

65 to 70 ohms. It is too bad those 4650 surplus connectors were 50 ohms. Seventy five ohm connectors would have been a better choice.

The Transmission Line Problem

Only the 75 meter man can be completely happy with the modern manufactured amateur transmitter. The antenna may be low enough so the radiation resistance does provide a good match to the 50 ohm coaxial cable. In fact, some do adjust the height of the antenna for the lowest s.w.r. reading. The frequency of the transmitter is never changed and some are compared with the pre-war crystal from the old a.m. rig.

With these conditions the simple coaxial line transmission system with the usual ferrite balun will operate with fair efficiency with a loss of 1.3 decibels. From the chart of fig. 3 decibels versus efficiency, it can be seen that a 100 watt output transmitter will

Loss (decibels)	vs	Efficiency (%)
0		100.0
0.25		94.5
0.5		89.0
0.75		84.0
0.1		79.5
1.25		75.0
1.75		67.0
2.0		63.0
2.5		56.0
3.0		50.0
3.5		44.0
4.0		40.0
4.5		35.5
5.0		31.5
6.0		25.0
7.0		19.5
8.0		16.0
9.0		12.7
10.0		10.0

Fig. 3—Efficiency vs. decibel loss on a transmission line.

deliver about 73 watts to the antenna terminals. This assumes very low s.w.r., 100 feet of RG-8/U cable (0.3 decibels loss) and a good ferrite balun (1.0 decibels loss) with the transmission line running away from the antenna at a right angle for a reasonable length.

At this point it would be reasonable to remove the balun from the system. The balun does cause the greater part of the system loss and if it is eliminated the power at the antenna terminals will be 92 watts. As a second reason for removing the balun, Carl Drummeller, W5JJ (*ham radio,* May '73) has proven by experiment that the only real advantage of the balun is the maintenance of a balance of voltages on either side of the dipole. Considering the location of the average amateur antenna, where the surrounding objects have a major effect on the dipole balance and the field pattern, it appears that the balun offers no advantage to the ham.

Thus far we have considered the coaxial line and balun as a non-resonant transmission line system. If it is desired to operate at a frequency removed by only a few percent from the resonant frequency, a standing wave will occur on the transmission line and the system must then be considered as a resonant system. As a result the balun will then operate under conditions for which it was never intended and very high s.w.r. will occur with increased losses. From tests made on several baluns offered for sale to amateurs the loss in a balun operating into an s.w.r. of 2 is quite high and the loss operating into a 200 ohm resistive load is prohibitive. Numbers are not expressed because accurate measurements cannot be made, but a definite value was noted far in excess of the manufacturers numberless specification of "insertion loss, negligible."

When a transmission line system is lossy and all are lossy to some degree, the loss tends to mask the s.w.r. as read on a Micromatch, Monimatch or power meter type of standing wave indicator. In fact, if the transmission line is made long enough so the loss is considerable, say 20 decibels, the line may be used as an excellent dummy load. As described in a previous article by the author[1] the radio frequency energy sent to the source end of the cable will travel along the line with a loss of 20 decibels when the end of

[1] LaHiff, W. J., "High Power VHF/UHF Dummy Loads," *CQ*, July '65, p. 35.

the cable is reached. At this point total reflection will occur and the power will flow to the source for a total of 40 decibels with the result that low or unity s.w.r will be indicated.

Figure 4 illustrates s.w.r. correction required when a loss is present on the transmission line. As an example, when the transmission line has a specified loss of 1.3 decibels and the s.w.r. measured with a standing wave indicator is 2.5 the actual s.w.r. proves to be 3.8.

To arrive at the overall transmission line loss this s.w.r. figure of 3.8 together with the original loss figure of 1.3 decibels may be applied to another chart (fig. 5) to determine the additional line loss caused by standing waves. The additional loss is one decibel making an overall line loss of 2.3 decibels so only 58 watts is fed to the antenna terminals. We can make a further excursion in frequency to where the s.w.r. is 3 for a system loss of 3.6 decibels. Congratulations, you are now eligible for membership in the QRPp club. If you are not ready for this, remove the balun. It does not belong in a resonant line system.

Without the balun and the associated loss a large change in the line loss situation is evident. The drop in line loss from 1.3 to 0.3 decibels makes operation at high s.w.r. levels without exceptionally high losses a possibility. If an s.w.r. of 2.5 is measured and referred to fig. 4 the actual s.w.r. is only 2.7. Inserting this figure, together with the 0.3 decibel original loss to fig. 5 shows an increase of only 0.15 decibels due to s.w.r. The total attenuation is then 0.45 decibels with 90 watts to the antenna. Even a measured s.w.r. of 4 will indicate only an 4.6 s.w.r. with an increase of less than 0.4 decibels for a total of 0.7 decibels loss with 85 watts to the antenna.

This is the transmission line problem. The pre-war transmitter with the wide impedance range output circuit would match these conditions with ease.

Compensatory Techniques

Unfortunately, only a few transmitters of the current manufactured types will operate satisfactorily into an s.w.r. greater than 2. This makes it necessary to install a Matchbox, Transmatch or other matching device to provide a match to high s.w.r. loads. Unfortunate, because like all other devices the matching circuitry has losses which again

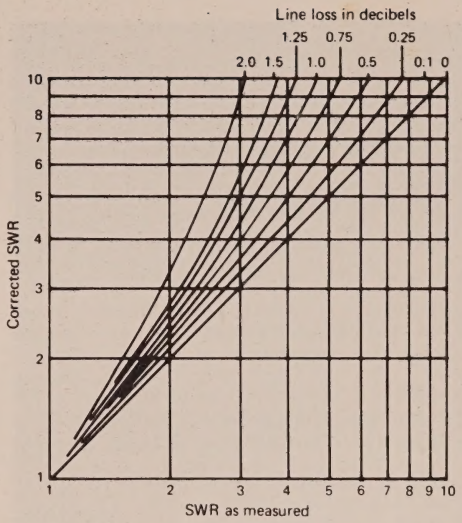

Fig. 4—Correlation curves for attenuation on transmission line.

are approximately one decibel.

It does look at first glance that we are right back where we started, but this is not so. The matching device is located at the sending end of the cable and when properly tuned it provides a match to the cable so all of the reflected wave coming down the cable is returned. The function is the same for all frequencies and the loss of the transmatch is constant over the whole of the 80 meter

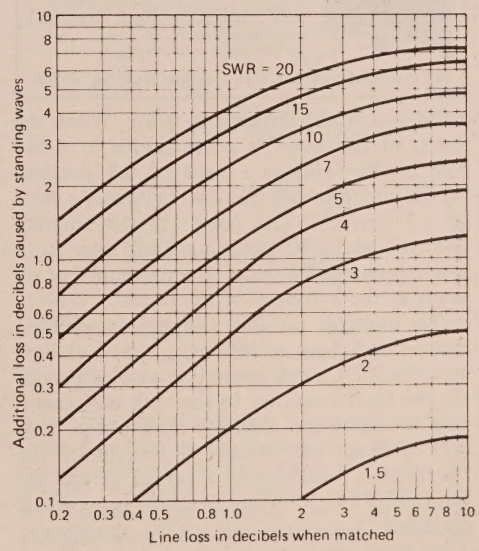

Fig. 5—Additional line loss caused by standing waves.

RINGO RANGER

4.5 db Gain (re ½ wave dipole)
6 db Gain (re ¼ wave whip)

THIS IS AN EXTENDED MODEL OF THE WORLD'S BEST VHF FM ANTENNA

ARX-2	146-148	MHz	**$26.50**
ARX-450	435-450	MHz	**$26.50**
ARX-220	220-225	MHz	**$26.50**

Conversion Kit to make your AR-2 into a Ranger
ARX-2K — **$10.95**

IN STOCK AT YOUR LOCAL DISTRIBUTOR

cushcraft CORPORATION
621 HAYWARD ST., MANCHESTER, N.H. 03103

SST T-1 RANDOM WIRE ANTENNA TUNER

All band operation (80-10 meters) with most any random length wire. 200 watt power cap ability. Ideal for portable or home operation. A must for Field Day. Size: 2 x 4¼ x 2-3/8. Built-in neon tune-up indicator. Guaranteed for 90 days. Compact - easy to use. . . . only 24.95 postpaid. (Add Sales Tax in Calif.)

SST ELECTRONICS, P.O. BOX 1, LAWNDALE, CA. 90260

band and is not affected by s.w.r. When the s.w.r. of the cable is a maximum of 4 the loss in the cable is a total of 0.7 decibels which added to the transmatch loss is a total of 1.7 decibels. The power to the antenna over the whole 80 meter band will vary from a maximum of 73 watts to a minimum of 69 watts at the extremes of the band.

To improve on this situation something radical will have to be done. You can borrow the XYL's can opener so you can modify the final amplifier to the tank coil/coupling circuit of the old time transmitter. This will eliminate one decibel of loss due to the transmatch, resulting in a power to the antenna of 93 to 85 watts. But this is a radical approach; you might damage the can opener.

A more moderate approach is to replace the coaxial line with an open wire feeder. This feeder has a minimum loss over the 80 meter band and the other high frequency bands through ten meters. The loss over the whole range now is the maximum of one decibel over the range of 3 to 29.7 megacycles, with 80 watts of power delivered to the antenna. The loss is essentially from the transmatch.

An important point: note that the charts of fig. 4 and fig. 5 cannot be used under these conditions. A little study is indicated here. When you realize the import of the charts you will have a fundamental command of transmission line theory.

Open wire transmission line is the most practical approach to antenna feeding over the frequency range of one through twenty nine megacycles and this type of line is widely used in broadcast and commercial communications applications, as well as practical amateur installations.

It is possible that open wire line cannot be used at a particular location, as is the case at W2IVT, where the transmission line must be threaded through many fire escapes en route to the roof. Very low loss coaxial line which has no more loss than open wire line may be used and many types with large diameters and extremely low loss are available, but at rather high prices. A good compromise is the JT200 Type manufactured by Times Wire and Cable Co. This cable has lower loss than RG-17U and is light enough so installation is not a problem. The loss for one hundred feet is only .11 decibels at 3.5 megacycles and 0.3 decibels at 30 megacycles. However, it is comparatively inexpensive when compared to air dielectric cables. The manufacturer has discontinued this cable but there is a good chance that the distributors have some on their shelves. With this low loss there is very little difference in the operation of this cable as a resonant line when compared to an open wire line, as you will note from perusal of figs. 4 and 5.

Of course, RG-17/U will also perform very well because it has less than half the loss of RG-8/U. It is difficult to install because of the great weight but many amateurs find means to overcome this type of disadvantage.

For those who are still not satisfied with the loss introduced by the Transmatch and have only an XYL with a motorized can opener there is one way to right the wrong that has been done. Design and build a linear amplifier using the wide impedance coupling circuit circa 1934. ■

antennas

BY WILLIAM I. ORR,* W6SAI

PENDERGAST opened the door of the shack. A scimitar of cold air slashed across his face and a flurry of snow sifted into the room. He closed the door hurriedly and said, "It's a cold night on the moor! Glad I don't have to shinny up a tower to work on an antenna tonight." Sensing no reply, he looked over at me and noted, "Still digging through the mail? Anything interesting?"

I dropped the pile of mail into my lap. "Never underestimate the ingenuity of a radio amateur," I replied. "Lots of hams are interested in the so-called "invisible" antennas because they have problems getting a sky-wire in the air." I paused, and pulled a letter out of the pile.

"Here's a great letter from John Milford, DA1JM. He's at a military base in Germany. Listen to his problem and how he solved it . . . 'I live on base and the houses are nearly identical on each and every base in Germany. They are 3 or 4 stories high, with either a flat or peaked roof. Until recently, we had a flat roof with a 30 foot tower atop it. The tower was capped off with a 2 element Quad built from the data in your "Cubical Quad Antennas" handbook[1].

'The flat roof is being replaced with a peaked roof, because of snow loading, I guess, and the antenna had to come down. And it can't go back up, because Uncle Sam doesn't want any antennas sticking out of the new roofs. All the roofs in the U.S. bases are being replaced with new, peaked roofs! Worse, still, the new roofs are all-metal construction, eliminating the possibility of an antenna under the roof.

'To get around this problem, I put up a vertical dipole on the side of the building, with a reflector. A simple two element beam, held to the vertical side of the wood building by small standoff insulators! In order to disguise the antenna, insulated wire was used with the same color jacket as the building color. A balun was used on the driven element and I painted it the same color as the building. The coax was run perpendicular to the driven element, half the distance to the reflector, and then straight down to the shack window. An old military rule of camouflage is that in a jungle or wooded area curved lines are best hidden, but in the open straight lines draw least attention! The finished antenna was well disguised and would be unnoticed if you did not know it was there.

'The beam worked so well I added 10 and 15 meter elements in a V-formation, at about 150 degrees to the 20 meter elements (fig. 1).'

"Pretty clever," said Pendergast. "Does DA1-JM say how the beam works out?"

I continued reading, "The antenna works well, though not as well as the Quad atop the tower. It seems to have good forward gain and a front-to-back ratio of about 15 db. The s.w.r. is quite low on all bands, running about 1.3 at resonance."

"Well," said Pendergast, "That proves it is pretty hard to keep a sharp ham off the air."

"Correct," I replied. "And here's a novel antenna scheme from Bob, WA2PCL. He can't put up a ham antenna, either, but all the apartments in his area have wash lines running out to poles in the back yard. Silly, isn't it? A wash line is OK, but a ham antenna on the roof is *verboten!*

"So Bob made the wash line into an antenna

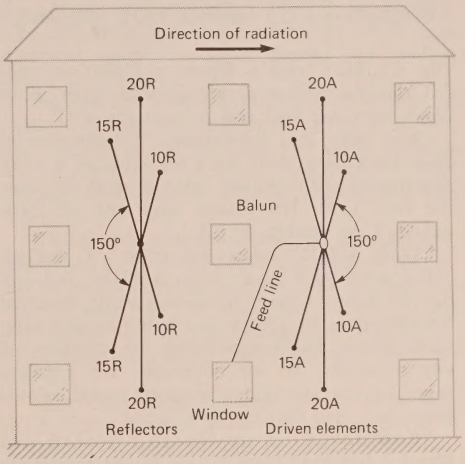

Fig. 1—DA1JM's "invisible" beam antenna in a vertical position on the wall of a 3 story wood frame apartment building. Beam dimensions are normal. The multiple reflectors are connected at the mid-point. The elements are constructed of insulated wire, painted to match the building and are held in position with small standoff insulators. The coaxial line is brought in a window. The beam is only one-inch away from the wood siding.

*48 Campbell Lane, Menlo Park, CA 94025.

[1] "All About Cubical Quad Antennas," Orr, Radio Publications, Wilton, Conn. 06897 ($3.95 plus 25¢ postage).

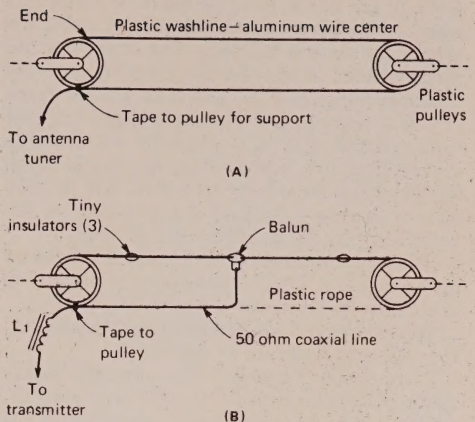

Fig. 2—WA2PCL's antenna is a washout! (A) Long wire antenna running back and forth between two plastic pulleys resembles a clothes line. End-fed antenna tuner is used in conjunction with a radial ground wire in the shack. (B) Dipole antenna with coaxial feed. Outer conductor of coaxial line should connect to left-hand side of dipole. Coaxial line is wrapped around ferrite core (L_1) to provide r.f. choke to suppress line currents. Choke consists of 3 turns of coaxial line passed through Indiana General CF-117 ferrite toroid, making a coil 4 inches in diameter for RG-58/U line. For data on ferrite, write Indiana General Corp., Crow Mills Rd., Keasby, NJ 08832. Core is Q-1 material, 1.875" diameter.

(fig. 2). He's tried a dipole and also an end-fed antenna, with a simple antenna tuner. Both ideas work out well and he's on the air."

"Not bad," said Pendergast. "I remember in New York City, there were big areas of 4 story apartments with clothes lines draped all over the rear yard. No reason why one of them wouldn't do double duty."

"Well, K4MD takes the prize," I replied. "He's stuck with an antenna problem, and one day he heard a ham in Pennsylvania describe his antenna. The fellow was living in an apartment house which prohibited the erection of *any* antennas. So he connected his antenna tuner to the aluminum window frame of his room and used that for an antenna.

"K4MD tried this out. He ran a piece of wire about 2 feet long from his rig to the aluminum window and used a quarter-wave ground radial in the shack, running along the floor. He used the window frame antenna on 40 meters.

"K4MD had an end-fed wire outside to compare the window antenna against, and found out it was about one S point weaker than the end-fed wire. He used it on some schedules and it worked fine. Admittedly, the window frame antenna is no DX antenna, but it does work and would be a boon to a cliff dweller who can't erect an outside antenna. Too bad we don't know who the Pennsylvania ham is who gave the idea to K4MD."

Pendergast scratched his head. "Glad I don't have antenna problems," he muttered.

"Sometimes you can't help yourself," I replied. "Here's a great letter from W9IZ with a report on an attic antenna. Some years ago Bill put up a 2 element beam on a tower. He moved about a mile, and took down the beam. Before he got it up again, his daughter moved to Boston and he wanted to work a phone patch with her.

"Since it was the dead of winter, he didn't want to put the old tower up, so Bill put his 2 element beam up in the attic of his home. This was about 25 feet high, I imagine.

"Bill says, 'I cut the beam up into 4 or 5 pieces, maneuvered it up into the attic through a closet ceiling access cut-out, reassembled it and—with a few pieces of 1 × 2 wood—hung it on the rafters. I then took it all down and reversed the elements and put it back again, having found I had aimed it at California instead of Massachusetts!

'A word of caution! When installing an attic antenna, *do not* grab hold of a rafter and a wasp nest at the same time. This could cause one to step through a bedroom ceiling, incurring the displeasure of the XYL, etc.

'Since I had used the same beam before, I had somewhat of an idea of what to expect in the way of results. It really beams! And I've been using it for seven years, and have never bothered to put the old tower up again!' "

"That's really great," said Pendergast. I always wondered what snow would do when an indoor antenna was used."

"I once read an article about the hams at the

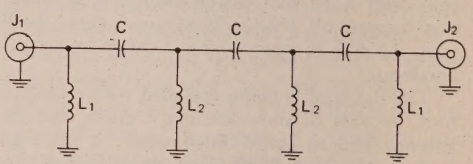

Band	80	40	20	15	10
L_1 (μH)	3.2	1.6	0.8	0.42	0.325
L_2 (μH)	1.6	0.8	0.4	0.21	0.17
C (pf)	600	300	150	80	62
f_{CO} (mHz)	2.5	5.0	10.0	18.0	25.0

Fig. 3—Low-pass filters for receiver protection. Each filter protects from signals lower in frequency than the designated band. Capacitors are silver mica, and inductors may be high-Q receiving type coils with movable powdered iron slug. Filter is built in aluminum box with coils arranged for minimum coupling between them.

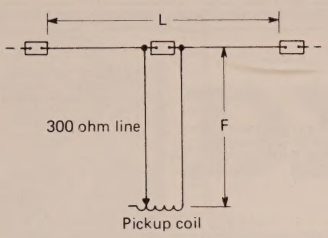

Antenna length, L	136	275.5	67	103
Feeder length, F	66	99	65	82.5
Bands	80–40–20	160 thru 20	40–20–10	80–40–20
Nominal input impedance	1200Ω	1200Ω except 75Ω on 40M	75Ω = 40M 1200Ω = 20, 10M	1200Ω

Fig. 4—Original Collins "multiband" antenna, the grandfather of the modern G5RV antenna. The antenna is center-fed, with flat-top and feeder length chosen to provide either a 1200 or 75 ohm termination at the transmitter on various bands. The 300 ohm line was made of aluminum tubing. Antenna was described in the 1937 issue of the *Radio Handbook* as well as the ARRL *Handbook*. Made with modern, open-wire 300 ohm line, and used with an antenna tuner, the Collins antenna serves as a good multiband antenna today. 300 ohm ribbon line may be used for low power, if feeders are cut to 82 percent of lengths given in table.

Antarctic bases who laid their antennas right on the snow," I replied. "It seems to be a good insulator."

Pendergast looked out of the shack window. The snow, which had been falling steadily, had now stopped, and there were only small flurries in a clearing sky. He sighed.

"It may seem silly at this time of year to think of Field Day", he said, "But I'm going to try to get things organized early this year so it won't be a last minute panic. One of the things that would help, I think, is a set of low pass filters for each band. When you go multi-operator, a real problem is receiver overload, especially from a nearby transmitter on a lower band. Have any ideas?"

"A simple low pass filter may help," I replied. "For example, a design like this, built into a small aluminum box would attenuate low frequency signals, provided the signals did not sneak around the filter and get directly into the receiver (fig. 3). For example, the 80 meter filter attenuates all signals below 2.5 mHz, which includes the 160 meter band. The 40 meter filter cuts off at 5 mHz, knocking out the 80 and 160 meter bands. The 20 meter filter cuts off at 10 mHz, knocking out the 40, 80 and 160 meter bands, and so on. They can be built using little, high-Q coils and will fit in a very small box."

"Thank you," said Pendergast. "I'll copy the information in my little black book." He paused. "Before I push off into the snow and sleet, why don't we have a little discussion about the G5RV antenna. I work a lot of Aussies and G's and many of them use the G5RV, but they don't tell what it is on their QSL card. Do *you* know what a G5RV antenna is?"

"Well, I think so," I replied. "Basically, it is a center-fed, multi-band antenna. Sometimes it uses an antenna tuner, and sometimes not. If my memory is correct, this design was first publicized by Collins Radio Company in 1937 as the 'Collins Multiband Antenna' (fig. 4). The original description was in the 1937 ARRL *Handbook*, and also the 1937 *Radio Handbook*. Antenna dimensions were chosen so that when a 300 ohm feedline was used, the impedance at the bottom end of the line was either a low, or high value (75 ohms or 1200 ohms, if my memory is correct). Then, either a series-tuned or parallel-tuned network was used to couple the antenna system to the transmitter.

"The original antenna was written up in the 1936 issue of the *Collins Signal* magazine, as an adjunct to the Collins 30FXB transmitter. The 300 ohm line was constructed of ¼-inch diameter aluminum tubes spaced 1½ inches, center-to-center.

"As you can see from the illustration, several lengths of flat-top and feeder were available, and the end of the feedline was either coupled to the tank coil of the transmitter via high voltage capacitors, or a tapped pickup coil was used.

"The G5RV antenna is the 103 foot version, shortened to 102 feet for some obscure reason. Either open-wire line, or 300 ohm ribbon line may be used (fig. 5). This information is from the RSGB *Radio Communication Handbook*, 4th edition—a darned good reference work, by the way.

"The G5RV antenna can also be used with a 75 ohm twin-lead feeder. In any event, it is a refined version of the original Collins antenna, transplanted to England."

Pendergast smiled. "It seems a lot of antennas are named after popular DX stations that use them. The VS1AA antenna is the old single-wire-fed antenna called the *Windom*. That, of course, is named after 'Windy,' W8GZ, who popularized it. And don't forget the popular W8JK beam, too." He began to tug on a heavy sweater and prepared to leave.

CURTIS KEYER

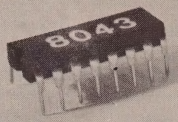

$24.95?

A remarkable new CMOS IC, created specifically for the CW op brings Curtis keying within everyone's reach. One 16 pin IC contains all features of the EK-420 (Oct. '73 QST review) . . . self-completing dots, dashes and spaces; iambic option; dot memory; weight control; key debouncing; sidetone and almost zero power drain. You add pots, pwr supply, speaker, chassis and customize as you like.

8043-1 . . . Type 8043 IC, PCB, socket and manual $24.95

8043-2 . . . Above plus partial kit excluding pots, spkr, chassis, jacks, etc. Solid state ±300V, 200mA keying $49.95

Postage anywhere in U.S.A. by air $1.50

CURTIS ELECTRO DEVICES, INC.

Box 4090, Mountain View, CA 94040

master charge THE INTERBANK CARD

CQ Country Chart

A two color, wall-sized country chart is available on poster stock and in large type for only $1.25 per copy postpaid. Address request to: CQ DX Country Chart, CQ Magazine, 14 Vanderventer Ave., Port Washington, N.Y. 11050.

HIGH INTENSITY STROBE WARNING LIGHT

With The Brilliant Flash!

CAN BE SEEN FROM HIGH FLYING AIRCRAFT OVER 100 MILES AWAY

Candle Power: *BL426 strobe produces in excess of 1,000,000 candle power assuring maximum visibility.

Dependability: Its low current requirement, no moving parts, and long life electronic components insure the maximal safety protection at all times. It is dependable in extreme hot or sub-zero weather (no moving parts to freeze up). Circuitry is dipped in protective coating compound to prevent corrosion.

Mounting: Mounting plate is designed for permanent installation.

GREAT FOR BOATS! FIRE CARS!

Now in use by: Police Departments ● Oil Companies ● Ambulances ● Utility Trucks ● Telephone Trucks ● Railroads ● Airport Vehicles ● Highway Maintenance Trucks ● Alarm Systems ● City and County Vehicles ● Fork Lift Trucks.

SPECIFICATIONS

Weight	5 lbs.	Bulb	Xenon flash tube
Height	10"	D. C. Voltage	12
Optic Lens	Plastic (Red, amber, blue, clear)	Current	3 amps
		Candle Power	1,000,000
Case & mounting plate	Aluminum	Flash Rate	60 to 80 F.P.M.

Model BL4-26, 12V-DC @ 3 amps $99.95

For magnetic mount and cigarette lighter plug add $11.

NOTE: When ordering, specify color of Dome Lens — available in red, blue, amber and clear. Send check or money order to:

HOUSE OF POWER ° P.O. Box 306, Merrick, N.Y. 11566

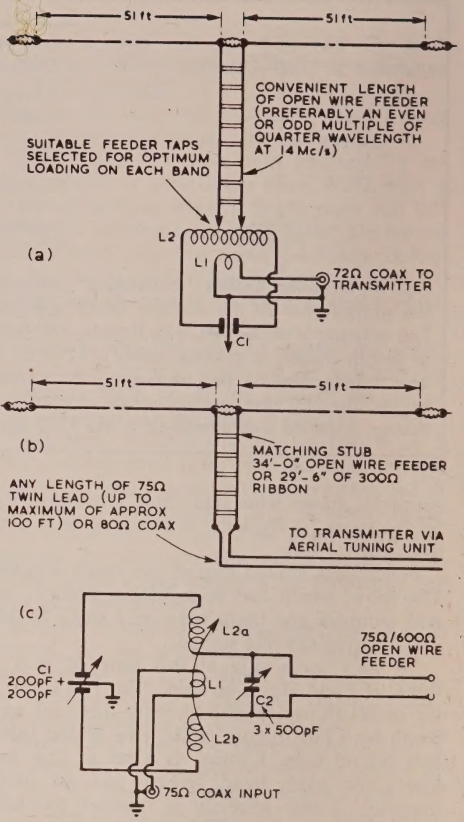
51 ft
51 ft
CONVENIENT LENGTH OF OPEN WIRE FEEDER (PREFERABLY AN EVEN OR ODD MULTIPLE OF QUARTER WAVELENGTH AT 14 Mc/s)
SUITABLE FEEDER TAPS SELECTED FOR OPTIMUM LOADING ON EACH BAND
(a)
L2
L1
72Ω COAX TO TRANSMITTER
C1
51 ft
51 ft
(b)
MATCHING STUB 34'-0" OPEN WIRE FEEDER OR 29'-6" OF 300Ω RIBBON
ANY LENGTH OF 75Ω TWIN LEAD (UP TO MAXIMUM OF APPROX 100 FT) OR 80Ω COAX
TO TRANSMITTER VIA AERIAL TUNING UNIT
(c)
L2a
75Ω/600Ω OPEN WIRE FEEDER
C1 200pF + 200pF
L1
C2
3 x 500pF
L2b
75Ω COAX INPUT

Fig. 5—Modern G5RV antenna, today's version of a 1937 idea. (A) Antenna tuner used with G5RV for multiband operation. (B) G5RV fed with matching stub and low impedance transmission line. (C) Universal antenna tuner. Impedance transformation ratio depends upon capacitance ratio of C_1 and C_2. Coils L_1 and L_2 are standard tuner coils. (Drawing courtesy of RSGB and *Radio Communication Handbook*).

"Season's Greetings and best wishes for 1975," he said with a smile. "What do you predict for amateur radio, antenna-wise, for the coming year?"

"Well, as Bob Booth, W3PS, says, 'It is difficult to prophetize, especially with respect to the future.' However, my guess is that there will be increased interest in log-periodic and log-periodic dipole arrays for the h.f. bands, increased interest in low frequency antennas for 80 and 160 meters—as the sunspot cycle drops—and more interest in moonbounce and moonbounce antennas. That guess covers a broad enough field so I can't be 100 percent wrong!"

Pendergast opened the door and a flurry of snow slid into the room. "Best Holiday Greetings," I said, "And may all your DX stations come back to you in 1975." ■

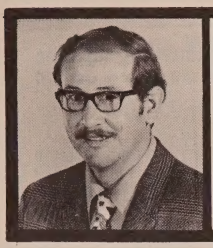

DX

BY JERRY HAGEN,* WA6GLD

THE DX Department certainly hopes that 1974 has been a good year for all and that the DX fraternity enjoys a peaceful holiday season. We also wish to thank the enthusiastic DXers who contribute information for the DX column and help make the job of editing a very enjoyable one.

USA Bicentenary Special Calls

In the June DX COLUMN, we noted that the FCC had tentatively planned for a special prefix authorization for the USA Bicentenary in 1976. The FCC later asked that comments on a prefix scheme be suggested by amateurs. At this time we have received two possible as outlined below.

Rich, K1OME writes "A possible prefix procedure would be to give each U.S. Amateur the option of substituting a two-numbered figure instead of the normal call area number. This figure would correspond to the order in which a particular state entered the Union. Thus, a station in Delaware would substitute "Ø1" for the "3" and would be WØ1XXX, KØ1XXX and etc. Likewise a Pennsylvania station would be WØ2XXX and onward to KH5ØXXX for Hawaii, the 50th state. These would not all be special prefixes by current WPX criteria, but they seem more appropriate than K or W prefixes which are allocated for special event stations at present. This system seems to be acceptable to the FCC criteria of being optional and would not involve FCC paperwork."

Gary, W6NJU proposes a straight conversion of prefixes with the substitution of A for W, AA for WA, N for K and NB for WB. However, Gary notes that there seems to be some confusion over assigning of prefixes as A2, A4 and several other A prefixes have been authorized to other countries. (*Ed. note: we have written to the ITU asking about this and will report the results in a future column*).

A second idea would be to have a series of blocks to chose from. This might be harder to understand but if specific blocks were used, one could still convert and relate to either W, WA, WB, etc. This would run something like W could use AA through AL, K could use NA through NL, WA could use NM through NS and WB could use NT through NZ. KH6 and KL7 would convert to KHØ and KLØ. Others such as KB6 and KP4 could also convert to Ø. Thus, W6NJU would have the choice of becoming AA6NJU, AB6NJU, AC6NJU. Picking prefixes in that block would always relate back that this was W6NJU.

*P.O. Box 1271, Covina, CA 91722

The CQ DX Award Program

C.W. DX

162.....K4KQB

2×SSB DX

366.....WA2FKF

367.....K9WEH
368.....K4KQB
369.....W1LQQ
370.....W3QND
371.....LA3UQ
372.....K5FKD

Endorsements

C.W.: K4KQB-150
2×S.S.B.: I8YRK-310, K9WEH-300, W4BQY-250, K4KQB, W3QND, K5FKD-200

Complete rules and application forms for the *CQ* DX Award Program may be obtained by sending a business size, self-addressed, stamped envelope to DX Editor, P.O. Box 1271, Covina, CA 91722.

Here And There In The World Of DX

We received several nice notes from amateurs going on DXpeditions during the spring and summer of this year. Some of their comments are recalled below.

Paul, WA3IJR and Glenn, WAØVPK made a five-day trip to Gibraltar and signed ZB2WY and ZB2WZ from the east side of the "Rock". They made over 1300 QSO's, however, only

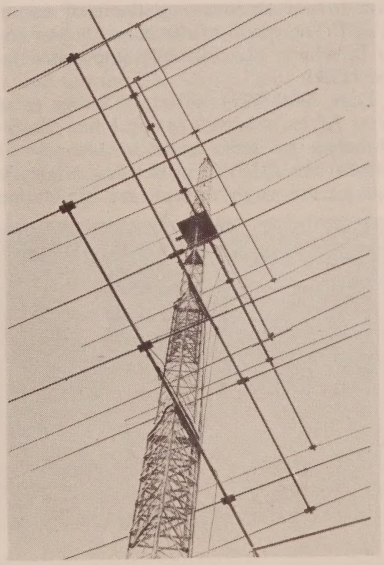

Ready for a contest? W9IY uses this impressive array which includes stacked 20 meter yagi's and yagi's for 40, 15 and 10 meters.

WPX HONOR ROLL

The WPX Honor Roll is based on confirmed current prefixes which are submitted by separate application in strict conformance with the CQ Master Prefix List. Scores are based on the current prefix total, regardless of an operators all-time prefix total.

Mixed

W4LRN 1375	DJ7CX 1004	I6SF 893	WAØKDI 824	K8UDJ 750
VE3GCO 1142	W4BQY 1002	W4WSF 877	SM7TV 822	CT1LN 749
WA6MWG 1120	WB2FMK 980	DL1CF 872	W6NJU 811	WA5LOB 749
F9RM 1100	ON4QX 975	K2AAC 863	W9WHM 811	PY4AP 735
W8LY 1082	W4IC 950	K6SDR 862	IØJX 803	KØBLT 733
W4CRW 1076	PAØSNG 943	W4BYU 859	WA5VDH 789	WA6EPQ 713
W3PVZ 1062	DL1MD 940	WØAUB 856	W3YHR 777	K6ZDL 708
W6TCQ 1056	W9FD 938	YU2DX 855	JA1AG 765	PAØVB 706
W3GJY 1052	K1SHN 934	WA2EAH 850	WA6JVD 763	W9ZTD 700
W8ROG 1051	WB4KZG 930	G3DO 849	WB4SIJ 755	WAØCPX 693
W2NUT 1025	YU1AG 928	W6ISQ 847	K2ZRO 751	WA6TAX 655

C.W.

W8LY 1067	W2AIW 813	VO1AW 742	I6SF 702	K6ZDL 609
W8KPL 1003	VK3AHQ 809	WA6JVD 741	W4IC 700	VE4OX 600
DL1QT 900	G2GM 785	YU1AG 741	OK2DB 693	OK2QX 600
W2HO 885	DJ7CX 782	W3ARK 739	W6ISQ 685	
WB2FMK 870	W4BYU 768	K2AAC 726	SM5BNX 652	
W9FD 870	K7ABV 767	WA6MWG 719	K2ZRO 635	
ON4QX 851	K1SHN 746	W6TCQ 707	K1LWI 629	

SSB

W4NJF 1100	WA6MWG 877	IT9TJ 806	OE2EGL 730	WA6TAX 665
F9RM 1047	ZL3NS 874	I4ZSQ 801	W6RKP 725	W2EHB 659
IØAMU 957	I8KDB 873	W4IC 800	W6YMV 720	WB4SIJ 652
DL9OH 932	W0YDB 869	I8YRK 766	OK1MP 715	WB4KZG 650
CT1PK 930	W6TCQ 860	G3DO 765	YU1AG 710	CR7IK 613
W9DWQ 917	DL1MD 858	K1SHN 753	WB6DXU 708	I4LCK 608
HP1JC 903	F2MO 835	W3YHR 750	WB2NYM 702	WA5VDH 607
IØZV 886	PAØSNG 824	WA5LOB 747	WA2EAH 700	
K2POA 883	W3DJZ 818	PY3BXW 734	CX2CN 679	

six W/K stations were worked due to the 1300 foot rock to the west of the operating QTH. The fellows hope to return to ZB2 in the spring and operate from the west side during the ARRL DX Test if a suitable hotel and permission to put antennas on the roof can be obtained. The photo of the island leaves no doubt as to why it was virtually impossible to work the USA!

Dan, WA9FZQ writes, "During a visit to West Africa this past spring I had the pleasure of being the house guest of Jacques, 5U7BB, and Elyane, 5U7YK, in Niamey, Niger. Jacques was kind enough to lend me his station and, from May 23 through May 26 (1974) I promised all those I contacted that I would QSL 100% and that cards should be sent to my home call, WA9FZQ. I cannot confirm contacts for days other than those of my operation, however, I have been inundated by QSL's running the gamut of Jacques' entire two-year stay in Niamey!

In spite of the 110° heat, I attempted to give a rare country to as many hams as possible. I will QSL 100% all contacts made during my stay at 5U7BB. Naturally, I ask that stations send along return postage if they want a direct reply."

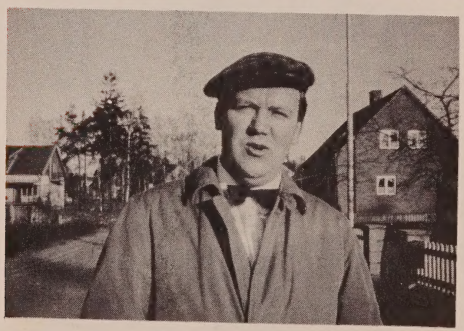

At the California DX Convention, VK3JW accepts a trophy from W6AOA for his effort in putting Mellish Reef on the DXCC list. (Photo via West Coast DX Bulletin)

John, SM7CRW. His business card reads, "Used cars, land, whiskey, nails, fly swatters, racing forms and bongos." What, no ham radio, John?

The WPX Program

Mixed

455.....W9LJL
456.....WB8LVA
457.....OK2BOL
458.....WA8TFJ

C.W.

1352.....PA0AAC
1353.....W3OJS
1354.....JA2IU
1355.....F2VO
1356.....JA2EG
1357.....WA2ZWH
1358.....DL1YK
1359.....WA8TFJ
1360.....LA7FJ

S.S.B.

817.....I3GRX
818.....WA8TFJ

WPNX

73.....WN4CTA
74.....WN8TFJ

VPX

79.....VU-0020

Endorsements

Mixed: WA6MWG, VE3GCO-1100, W4BQY, W4CRW, W3GJY-1050, W4WSF-1000, K1SHN-950, I6SF-900, WA2EAH-850, K4CIA-800, W2MB-750, K7NHG, WA6TAX-700, HI8LC-600, WA2DHF, K4ZYU, WA8-TFJ, OK2BOL-500.
C.W.: WB2FMK-900, G2GM-850, WA6JVD, WB4SIJ, K1SHN-750, I6SF-700, W3URE-650, WA9UES-600, W6CLM-500, K9DDA, G3FVC, WA1JMP, JA2IU, LA7FJ-400, PA0AAC, JA2EG, WA8TFJ-350.
S.S.B. I8AA, W0YDB-850, IT9JT-800, WA8TFJ-350.
WPNX: WN1ORL-150.
VPX: W4-10640-500, OE1-10117-400.
160 Meters: OK2BOL
80 Meters: OK2BOL
40 Meters: W4WSF
20 Meters: WA2EAH
Asia: JA1VE
Europe: W4-10646
North America: W4-10646
Oceania: W0-6437, JA1VE
South America: WA2EAH

Complete rules for WPX, WPNX and VPX may be found on pg. 67 of the February 1972 issue of *CQ*. Application forms and reprints of the rules may be obtained by sending a business size, self-addressed stamped envelope to WPX Award Manager, P.O. Box 1271, Covina, CA 91722.

Both Jacques and Elyane have now left Niamey. Cards for them, 5U7BB and 5U7YK, should be sent to F6AJW.

The *Long Island DX Association Bulletin* printed the following letter from Diane, VQ9-DC about the September DXpedition to Desroches. "When my OM John, VQ9MI, couldn't go, I offered my services to make the rough sea journey aboard the racing yacht *Stormy*—the sleek boat that won the Cape-to-Rio race two years ago. With a promise of good propagation for 10 days, I purchased stores while Bill, VQ9BP, Dick, VQ9D and Ron, VQ9M loaded all their gear plus gas, generators, tools and spares, together with personal and photographic kits. We set sail on Saturday afternoon September 7th, at 1300Z and thankfully arrived in calmer seas the following morning with a first light view of Desroches; 800 acres of beautiful, peaceful, remote island—the shorefront clothed with cedars, mangroves and tall palms, and the air filled with thousands of Red Cardinals.

A TH3 can come down faster than it goes up! That was the only incident to mar an otherwise routine setup of our stations. Even with a right-angle bend in one if its elements (note to Hy-Gain) it worked like a treat! Within minutes of my KW2000E getting warm, I was in contact with 5Z4NH. His "Wow" when I gave the /D, made our first day! Four days and sixty countries later, my rig went on the blink and from then on I was 2nd operator at the other rigs on 7, 14, 21 and 28 mHz, finally winding up with 75 countries.

The pretty DXer is Elyane, 5U7YK who has returned to France after two years of operating from Niamey. (Tnx WA9FZQ)

We were all very much impressed by the standard of operating of the calling stations. Their courtesy and standing by when requested were appreciated by us weary ops. The long queues increased as the nights progressed but we would have been disappointed if it had been otherwise. I was delighted to work into the YL-ISSB-ers system with Mary-Ann, WA3HUP ably pushing through as many callers as possible in the shortest amount of time and it was nice to have a contact with Harvey, W2IYX, amongst many other friends. By the way, we expect our special QSL cards from a Stateside printer in about six weeks—so don't despair, you will all collect one!

Lots of work but lots of fun, too. Like huge breakfasts cooked outside in the dark, smokey kitchen. With two wood open-fires going,

The QTH of ZB2WY and ZB2WZ was in this hotel . . . no wonder they had trouble working the US!

On the left is Paul, ZB2WY (WA3IJR) and on the right is Glen, WAØVPK during their DXpedition to Gibraltar.

smoke everywhere and the temperature at 90°F, it seemed difficult to produce true American meals like Mom used to make—especially for a Limey. But we survived and they ate everything I put in front of them, plenty of freshly caught fish, sausage, Chinese noodles and champagne. Bill adopted a puppy (or vice versa) which he promptly named "CQ" and which delighted us by joining us for meals and playfully chewing at our bare feet. We got in a little swimming, lots of photography and snorkelling, and Ron speared a very fine (delicious) lobster.

The two weeks flew by and again we were sailing (?) in very, very rough waters whipped by a 30-knot wind. For 15½ hours the only safe place was in one's bunk and it was a bleary-eyed, wet quartet that disembarked on the *Seychelles* at 0400Z on September 21st, with a single thought: not only was it worth every minute, but we would do it again.

ARRL DX Advisory Committee

The ARRL DX Advisory Committee has released the following questions for comment by DXers. Question number 5 appears to be the most controversial and the summary of replies should be most interesting!

1. Should home-station DXCC credit be given automatically (no actual contact need be made with the home station) to the activator of a DXpedition for the country visited?

2. Should check of QSL's for DXCC endorsements (for country totals of 120 through 290) be performed by IARU Societies?

3. Should a c.w.-only DXCC Award be established?

4. Should contacts made by the holders of special "ITU" calls be creditable towards their "regular-call" DXCC Award?

5. Should a country in which there has been no amateur radio activity for a period of ten years be considered (for purpose of DXCC Honor Roll) as are deleted countries? (Any subsequent activity would reinstate past credits. This to be retroactive to all current listings on the ARRL Countries list.)

6. Should yearly listing of all holders of the 5BDXCC Award appear in *QST?*

7. Should DXCC Rule 9 be changed to read "Contacts may be made from within the continental boundaries of any country"?

8. Should DXCC Rule 9 be changed to read "All stations must be contacted from a fixed location for which the original DXCC Certificate was issued? One exception is allowed to this rule: Where the station moves within the original Call Area or to an adjacent Call Area, or from one country to another, all contacts must be made from within a radius of 500 miles of the initial location.

If you have any comments on any of these questions, write the DXAC via ARRL HQ. Whatever is received at HQ will be copied and sent off to all members. ■

This is Jerry, 4W1GM, of Sanaa, Yemen, who previously signed SVØWUU. He looks for W/K's weekends at 1800Z on 14.222 mHz. Photo via W3HNK, Jerry's QSL Manager.

The WAZ Program

S.S.B. WAZ

1225 JA4BBN	1227 W8EX
1226 WA1JMP	1228 W3DBT

C.W.—Phone WAZ

3756 HI8LC	3763 W5JLU
3757 I8LEL	3764 YU2RIO
3758 W1LQQ	3765 YU2CAW
3759 HB9ASK	3766 YU2RAZ
3760 DJ8CR	3767 OZ1W
3761 W7TE	3768 DK6ML
3762 W6HJ	3769 DJ8JP

Phone WAZ

500 WA9SLD

Complete rules for the Single Band WAZ Program are shown on pgs. 57-58 of the December, 1972 issue of *CQ*. Complete rules for regular WAZ may be found on pgs. 64-66 of the June, 1970 issue. Application blanks and reprints of the rules for WAZ awards may be obtained by sending a self-addressed, stamped envelope to the Assistant DX Editor, P.O. Box 205, Winter Haven, FL 33880.

CALL 516-883-6223
FOR DIAL-A-PROP

Propagation

BY GEORGE JACOBS,* W3ASK

ALTHOUGH solar activity continues to decline slowly, winter propagation means higher daytime frequencies and improved conditions on *10, 15* and *20* meters during the hours of daylight. It also means longer hours of darkness and considerably lower static levels, which should result in improved DX conditions on *40, 80* and *160* meters during the hours of *darkness*. All-in-all, it should be a relatively good month for DX propagation, whatever h.f. band you operate on.

Ten meters should open to several areas of the world when conditions are normal. Signals should peak towards Europe, Africa and the east before Noon; towards South America during the early afternoon and towards the Pacific and Australasia during the late afternoon.

Openings on *15 meters* should follow a similar pattern, but this band should open more often than *10 meters,* stay open longer, and with stronger signal levels.

Expect *20 meter* openings in almost all DX directions for several hours after sunrise. Signals should peak toward Europe and the east during the early afternoon; towards Africa an hour or two later; towards South America during the late afternoon and into the early evening; towards the Far East, the Pacific area and Australasia during the early evening and towards Antarctica during the evening almost to Midnight.

Forty meters should being to open for DX during the late afternoon, with the first signals coming from Europe. After sundown the band should open to Africa and to South America. Signals from the Pacific area, the Far East and Australasia should peak just before sunrise, but the band may be open for several hours earlier.

Fairly good DX is also expected on *80 meters* between sundown and sunrise. Signals from Europe, Africa and the east should peak before Midnight; signals from South America should be in for most of the hours of darkness; and signals from Australasia and the Pacific area should peak just before sunrise.

This should be quite an active month for *160* meter DXers. The ARRL Annual 160 Meter DX Test will be held on Dec. 7 and 8, and the 42nd Annual Trans-Atlantic DX Tests will be held between 0500 and 0730 GMT on Dec. 22. It looks like nature might cooperate with relatively good DX conditions for this band. Check for openings towards Europe and the east beginning about 8 P.M. and until 2 A.M. in EST time zone; 1 A.M. in CST; Midnight in MST and 11 P.M. *in* PST. Some openings towards the south, especially to the Caribbean area, should be possible from about 10 P.M. to 2 A.M. in all time zones. Openings towards the Pacific and Australasia favor west coast stations, but it's worth looking for them in all time zones between 4 A.M. and sunrise. Remember that DX conditions tend to peak on *160* meters about the time that the sun *rises* at the *easternmost* terminal of a DX path.

For *short-skip* openings during December of less than 250 miles, try *80* meters during the day and *160* meters at night. For openings between 250 and 750 miles, best bet is *40* meters during the day and *80* at night. Between 750 and 1300 miles try *20* during the day, *40* during the early evening and *80* later in the evening and until sunrise. For openings between 1300 and 2300 miles, *20* looks best during the day, but check *15* during the afternoon. Try *40* during the evening to about Midnight and *80* for the remainder of the night to sunrise. An occasional short-skip opening between approximately 1500 and 2300 miles may be possible on *10 meters* during the afternoon.

LAST MINUTE FORECAST

Day-to-Day Conditions Expected For December, 1974

	Rating & Forecast Quality			
Propagation Index .....(4)		(3)	(2)	(1)
Date *November*				
Above Normal: 3, 6, 29-31	A	A-B	B-C	C
Normal: 1-2, 4-5, 7, 14-17, 21-24, 26-28	A-B	B-C	C-D	D-E
Below Normal: 8-10, 13, 18-20, 25	B-C	C-D	D-E	E
Disturbed: 11-12	C-D	D	E	E

Where *expected signal quality is:*

A—Excellent opening, exceptionally strong, steady signals.

B—Good opening, moderately strong signals with little fading or noise.

C—Fair opening, signals between moderately strong and weak, with some fading and noise.

D—Poor opening, signals weak with considerable fading and noise.

E—No opening expected.

HOW TO USE THIS FORECAST

1. Find *propagation index* associated with particular band opening from Propagation Charts appearing on the following pages.

2. With the *propagation index*, use the above table to find the expected signal quality associated with the particular opening for any day of the month. For example, all openings shown in the Charts with a *propagation* index of (3) will be fair-to-good on Dec. 1-2, (B-C), good-to-excellent on Dec. 4 (A-B) and poor on Dec. 11 (D), etc.

For updated information dial Area Code 516-883-6223 for DIAL-A-PROP, or subscribe to weekly MAIL-A-PROP, P.O. Box 86, Northport, NY 11768.

*11307 Clara St., Silver Spring, MD 20902.

How To Use The DX Propagation Charts

1. Use Chart appropriate to your transmitter location. The Eastern USA Chart can be used in the 1, 2, 3, 4, 8, KP4, KG4 and KV4 areas in the USA and adjacent call areas in Canada; the Central USA Chart in the 5, 9 and 0 areas; the Western USA Chart in the 6 and 7 areas, and with somewhat less accuracy in the KH6 and KL7 areas.

2. The predicted times of openings are found under the appropriate meter band column (10 through 80 Meters) for a particular DX region, as shown in the left hand column of the Charts. An * indicates 80 Meter openings. Openings on 160 meters are likely to occur during those times when 80 meter openings are shown with a *propagation index* of (2), or higher.

3. The *propagation index* is the number that appears in ( ) after the time of each predicted opening. The index indicates the number of *days* during the month on which the opening is expected to take place as follows:

(4) Opening should occur on more than 22 days
(3) " " " between 14 and 22 days
(2) " " " between 7 and 13 days
(1) " " " on less than 7 days

Refer to the "Last Minute Forecast" at the beginning of this Propagation column for the actual *dates* on which an opening with a specific propagation index is likely to occur, and the signal quality that can be expected.

4. Times shown in the Charts are in the 24-hour system, where 00 is midnight; 12 is noon; 01 is 1 A.M., 13 is 1 P.M., etc. Appropriate *standard* time is used, *not* GMT. To convert to GMT, add to the times shown in the appropriate Chart 8 hours in the PST Zone, 7 in the MST Zone, 6 in the CST Zone and 5 in the EST Zone. For example 14 in Washington, D.C. is 19 GMT and 20 in Los Angeles is 04 GMT, etc.

5. The charts are based upon a transmitter power of 250 watts c.w., or 1 kw, p.e.p. on sideband, into a dipole antenna a quarter-wavelength above ground on 160 and 80 meters, a half-wave above ground on 40 and 20 meters, and a wavelength above ground on 15 and 10 meters. For each 10 db gain above these reference levels, the *propagation index* will increase by one level; for each 10 db loss, it will lower by one level.

6. Propagation data, contained in the Charts has been prepared from basic data published by the Institute For Telecommunication Sciences of the U.S. Dept. of Commerce, Boulder, Colorado, 80302.

Sunspot Cycle

The Swiss Federal Observatory at Zurich reports a mean sunspot number of 42 for September, 1974. This results in a smoothed sunspot number of 36 centered on March, 1974.

A smoothed sunspot number of 28 is forecast for December, as the solar cycle continues to decline towards a minimum now estimated to be about two years away.

V.H.F. Ionospheric Openings

Quite a bit of meteor activity is expected during the month. *Geminids*, a major meteor shower, should begin on December 13 and last for about three days. Maximum intensity is expected at approximately 4 A.M. EST on December 14, with a meteor rate of about one a minute. This should permit fairly good meteor-type openings on both *6* and *2* meters. A second, but somewhat less intense shower period is expected later in the month. Called *Ursids*, it should take place on December 21 and 22, peaking at about 8 P.M. on the 22nd. A meteor rate of about 15 per hour is expected at its peak.

A secondary seasonal peak in sporadic-E propagation usually occurs during December (the major peak takes place during the summer months). This should result in some fairly good short-skip type openings on *6* meters, between distances of approximately 800 and 1400 miles. Conditions are most likely to peak during the early evening, but openings can occur at other times as well.

Some auroral-type v.h.f. ionospheric openings are also likely to occur during December, especially when ionospheric conditions on the h.f. bands are below normal or disturbed. Be sure to check on December 11 and 12, and auroral activity may also occur on the 8-10, 13, 18-20 and 25th of December.

160 Meter Annual DX Tests

W1BB informs us that the 42nd Annual TransAtlantic 160 Meter DX Tests will take place on Dec. 22, Jan. 12 and February 9, between 0500 and 0730 GMT. W/VE stations operate in the 1800-1807 kHz portion of the band while DX stations should operate in the 1825-1830 kHz portion. W/VE stations call "CQ FT DX" or "FT DX" for the first *three* minutes of each fifteen minute period starting on the hour. The remaining twelve minutes of each period are used for contacts or for CQ calls by DX stations.

This is not a contest, but a test period in which it is hoped to bring on the air as many stations as possible on both sides of the Atlantic, especially new stations that have not worked *160* meter DX before. W1BB expects that stations in as many as two dozen or more countries may be on during this year's test periods. If you're looking for DX activity on *160* meters, be sure to check into the test periods. With lower solar activity, this may be the best year for *160* meter DX since a decade ago.

Reports of QSOs made during the test periods should be sent for tabulation and propagation analysis to W1BB, Stewart S. Perry, 36 Pleasant St., Winthrop, Mass. 02152.

This month's column contains DX Propagation Charts valid through February 15, 1975. Short-Skip Propagation Charts for use during December appeared in last month's column.

The Editor of this column would like to take this opportunity to extend his warmest wishes to everyone, everywhere during this holiday season. 73, George, W3ASK

CQ'S DIAL-A-PROP

For the latest up to the minute propagation forecasts and special contest predictions call 516-883-6223 any time day or night for a recorded message on conditions.

December 15, 1974—February 15, 1975
Time Zone: EST (24-Hour Time)
EASTERN USA TO:

	10 Meters	*15 Meters*	*20 Meters*	*40/80 Meters*
Western & Central Europe & North Africa	09-11 (1)	08-09 (1) 09-11 (3) 11-12 (2) 12-13 (1)	06-07 (1) 07-09 (4) 09-11 (3) 11-13 (4) 13-14 (3) 14-15 (2) 15-17 (1)	15-16 (1) 16-17 (2) 17-19 (3) 19-00 (4) 00-02 (2) 02-03 (3) 03-05 (1) 17-19 (1)* 19-20 (2)* 20-02 (3)* 02-03 (2)* 03-04 (1)
Northern Europe & European USSR	08-10 (1)	08-09 (1) 09-10 (2) 10-11 (1)	06-07 (1) 07-09 (3) 09-12 (2) 12-14 (1)	16-19 (1) 19-23 (2) 23-03 (1) 19-02 (1)*
Eastern Mediterranean & Middle East	08-10 (1)	08-09 (1) 09-10 (3) 10-11 (2) 11-12 (1)	06-09 (1) 09-10 (2) 10-13 (3) 13-15 (2) 15-17 (1)	18-20 (1) 20-22 (2) 22-00 (1) 20-23 (1)*
West Africa	09-11 (1) 11-13 (2) 13-15 (1)	07-08 (1) 08-09 (2) 09-12 (3) 12-14 (4) 14-15 (3) 15-16 (1)	06-07 (1) 07-09 (2) 09-13 (1) 13-15 (2) 15-17 (4) 17-18 (3) 18-19 (2) 19-20 (1)	18-22 (1) 22-00 (2) 00-03 (1) 03-04 (2) 00-02 (1)*
East & Central Africa	10-13 (1)	08-10 (1) 10-12 (2) 12-13 (3) 13-15 (2) 15-16 (1)	07-13 (1) 13-15 (2) 15-17 (3) 17-18 (2) 18-19 (1)	18-00 (1)
South Africa	09-12 (1)	08-09 (1) 09-11 (2) 11-13 (3) 13-14 (2) 14-15 (1)	07-09 (1) 12-14 (1) 14-15 (2) 15-17 (3) 17-18 (2) 18-20 (1)	18-19 (1) 19-21 (2) 21-00 (1) 19-22 (1)*
Central & South Asia	*Nil*	17-19 (1)	06-07 (1) 07-09 (2) 09-11 (1) 18-21 (1)	06-08 (1) 20-22 (1)
Southeast Asia	*Nil*	17-19 (1)	06-07 (1) 07-09 (2) 09-12 (1) 19-21 (1)	06-08 (1) 20-22 (1)
Far East	*Nil*	16-17 (1) 17-18 (2) 18-19 (1)	06-07 (1) 07-09 (2) 09-11 (1) 16-18 (1) 18-20 (2) 20-21 (1)	05-08 (1) 05-07 (1)*
South Pacific & New Zealand	13-17 (1)	11-14 (1) 14-15 (2) 15-17 (3) 17-18 (2) 18-19 (1)	03-07 (1) 07-09 (2) 09-11 (1) 16-18 (1) 18-20 (2) 20-22 (1)	01-02 (1) 02-04 (2) 04-07 (3) 07-08 (2) 08-09 (1) 04-05 (1)* 05-07 (2)* 07-08 (1)*
Australasia	15-17 (1)	11-16 (1) 16-18 (2) 18-19 (1)	06-07 (1) 07-10 (2) 10-14 (1) 14-16 (2) 16-18 (1) 18-20 (2) 20-22 (1)	03-05 (1) 05-07 (2) 07-09 (1) 05-08 (1)*
Central America & Northern Countries of South America	09-10 (1) 10-12 (2) 12-14 (1) 14-15 (2) 15-16 (1)	08-09 (1) 09-11 (3) 11-13 (2) 13-15 (4) 15-16 (3) 16-17 (2) 17-18 (1)	06-07 (2) 07-09 (4) 09-11 (3) 11-15 (2) 15-17 (3) 17-18 (4) 18-19 (3) 19-20 (2) 20-22 (1) 22-00 (2) 00-06 (1)	17-18 (1) 18-19 (2) 19-21 (3) 21-04 (4) 04-05 (3) 05-06 (2) 06-07 (1) 19-20 (1)* 20-22 (2)* 22-02 (3)* 02-04 (2)* 04-06 (1)*
Peru, Bolivia, Paraguay, Brazil, Chile, Argentina & Uruguay	09-12 (1) 12-15 (2) 15-16 (1)	07-08 (1) 08-10 (2) 10-12 (1) 12-14 (2) 14-16 (4) 16-17 (3) 17-18 (1)	13-14 (1) 14-15 (2) 15-17 (3) 17-18 (4) 18-19 (3) 19-20 (2) 20-22 (1) 22-00 (2) 00-03 (1) 05-06 (1) 06-08 (2) 08-09 (1)	19-21 (1) 21-02 (2) 02-05 (1) 21-03 (1)*
McMurdo Sound, Antarctica	*Nil*	15-17 (1)	07-09 (1) 17-18 (1) 18-22 (2) 22-00 (1) 00-02 (2) 02-03 (1)	00-05 (1)

Time Zones: CST & MST (24-Hour Time)
CENTRAL USA TO:

	10 Meters	*15 Meters*	*20 Meters*	*40/80 Meters*
Western & Southern Europe & North Africa	08-10 (1)	08-09 (1) 09-12 (2) 12-13 (1)	06-08 (1) 08-09 (2) 09-12 (3) 12-13 (2) 13-15 (1) 22-00 (1)	16-18 (1) 18-20 (2) 20-00 (1) 00-02 (2) 02-03 (1) 17-20 (1)* 20-01 (2)* 01-02 (1)*
Northern & Central Europe & European USSR	*Nil*	08-11 (1)	07-08 (1) 08-11 (2) 11-13 (1) 22-00 (1)	17-19 (1) 19-22 (2) 22-01 (1) 19-00 (1)*
Eastern Mediterranean & Middle East	*Nil*	08-11 (1)	06-09 (1) 09-14 (2) 14-15 (1) 22-00 (1)	18-20 (2) 20-22 (2) 22-23 (1) 20-22 (1)*
West Africa	09-10 (1) 10-12 (2) 12-13 (1)	07-09 (1) 09-11 (2) 11-13 (3) 13-14 (2) 14-15 (1)	06-11 (1) 11-13 (2) 13-16 (3) 16-17 (2) 17-19 (1) 22-01 (1)	18-21 (1) 21-23 (2) 23-01 (1) 19-22 (1)*
East & Central Africa	10-12 (1)	08-11 (1) 11-13 (2) 13-14 (1)	06-12 (1) 12-14 (2) 14-16 (3) 16-17 (2) 17-18 (1)	19-23 (1)
South Africa	09-10 (1) 10-12 (2) 12-13 (1)	08-09 (1) 09-11 (2) 11-13 (3) 13-14 (2) 14-15 (1)	07-13 (1) 13-15 (2) 15-17 (3) 17-18 (2) 18-19 (1) 23-01 (1)	18-19 (1) 19-21 (2) 21-23 (1)
Central & South Asia	*Nil*	18-20 (1)	06-07 (1) 07-09 (2) 09-11 (1) 18-19 (1) 19-21 (2) 21-22 (1)	06-08 (1) 19-21 (1)
Southeast Asia	*Nil*	17-19 (1)	07-08 (1) 08-10 (2) 10-12 (1) 16-18 (1) 18-20 (2) 20-22 (1)	04-07 (1)
Far East	16-18 (1)	16-17 (1) 17-19 (2) 19-20 (1)	06-07 (1) 07-09 (2) 09-11 (1) 15-17 (1) 17-19 (2) 19-21 (1)	02-04 (1) 04-06 (2) 06-07 (1) 04-07 (1)*

*Indicates best time to listen for 80 Meter openings. Openings on 160 Meters are also likely to occur during those times when 80 Meter openings are shown with a forecast rating of (2), or higher.

[*Continued on page 71*]

Contest Calendar

BY FRANK ANZALONE,* W1WY

Calendar of Events

*Dec.	7-8	TOPS C.W. Contest
*Dec.	6-8	ARRL 160 Meter Contest
*Dec.	7-8	Space Net VHF Contest
*Dec.	8-14	Hoosier Amateur Radio Week
*Dec.	14-15	Spanish C.W. Contest
Dec.	14-15	ARRL 10 Meter Contest
Dec.	22	Hungarian Contest
Dec.	29	Zip Code Contest
Jan.	4-5	ARRL VHF Sweepstakes
Jan.	8-9	YL DX C.W. Contest
Jan.	11-12	YU 80 Meter C.W. Contest
Jan.	11-12	DL QRP C.W. Contest
Jan.	18	RTTY Flash Contest
Jan.	**24-26**	**CQ WW 160 C.W. Contest**
Jan.	25-26	French C.W. Contest
Jan.	26	RTTY Flash Contest
Jan.	29-30	YL DX Phone Contest
Feb.	1-2	ARRL DX Phone Contest
Feb.	2	Two Meter RTTY Contest
Feb.	8-9	QCWA QSO Party
Feb.	15-16	ARRL DX C.W. Contest
Feb.	22-23	French Phone Contest
Feb.	22-24	Vermont QSO Party
Mar.	1-2	ARRL DX Phone Contest
Mar.	15-16	ARRL DX C.W. Contest
Mar.	**29-30**	**CQ WW WPX SSB Contest**
Apr.	26-27	WAEDC RTTY Contest
May	17-19	Michigan QSO Party

*Covered in last month's Calendar.

ARRL 10 Meter Contest

Starts: 1200 GMT Saturday, December 14
Ends: 2359 GMT Sunday, December 15

Last year's initial contest was a big success in spite of the low sunspot cycle, and should be well attended this year.

This is a worldwide activity in which DX stations can work other DX and not be limited to working W/K and VE only. The same station may be worked both on phone and c.w.

Exchange: Stations in the 50 US states and Canada send RS(T) and state or province. Others send RS(T) and a contact number starting with 001. KP4, KV4, KZ5, KC6 and etc. also use the contact number. Stations not land-based give their ITU Region.

Scoring: Each completed QSO is worth 2 points, 4 points if its with a Novice. The multiplier will consist of US states, VE call areas, ITU regions and DXCC countries worked. (except US and Canada)

Awards: Certificates to the highest scoring single operator in each ARRL section, VE call area and DX country. Multi-operator and Novice awards will be given if three or more entries in a section are received.

It is recommended you send a large s.a.s.e. to ARRL who will provide you with more details and appropriate contest forms.

Mailing deadline for logs is January 21st to: ARRL Communications Dept. 225 Main Street, Newington, Conn. 06111.

Hungarian Contest

Starts: 0000 GMT Sunday, December 22
Ends: 2400 GMT Sunday, December 22

This is a worldwide type contest with operation permitted on all bands, both phone and c.w. There are three categories, single operator, multi-operator and s.w.l.

Exchange: RS(T) and ITU Zone number.

Scoring: Contacts between stations on the same continent 1 point, on different continents 3 points. Contacts with Hungarians, HA/HG5 are worth 4 points, and 5 points if its with the special HA5 prefix. The multiplier is determined by number of ITU Zones worked.

Awards: Certificates to the top scoring stations in each category in each country. The world leaders in each of the three categories will receive the Budapest Plaque.

A summary sheet with the scoring and other necessary information, and a signed declaration is also requested.

Mailing deadline is January 15th to: BRAL Contest Committee, P.O. Box 214, Budapest 134, Hungary.

Christmas Zip-Code Contest

Starts: 0000 GMT Sunday, December 29
Ends: 2359 GMT Sunday, December 29

This is the second of a series of Zip-Code contests organized by the South Eastern Virginia Wireless Assoc. There are 3 each year, Labor Day, Christmas and Memorial Day.

The same station may be worked once per band and Mode. Phone and c.w. are separate and should be scored separately.

Exchange: RS(T), Zip-Code as it appears on station license, and state, province or country. (DX stations use 00050.)

Scoring: Based on the last two digits in the Zip-Code worked. (*i.e.*: 23518 is worth 18 points) Multiplier of one for each state worked, plus 1 for the first DX contact. (max. of 51) KH6 and KL7 are states but may be counted for the first DX contact.

Final Score: Total of all Zip points × the state plus DX multiplier.

*14 Sherwood Road, Stamford, Conn. 06905.

Frequencies: C.W.—60 kHz up from each band edge. Phone—3900, 7225, 14275, 21350, 28550. Novice—3710, 7110, 21110, 28110.

Awards: Highest score in each call area and overall winner, both phone and c.w. Also overall DX winner on each continent and for the top Novice.

Mailing deadline January 30th to: SEVWA Zip-Code Contest, P.O. Box 14411, Norfolk, Virginia 23518.

YL—DX to North America Contest

C.W.: Jan. 8-9 Phone: Jan. 29-30
Starts: 1800 GMT Wednesday
Ends: 1800 GMT Thursday

YL's on the North American continent, US states and Canadian provinces, will be working the DX YL's (inc. KH6 and KL7) in this one. Alaska however is limited to working the Eastern Canadian provinces and may not contact stations in VE5 thru VE8, but may work Hawaii. (*Gets rather complicated. Ed.*)

Phone and c.w. are separate contests and require separate logs. The same station may be worked on each band for QSO credit, net contacts are not permitted and only QSO's with other YL's are valid.

Exchange: QSO no., RS(T) and QTH. State for W/K, province for VE and country for DX.

Scoring: One point for each QSO. North American stations will count DX countries as their multiplier. DX stations, US states and VE provinces. There is a power multiplier of 1.25 if power input is 150 watts or less. (300 p.e.p. on s.s.b.)

Final Score: QSO points × multiplier × power multiplier if any.

Awards: Trophies to 1st place c.w. and phone winners, both DX and North America. Plaques to highest combined scores for both and certificates to second and third place winners.

Submit separate logs for each section and a signed declaration no later than February 6th. They must be received before Feb. 21st so overseas entries should use air mail.

Logs: Myrtle Cunningham, WA6ISY, 1105 E. Acacia Ave., El Sugundo, CA 90245.

YU 80 Meter C.W. DX Contest

Starts: 2100 GMT Saturday, January 11
Ends: 2100 GMT Sunday, January 12

The YU DX Club organized this one to stimulate activity on 80 c.w.

Exchange: RST plus QSO number. (001)

Scoring: Contacts between stations in the same country 1 point. With other countries on the same continent 2 points. With countries on other continents 5 points. Contacts with YU stations 10 points.

Multiplier: One for each DXCC country, including own, and each YU prefix worked.

Final Score: Sum of QSO points × sum of DX countries and YU prefixes worked. (Entries may be single or multi-operator.)

Warren Croke, WA4DWR proudly displays the Ted Thorpe, ZL2AWJ Memorial Trophy, won by station W4IZ/KV4 in the 1972 CQ WPX SSB Contest. The award was donated by Don Miller, W9WNV for the world high score in the multi-operator, single transmitter category. Operators on the winning team were K4BBF, W4DQD, W4PJD and WA4DWR.

Awards: Certificates to top scorers in each country, with 2nd and 3rd place awards where justified. (Call areas in W/K, VE, PY, VK, ZL, JA, UA9 & UAØ will be considered as separate areas for awards.) There are also Trophies for continental leaders.

Include a summary sheet and the usual signed declaration. Check log for duplicate QSO's. Taking credit for dupes in excess of 3% of the total made means disqualifiication.

Mailing deadline is March 15th to: YU DX Club SRJ, P.O. Box 48, 11001 Belgrade, Yugoslavia.

DL QRP C.W. Contest

Starts: 1800 GMT Saturday, January 11
Ends: 1500 GMT Sunday, January 12

The DL Activity Group runs two of these QRP Contests each year, July and January.

Power input is limited to 10 watts or less, single operator and c.w. only. QRO stations may participate but only contacts with QRP stations are valid. Limit your operation to 15 hours, the 6 hours rest period may be taken in two parts.

Contacts may be made on 3.5, 7, 14, 21 and 1.8 or 28 mHz, with any station QRP or not.

Exchange: RST plus QSO no. and power input. Add "x" if transmitter is crystal controlled. (ie: 579001/8x) Stations using more than 10 watts use QRO instead of power number.

Scoring: Contacts with stations in same country 1 point, other countries on same continent

2 points, DX on other continents 3 points. If QSO is with another QRP station add 3 more points. (4 to 6 pts) There are also "handicap" QSO points if your power is less than 3 watts or you are xtal control. Additional points if station worked also meets above requirements. (*Much too complicated, suggest you let DJ7ST figure out that part of score. Ed.*)

Multiplier: Each DXCC country, 1 if on own continent, 2 if on other continents. Call areas in JA, PY, VE, VK, W/K, ZS will be considered as separate multipliers.

Final Score: Total QSO points × country multiplier from each band.

Use separate log for each band and a summary sheet showing the scoring, time of rest period equipment description. Plus usual signed declaration.

Mailing deadline is February 15th to: Hartmut Weber, DJ7ST, D-3201 Holle, Kleine Ohe 5, West Germany.

Giant RTTY Flash Contest

1500-2300 GMT Saturday, January 18
0700-1500 GMT Sunday, January 26

This is the 7th RTTY contest sponsored by *CQ Elettronica* magazine of Italy, called Flash because of the short two periods of operation.

All bands may be used, 3.5 thru 28 mHz, in that portion of the bands used by RTTY stations. The same station may be contacted on each band for exchange points and multiplier credit.

Exchange: Call, RST and CPR Zone.

Scoring: Contacts with stations in the same Zone 2 points. With stations outside one's own Zone, according to value in the CPR exchange point table.

Multiplier: Each DXCC country and W/K and VE call areas worked on each band.

Final Score: Total exchange points × total multiplier × number of QSOs. (There is also a handicap of 2% to 8% deducted from the final score based on the position achieved in former contests.)

Awards: Gold medal for 1st place, Silver for 2nd and Bronze for 3rd. The 4th to 6th place winners will receive a years subscription to *CQ Elettronica,* 7th to 10th place a 6 month's subscription.

Points and position achieved in this contest will be included for the World RTTY Championship for 1974.

The contest is also open to s.w.l RTTYers with the same scoring rules.

Logs must be received no later than Feb. 28th and go to: Prof. Franco Fanti, via Dallolio n 19, 40139 Bologna, Italy.

CQ WW DX 160 Contest

Starts: 2200 GMT Friday, January 24
Ends: 1600 GMT Sunday, January 26

Rules same as in previous years. This is a c.w. only contest, no c.w. to phone or cross bands contacts will be allowed.

Exchange: RST plus a three figure QSO number starting with 001, and your state or VE province. It is not necessary for DX to send their QTH, the prefix will identify them.

Scoring: For W/VE/VO, 2 points per QSO with other W/VE/VO stations. All DX contacts are worth 10 QSO points. (DXCC country list)

For all other countries, 2 points per QSO with stations in same country, 5 points with stations in other countries. Except for contacts with W/VE/VO which count 10 points.

Multiplier: For all stations. A multiplier of one (1) for each US state, Canadian province and DX country worked. (KH6 and KL7 are considered DX, the District of Columbia same as Maryland. And remember that VE1 is divided into 3 provinces, New Brunswick, Nova Scotia and Prince Edward Island. VO1 and VO2 are separate.)

Final Score: Total QSO points multiplied by the sum of the multiplier.

Disqualification: Violation of the rules and regulations pertaining to amateur radio in the country of the contestant, or the rules of the contest, or unsportmanship conduct, or taking credit for excessive duplicate contacts will be deemed sufficient cause for disqualification. Decision of the Committee is final.

Awards: Certificates to the top scorers in each state, VE province and DX country, additional awards if the score or participation warrants. A Plaque will be awarded by *CQ* to the highest scoring single operator station.

Log sheets and United States Regulations for 160 may be obtained from *CQ* by sending a large s.a.s.e. with sufficient postage.

Mailing deadline for contest logs is February 28th to: *CQ* 160 Contest, 14 Vanderventer Ave., Port Washington, L.I., N.Y. 11050.

Editor's Notes

If you have not already sent in your Phone log for the recent *CQ* WW Contest you had better get it in the mail as soon as possible.

A late ARRL Bulletin advises that the 1975 ARRL DX Contest will have several rules modifications. The most important being that single operator stations will now be able to compete in one of three categories. All band, High band (20-15-10) Low band (160-80-40). A very noteworthy improvement, one I am sure will be welcome by the contest fraternity. Now if we can have the contest period cut down to one week-end for each section we would just about make everybody happy.

May the Holiday Season be a very happy one for you and yours and that you will receive many Blessings during the coming year.

73 for now, Frank, W1WY

THE awards PROGRAM

BY ED HOPPER,* W2GT

USA-CA HONOR ROLL

2000		500			
WA1KMP	208	W1UYL	1012	K7AHO	1015
1000		WA5ZKE	1013	W1SBU	1016
W1SBU	337	WA3TLS	1014		

THE "Story of the Month" for December as told by "Kib" is:

James K. Ramsey, WA4ULL

(All Counties #72, 3-2-72)

"Saw daylight September 26, 1913. Have been in textiles most of my life, electronics is my hobby and has been since I was a small boy.

"My amateur ticket was received in 1964 and I was introduced to County Hunting by Roger, WB2WZE. On March 11th, 1969 I was playing around on 20 meters and when I called QRZ, I think about 50 fellows yelled out, "you are on a busy frequency". Roger was mobile at the time and asked what County I was in, and if I would run it on the Net. I put out Aiken County, S.C. and had about 30 contacts, some with those who are 3079ers now. Boy was I scared, but I survived it all. *(Note by Ed: Reminds me of the fist time I checked into the Net—what a mess I made of it—WOW!)*.

"I got so enthused about County Hunting that I bought a mobile rig, and wow, made 'em all by March 1972.

"I would like to thank *all* those who gave me the many Counties and also the NCS stations who were very patient with me. The stations are so numerous, but I would like to mention some, such as WAØWOB, WØSJE, WØYLN, W4YWX, WB4FBS and I can't leave out Danny, K8DCR who gave me my last two in Kentucky to finish them all.

"I guess County Hunting gets in the blood like hunting or fishing, as I can't stay away from the Nets and trying to work them all again!

"And to climax it all, each County Hunter should go to at least one July 4th Convention and meet so many of the fine gals and fellows who comprise the County Hunter Group—boy that's a real treat!

"Oh yes, to cap it all off, I had the pleasure of meeting Roger, WB2WZE at the Fort Wayne Convention in 1973."

*P.O. Box 73, Rochelle Park, N.J. 07662.

Our records show that "Kib" got USA-CA-500 July 25, 1969. Then on August 4, 1971 he received USA-CA-1000 through USA-CA-3000, with the jack pot being hit on March 2, 1972.

Awards Issued

Marge Doucette, WA1KMP (XYL of WA1-KMQ) acquired— USA-CA-2000, endorsed All A-1.

Stan Swenton, W1SBU won USA-CA-500 and USA-CA-1000, both All A-1.

Mixed USA-CA-500 Awards went to:

Jim Carroll, W1UYL.
Don Banta, WA5ZKE.
Lawrence Barbary II, WA3TLS.
Marten Martenson, K7AHO.

Awards

The Lee William Cook, WA8WNK/DL5LC Certificate: Although the foto of this award was on page 63 of August '74 *CQ*, some might have missed the rules which were in the "Story of the Month" and next to the foto on page 63.

Space Net Award: Although the foto of this award did appear on page 64 of August '74 *CQ*, no rules were listed. This Award will be presented to any and all contacts in excess of 200 miles, additionally it will be presented to check-ins on the new Space Net, 50.2 mHz weekly on Friday 8:00 P.M. local time. Write to: Mr. A. W. Slapkowski, Director Space Net, WB2MTU, Box 909, Sicklerville, N.J. 08081.

Worked Central America Certificate: Work all 7 Countries, TG, VP1, YS, YN, TI, HR, and HP (KZ5). Send list and $1.00 to HC1TH/K5ODZ, 4805 Willowbend Blvd., Houston, Texas 77035.

G P CW Award: Sponsored by the Beach Group of CW—Santos—Brazil, the GPCW Award is

[*Continued on page 69*]

Short wave listener county hunters also like special auto license plates, Fred, WDX2OBU, got SWL-73.

SURPLUS sidelights

BY GORDON ELIOT WHITE*

THE Collins AN/ARN-14 navigation receiver has had a long and honorable career in the U.S. Air Force, and is now being retired from service. I have seen quite a few of these units in surplus, and at prices which indicate that they are being sold more to the hobbyists than to, say, foreign air forces.

The AN/ARN-14 was one of the first "omni" navigation receivers, built after World War II to use the VOR system, developed by the Civil Aeronautics Administration late in the War. VOR stands for **V**ery high frequency **O**mni-directional **R**adio range. It replaced the old low frequency Adcock ranges which were dramatized in the old radio shows.

(*Pilot says "we're on the beam!" static crackles, and a faint "dit-dah" is heard.*)

Where the Adcock ranges required the pilot to navigate by listening for a merged tone and gave an "A" or an "N" in Morse for deviating to the left or right, the "omni" range displayed its information on a panel meter, a great advance over listening for the beam tone in a headset. It was v.h.f., which eliminated much interference, and perhaps best, it had 360 "beams" to or from each station, versus the four courses of the Adcock ranges. I well recall being lost near Philadelphia once, on top of a low cloud layer and trying to figure out which of the four range legs I was on. My compass had hung up, and although I flew right over the transmitter, I hadn't the foggiest idea which leg to fly from there.

The basic theory of the omni range is similar to that of a lighthouse, translated into electronics. When the rotating beam passes through North, a second light flashes. By timing the period between the flash and the arrival of the rotating light, a navigator can tell the compass direction to the lighthouse. In the Omni, a directional transmitter rotates a narrow v.h.f. beam at a 30 c.p.s. rate. When it passes through North, a reference signal is transmitted. The receiver computes the phase difference between the two and circuits in the navigation demodulator match the phase shift with a servo-type device which indicates direction when the phase shifts are at zero difference.

A Morse tone superimposed on the signal allows identification of the station by ear, although Omni channels are generally selected by crystal control, rather than by tuneable receivers, and there is little chance for error. Voice signals are also added to the VOR signal, for transmitting weather reports or other airborne communications, so VOR receivers are pretty good general-purpose audio receivers as well as navigation sets.

The AN/ARN-14 consists of an R-540/ARN-14 receiver, ID-249 or ID-250 course indicator, ID-251 control indicator, AT-172 antenna, C-760-B or C-996-A control head, and DY-66B or DY-84 dynamotor.

For amateur use, the receiver and the control head are the only components really required, if an a.c. power supply is to be built. If you have a good stiff 24 v.d.c. power supply, you can use the dynamotor, although the efficiency is so low as to be wasteful of electric power for long-term use, as well as noisy.

The R-540 is a double-conversion superhet covering 108-135.9 mHz. It has 280 channels spaced 100 kHz apart. (This alone makes it obsolete now, with v.h.f. channels spaced 25 kHz apart.)

In aircraft usage, 108.1-111.9 mHz is a "localizer" band, used for airport instrument landings. The 112.0-117.9 mHz band is reserved for the omnirange, 118.0-121.9 mHz is an airport tower band. General en-route airways communications are carried out in the 122.0-135.9 mHz band.

In the late 1950's the military went to a different type of navigation, more useful to tactical combat use, known as TACAN. A portion of the TACAN system, providing a display of distance information not offered in the omni system, has been adapted to civilian aircraft under the designation DME, for **D**istance **M**easuring **E**quipment. TACAN helped obsolete the ARN-14 as more recent gear has offered more performance with less weight.

The antenna input to the R-540 id 52 ohms coax. Audio output is 300 milliwatts into a 500 ohm load.

Sensitivity is better than 3 microvolts for a 6 db signal to noise ratio. Selectivity is only fair by amateur standards; 6 db attenuation outside of a 45 kHz bandwidth. For 160 kHz band, attenuation is 60 db.

Stability is rated at .01% or better, and frequency response, important in the omni navigation system, is within 8 db from 300 c.p.s. to 3500 c.p.s.

The set has automatic volume control, noise limiter, and squelch.

The dynamotor power supply draws 3.25 amps at 26 volts, the dynamotor output is 245 v.d.c. at 240 ma. The 21 tubes and other current drawing components boosts the full power consumption of the set to 5.7 amps at 26 volts, plus another 2.3 amps to operate the channel-switching mechanism.

*1502 Stonewall Rd., Alexandria, Va. 22302.

RECEIVER-TRANSMITTER

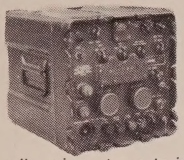

R-392/URR RECEIVER: High performance, rugged 32 bands; 500 kHz thru 32 MHz continuous. Mechanical counter type digital readout to 300 Hz. Separate Megacycles and Kilocycles tuning. Triple conversion lower eight bands, double conversion all others. Built in crystal calibrator, squelch, RF gain, audio gain, antenna tuning, BFO, variable selectivity 8, 4, 2 kHz. Requires 22-30 VDC 3 Amps. Size: 11½ x 14¼ x 11". Wt.: 52 lbs.; Shpg. Wt.: 65 lbs.
USED, REPAIRABLE **$125.00** USED, CHECKED **$195.00**

T-195/GRC-19 TRANSMITTER: 1.5-20 MHz, 10 Bands. Freq. stability 0.03% plus 1000Hz. Manual or automatic tuning. CW, voice, or FSK operation. Power output: 50 Ohm antenna; 1.5-12 MHz 100 watts, 12-16 MHz 90 watts. 16-20 MHz 80 watts. Input voltage required: 22-30 VDC 42 Amps maximum, standby 9 amps. Size: 11½ x 14¼ x 22". Wt.: 122 lbs.; Shpg. Wt.: 150 lbs. Price: Used - Complete Repairable: **$89.50**

MT-851 MOUNTING BASE for R-392 & T-195. Shpg. Wt.: 60 lbs. **$10.00**

CX-1599 CABLE, connects R-392 to T-195 — 10" length: $6.95. BATTERY CABLE for T-195 w/Plug: $4.95. T-195 Maint. MANUAL: **$7.50**., AN/GRC-19 Manual: **$8.50**.

COMBINATION OFFER: Repairable R-392, T-195, MT-851, CX-1599, T-195 Bat. Cable: Spec. Price, com. **$200.00**

All Prices FOB, Lima, Oh. Send for Free Catalog. Dept. CQ

FAIR RADIO SALES
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

The first intermediate frequency amplifier is variable from 19.45 mHz to 21.35 mHz, while the second i.f. is a fixed 3.15 mHz.

Obviously the ARN-14 is useful for monitoring aircraft frequencies, even, with a bit of re-tuning, for picking up f.m. broadcasting, but it should lend itself to conversion to 2 meters, although a point-by-point conversion is rather complex, and too lengthy to go into in this column. For someone interested in learning more about aircraft navigation systems, the ARN-14, with its localizer, omni, and phase localizer systems, is a pretty inexpensive training aid.

Although we cannot re-print the diagram here, I have the original, and will make Xerox copies at $1.00 each, postpaid. ■

FREE CATALOG
CRAMMED WITH GOV'T SURPLUS ELECTRONIC GEAR WRITE TODAY!

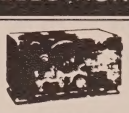

BC-348 RADIO RECEIVER
200-500 Kc & 1.5 - 18 Mc. 8-Tube 6-Band Communications Receiver, Excellent Used, with tubes and Dynamotor. Checked out. $58.50

BC-342 RADIO RECEIVER with AC Power Supply. Checked $69.50

MILITARY RECEIVER TRANSMITTER

Receiver R-392 URR
Used, clean, reparable $125.00
Transmitter T-195-GRC-19
Used, clean, reparable $50.00
SCHEMATICS INCLUDED

BRAND NEW **BC-645 TRANSCEIVER**
EASILY CONVERTED FOR 420MC OPERATION
This equipment originally cost over $1000. You get all in original factory carton.

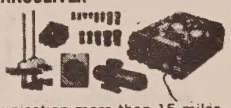

Dependable Two Way Communication more than 15 miles.
"SPECIAL PACKAGE OFFER" $26.95
TRANSCEIVER ONLY. $15.95

LOW IMPEDANCE HEADSET, New with Plug. Reg ..... $12.50 ..... $1.59

TERMS: F.O.B. NYC. 25% deposit with order, balance COD or remittance in full. MINIMUM ORDER $5.00. Subject to prior sale and price change

G & G RADIO ELECTRONICS COMPANY
45 Warren St., Dept. Q-D, New York, N.Y. 10007/Ph(212)267-4605

Cash for any Collins military or commercial equipment or parts, especially 618 T Tranceivers. 490 T antenna couplers. AN/ARC-102. AN/ARC-94.

CASH

AN/MRC-95. SPACE ELECTRONICS CO., 76 Brookside Drive, Upper Saddle River, N.J. 07458 (201) 327-7640

WE PAY HIGHEST CASH PRICE FOR ELECTRON TUBES & SEMICONDUCTORS
IMMEDIATE PAYMENT ON UNUSED TUBES
H & L ASSOCIATES
ELIZABETHPORT INDUSTRIAL PARK
ELIZABETH, NEW JERSEY 07206
(201) 351-4200

Awards [*from page 67*]

issued to amateurs of any country who send proof of contacts with 3 different members. Contacts must have been made after November 5, 1973. All authorized amateur bands can be used, but only c.w. (A-1), with a minimum report of 3-3-8. Applications should include log data anthenticated by a recognized Amateur Radio Association/Club and be sent to: Grupo Praiano De CW—GPCW, P.O. Box 1319, Santos, 11.100 S.P., Brazil. To cover postage 5 IRCs should also be enclosed. Members are: PY2BBO; PY2BKT; PY2CE; PY2CJW; PY2-CZL; PY2EQR; PY2FNE; PY2FPE and PY2TT.

Notes

I was just enjoying looking through my foto Albums of my *many* County Hunter *friends,* and wish I could drop each and every one of you a thank-you note, but you know that is impossible. But may I please thank Bertha, WA4-BMC for *all* her kind help and cooperation?

For special MARAC information, QSL data, ICHN data, etc. . . . request same from Bertha Eggert, P.O. Box 6811. South Boro Station, West Palm Beach, Florida 33405 and be sure to include a legal sized self addressed envelope with 30¢ postage on it.

Merry Christmas to you all, hope Santa is good to you all. Write and tell me, How was your month (Year)? 73, Ed., W2GT.

CQ WPX Contest Results [*from page 37*]

UK5ICD	228,256	564	224
UK4HBB	201,587	526	199
UK3AAY	197,800	610	215
UK3WAC	182,208	584	192
UK6AAJ	159,642	467	181
UK2WWW	**154,755**	**533**	**181**
UK1CID	152,609	657	191
UK6LAA	132,060	504	186
UK2WAF	120,624	436	168
UK6LEW	118,736	423	164
UK2PAT	110,408	414	148
UK2GAZ	109,324	447	151
UK2PAO	104,682	404	146
UK5ZAI	97,474	352	163
UK2PAA	26,840	184	88
UK5VAA	13,328	105	68
UK3XAM	5,202	70	51
UK5UAM	2,160	40	27

MULTI-OPERATOR
Multi-Transmitter

CV2T	**2,859,213**	**2803**	**357**
SV1GA/5B4	**2,819,945**	**2381**	**359**
SK5AL	**1,031,916**	**1502**	**339**
JD1YAH	**678,679**	**2708**	**173**
W5NOP/5	**279,720**	**540**	**210**
'A?YEF	**217,434**	**509**	**167**
WB6JOD	**132,080**	**432**	**127**
W9ZTD	**20,145**	**157**	**79**

Our thanks to the following stations who submitted their logs for checking purposes: DK5OS, OH2BOZ, OH5YX, SM1CXE, SP1AGE, SP5JB, SP6DXB, UA1WBG, UA3VAQ, UA3XAW, UA6GL, UB5WAD, UK2WAT, UK3ABX, UK3MAX, UK4FAA, UK4LAC, UK4NAA, UK5IBM, UK5MAZ, UK5MBG, UK5QAV, UK6LAZ, UK6LDN, UT5HP, UT5HT, YO3JU, 9J2EP.

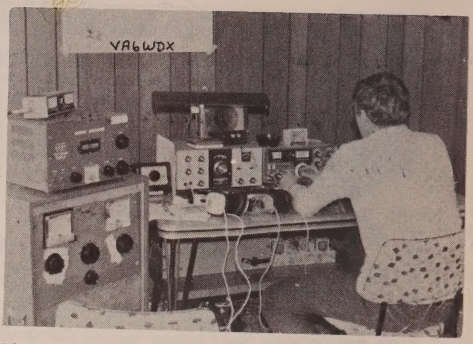

This is the operating position at VA6WDX. The Wizard Lake DX Club House is located 40 miles from Edmonton, Alberta, Canada. Due to the 4-ft. deep snow and the closest road being 1½ miles away VE6AN, VE6GS, and VE6LB had to haul their gear in snowmobiles and found it necessary to use snowshoes. The boys feel it was well worth the effort.

1975 SSB Contest. Request your log forms and summary sheets from the *CQ* office. Please send s.a.s.e. or IRC's. The next one coming up is the 29th and 30th of March. Remember it doesn't take a giant score to win a certificate. This is an excellent reason for submitting your logs, regardless of scores.

Hope all you DX stations will tune the US phone parts of the 40 and 80 meter bands, as well as the General portions of all the bands for those extra multipliers and points.

Thanks to all who helped make this 17th annual event a success. It is impossible to acknowledge everyone behind the scene, however, a group that is sometimes taken for granted are the QSL Managers who make DX logs available to us. Thanks for the special assistance provided by Willy, LX1BW; Joe, DL6QX; Bob, W1YRC; Irv, K5YIN; Rubin, WA6AHF; and last but not least, Mr. *CQ* Contest, Frank W1WY.

Hope to work ya in the next one.

73 Bernie, W8IMZ

STATION OPERATORS

Multi-Operator Single Transmitter

CR4BC & CR4BS. **DJØEK** & DJØBA. **DK4OV:** DJ4GO, DJ6WO, DK2HP, DL3LU. **DKØSD:** DK3GI, DK8NH. **EI1AA:** EI2BB, EI2CA, EI2CL, EI2CN, EI7CC, EI8CC. **G3RCV:** G3XMD, G3ZAY, G3ZEN, G3ZRJ, G4BAL, G8GGP, G8HYH. **G4BUE** & G4BUH. **G4DAA:** G3FXB, G3MXJ. G3XBN, G3ZQX. **HA2KMR:** 2 Oprs. **HA5AIR:** HA5CH, HA5CJ, HA5CL, HA5ED, HA7TJ. **HA5KAS:** HA5CE, HA5FZ, H5-304. **HA5KKB:** Club. **HA5KKW:** 2 Oprs. **HA5KMB:** HA5CQ, HA5EO, HA5MB. **HA5KRL:** 2 Oprs. **HA7KLC:** H7-025, H7-054. **HA7KLF:** H7-013, H7-014, H7-045, H7-049. **HA7KLG:** HA7MCH733, H7-015, H7-032, **HA9KOB:** Club. **HG8U:** HA3NS, HA8UD, HA8VT, HA8VY, HA8VZ. **I3BKT** & I3BA, I3GLT, I3SQA, I3VRR. **I6FLD** & I6BQI, I6ICD, I6MRD, I6PLN. **JA1YFG:** JA2WIG, JE1XZL, JG1ILP, JH1FSF, JR1CKM. **JA6YTU:** JA4RIT, JA6AAB, JA6AKT, JA6BPA, JA6BSM, JA6CTN, JA6ERP, JA6ERR, JA6HNZ, JA6JVJ, JA6MDD, JA6MVU, JA6PFZ, JA6QET, JA6RCB, JA6RLM, JA6STS. **JH1YDT:** JH1AGH, JH1BNC, JR1IMM. **K3IVO:** K3TNM, W3DPU, W3VUH, WA3OEJ, WA3TDZ, WB6VGI. **LA1K:** LA1BP, LA1FR, LA2RQ, LA2RR, LA4CQ, LA7DS, LA9KL. **LZ2KPD:** LZ2LQ, LZ2VP & 1 Opr. **OH3AM:** OH1PF, OH2KQ, OH2LU, **OH4RH:** Group. **OH5WJ** & OH5TQ. **OH8RC** & OH8TW, OH8SW. **OK1KPU:** Club. **OK1KUQ:** Club. **OK1KUR:** Club. **OK2KWL:** OK2BNG & group. **OK3KAP:** OK3OGI & group. **OK3KGI:** OK3UE & group. **OK3KTR:** OK3CFK, OK3IAG, OK3TBY, OK3YCA. **PI1ARS:** PAØBBC, PAØHTR, PAØTAS, NL4373. **PJ9JR:** W3ZKH, WA3IAQ. **PS7BDX:** PY7AKW, PY7AOJ, PY7APR, PY7APS, PY7AUR, PY7AZQ, PY7DX, PY7PO, PY7ZAV. **PS7NS:** PY7ARM, PY7NS. **PY2CAB** & PY2DYI, PY2ELV. **SK4EN:** SM4EGS, SM4-3637. **SK6BA:** SM6CKU, SM6DHU, SM6EVE, SM6FYJ, SM7BZV. **SP2KGJ:** Club. **SP3ZAH: SP3ZAH:** SP3GUI & group. **SP5KOH:** SP5GNG, SP5GNI, SP5-1594. **SP5PWK:** SP5BSV, SP5DZJ & 1 Opr. **SP6KDA:** SP5FSH & group. **SP6PZB:** SP6FAF, SP6-5090. **SP9KRT:** SP9HMF, SP9ZW, SP9-2357. **SP9ZAF:** SP9EWO, SP9EYX. **VA6WDX:** VE6AN, VE6GS, VE6LB. **VP5CW:** W4ORT, W4SME, WB4EYX, WB4IAE. **W6VPZ:** K6HRT, K6KH, W6CFM, WB6WWU. **WØEEE:** WA0RAD, WB4OEM, WB9FSL, WB0GQP, WN0MAT. **WA6GLD** & WA6ISP. **WAØCGV:** WBØHPB & Club. **WB8IAY** & WA8LXW, WA8UUY, WB8BIU. **WM5BIL:** K5YIN, W5BW, WA5EZQ, WA5FDP, WA5FMF, WB5DCY, WB5EHI, WB5HVY & Club. **YU1BCD:** YU1NZV, YU1ODO, YU1ODS, YU1PCF, YU1OBC, YU3-Y. **YU2CBM:** YU?RMG, YU2ROJ, YU?RTW, & 2 Oprs. **YU2CDO:** Club. **ZB2WPX:** ZB2BL, ZB?CF. **ZL2HV:** ZL2AHC, ZL2ARW, ZL2ASO, ZL2AYF, ZL2BBT, ZL?BGL, ZL2BHP, ZL2TNK. **4X4NJ:** 4X4DK, 4Z4HF, 4Z4LF. **9M2CX** & 9M2CJ.

Multi-Operator Multi Transmitter

CV2T: CX1BBL, CX3BH, CX4AAC, CX4CR, CX8BBH, CX9BT. **JA2YEF:** Club. **JD1YAH:** JA3GZN, JA7KAC, JA7MQM, JF1SER, JH3TKM, JR1EUX. **SK5AL:** SM5BUT, SMØDSG, SMØEIE, SMØGM. **SV1GA/5B4:** OD5HC, OH2BH, OH2MM, SV1GA. **W5NOP/5:** K5FVA, W5KKZ, W5NOP, W5UDK, W5WQI, WA5AWF. **W9ZTD** & W9VNE. **WB6JOD:** K6PPZ, K6QJZ, K6YP, W6AD, W6KHS, W6SMW, WA6HCL, WA6SUQ, WA6UPE, WB6CNH, WB6RWU, WB6TKE.

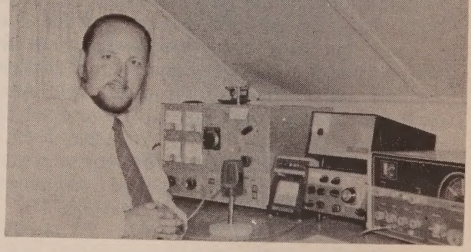

The 10 meter score of CE6EZ was limited only by the amount of activity on that band, because according to Ralf, the band was wide open. He came in second world high.

Electronic Keyer [*from page 31*]

Switches S_1, S_2, and S_3 may be combined into a three pole four position switch with positions OFF, LOCAL, OPERATE, and TUNE. The LED's can either be mounted in 14-pin DIP sockets, or soldered on a piece of Vector Board. The actual enclosure used in the prototype keyer was a large Minibox that had been used in other projects; the keyer can be packaged in a smaller enclosure.

The LM309K voltage regulator should be bolted to the chassis or a heat sink.

Parts Procurement

This was the first TTL project I had tackled, and I had a bit of trouble finding all the parts at a low cost. Hopefully, the following list of parts and suppliers will be helpful:

Resistors, capacitors, transistors, diodes, phone plugs/jacks:
HAL Communications Corp.
Box 365
Urbana, Illinois 61801

Integrated Circuits, LED's, rectifiers, sockets, LM309K:
Poly Paks
Box 942
South Lynnfield, Mass. 01940

Babylon Electronics
P.O. Box J
Carmichael, Calif. 45608

LM309K, IC's:
International Electronics Unlimited
Box 1708
Monterey, Calif. 93940

Radio Shack (local)

Pots, Vectorboard, misc. parts:
Local or national electronics parts distributors

Dual paddle key for use with keyer:
Brown Bros. Mach. Co.
5370 Southwest Avenue
St. Louis, Mo. 63139

Operation

If a dual paddle is used with the keyer, iambic operation can be obtained. A single paddle key may also be used. The volume and tone controls may be set as desired (these controls may either be on the front panel or on the circuit board). As the keyer warms up, the speed of the clock may vary one w.p.m. or so, but after that the display should not vary except when the speed pot is changed.

I have found that using this keyer is much more satisfying than any other key or keyer I have used before, because I can finally see just exactly how fast I am sending. It should be, even more helpful when preparing to pass a new code exam. ■

Propagation [*from page 63*]

South Pacific & New Zealand	12-14 (1) 14-16 (2) 16-18 (1)	10-12 (1) 12-14 (2) 14-17 (3) 17-19 (2) 19-20 (1)	06-07 (1) 07-09 (3) 09-12 (2) 12-15 (1) 15-17 (2) 17-20 (3) 20-21 (2) 21-22 (1) 02-04 (1)	23-01 (1) 01-02 (2) 02-06 (3) 06-07 (2) 07-08 (1) 03-07 (1)*
Australasia	14-15 (1) 15-17 (2) 17-18 (1)	09-11 (1) 13-15 (1) 15-17 (3) 17-19 (2) 19-20 (1)	06-07 (1) 07-08 (2) 08-10 (3) 10-12 (2) 12-18 (1) 18-21 (2) 21-22 (1)	02-04 (1) 04-07 (2) 07-09 (1) 03-06 (1)*
Central America & Northern Countries Of South America	08-10 (1) 10-14 (2) 14-16 (1)	07-08 (1) 08-09 (2) 09-13 (3) 13-16 (4) 16-17 (2) 17-18 (1)	06-07 (2) 07-11 (3) 11-14 (2) 14-16 (3) 16-18 (4) 18-19 (3) 19-20 (2) 20-22 (1) 22-00 (2) 00-06 (1)	18-20 (1) 20-22 (2) 22-03 (3) 03-05 (2) 05-07 (1) 19-21 (1)* 21-01 (2)* 01-04 (1)*
Peru, Bolovia, Paraguay, Brazil, Chile, Argentina, Uruguay	09-11 (1) 11-15 (2) 15-17 (1)	07-08 (1) 08-13 (2) 13-15 (4) 15-16 (3) 16-17 (2) 17-18 (1)	05-06 (1) 06-08 (2) 08-10 (1) 12-14 (1) 14-15 (2) 15-17 (3) 17-19 (4) 19-20 (2) 20-22 (1) 22-00 (2) 00-03 (1)	19-21 (1) 21-02 (2) 02-05 (1) 21-04 (1)*
McMurdo Sound, Antarctica	*Nil*	16-18 (1)	06-07 (1) 07-08 (2) 09-11 (1) 17-18 (1) 18-22 (2) 22-00 (1) 00-02 (2) 02-03 (1)	22-05 (1)

Time Zone PST (24-Hour Time)

WESTERN USA TO:

	10 Meters	*15 Meters*	*20 Meters*	*40/80 Meters*
Western & Southern Europe & North Africa	08-09 (1)	07-08 (1) 08-10 (2) 10-11 (1)	06-07 (1) 07-09 (2) 09-10 (1) 10-12 (2) 12-14 (1) 23-01 (1)	18-20 (1) 20-23 (2) 23-01 (1) 19-23 (1)*
Central & Northern Europe & European USSR	*Nil*	07-09 (1)	06-07 (1) 07-10 (2) 10-13 (1) 23-01 (1)	17-00 (1) 19-23 (1)*
Eastern Mediterranean & Middle East	*Nil*	07-10 (1)	06-07 (1) 07-09 (2) 09-11 (1) 11-12 (2) 12-13 (1) 21-23 (1)	06-08 (1) 18-21 (1)
West Africa	09-12 (1)	08-09 (1) 09-10 (2) 10-12 (3) 12-13 (2) 13-14 (1)	07-10 (1) 10-13 (2) 13-16 (3) 16-18 (2) 18-19 (1)	18-22 (1) 20-22 (1)*
East & Central Africa	*Nil*	09-11 (1)	08-10 (1) 13-16 (1) 21-23 (1)	06-08 (1) 18-20 (1)
South Africa	08-11 (1)	08-10 (1) 10-13 (2) 13-14 (1)	07-11 (1) 11-13 (2) 13-16 (3) 16-18 (2) 18-19 (1) 23-01 (1)	18-20 (1)

New INTERNATIONAL broadband amplifier

MODEL 150-299

14 db gain—10 to 1,000 MHz

International's inline amplifier provides 14 db gain flat within 1 db over a range of 10 to 1,000 MHz. Impedance 50 phms. Requires 20 VDC @ 50 ma. For increased gain additional amplifier may be added. Uses BNC type terminals.

SPECIFICATIONS

Range	10 to 1,000 MHz
Impedance	50 ohms
DC Input*	20 VDC 50 ma
Gain* *	14 db
Flatness	±1 db (Ref. 500 MHz)
Operating Temperature	−25 to +70° C
Noise Figure	9 db
VSWR Output	2.0
Output capability for −60 db near intermodulation distortion	100 MV

*Will operate 12 to 24 VDC with some loss characteristics.
**May cascade for additional gain with consideration of noise and flatness.

Price **$40.00** plus postage
Write for complete catalog.

INTERNATIONAL
CRYSTAL MFG. CO., INC.
10 North Lee
Oklahoma City, Oklahoma 73102
405 236-3741

Central & South Asia	*Nil*	17-19 (1)	08-10 (1) 17-19 (1) 19-20 (2) 20-21 (1)	05-07 (1) 18-20 (1)
Southeast Asia	15-17 (1)	15-16 (1) 16-17 (2) 17-18 (1)	07-09 (1) 09-11 (2) 11-16 (1) 16-19 (2) 19-20 (1)	03-08 (1)
Far East	15-17 (1)	14-15 (1) 15-16 (2) 16-17 (3) 17-18 (2) 18-19 (1)	08-10 (1) 13-14 (2) 14-15 (2) 15-18 (3) 18-19 (2) 19-20 (1)	00-01 (1) 01-03 (2) 03-06 (3) 06-08 (2) 08-10 (1) 02-08 (1)*
South Pacific & New Zealand	12-14 (1) 14-16 (2) 16-17 (1)	10-12 (1) 12-14 (2) 14-16 (4) 16-17 (3) 17-18 (2) 18-19 (1)	07-08 (1) 08-10 (2) 10-15 (1) 15-16 (2) 16-18 (4) 18-19 (3) 19-20 (2) 20-22 (1) 03-05 (1)	22-00 (1) 00-03 (2) 03-06 (3) 06-07 (2) 07-08 (1) 00-03 (1)* 03-06 (2)* 06-07 (1)*
Australasia	14-17 (1)	08-12 (1) 12-15 (2) 15-17 (3) 17-18 (2) 18-19 (1)	07-08 (1) 08-10 (3) 10-12 (2) 12-17 (1) 17-18 (2) 18-20 (3) 20-21 (2) 21-22 (1)	01-03 (1) 03-06 (2) 06-08 (1) 01-03 (1)* 03-06 (2)* 06-07 (1)*
Central America & Northern Countries of South America	09-11 (1) 11-14 (2) 14-16 (1)	07-08 (1) 08-12 (3) 12-14 (4) 14-15 (3) 15-16 (2) 16-17 (1)	06-07 (2) 07-09 (3) 09-13 (2) 13-15 (3) 15-17 (4) 17-18 (3) 18-20 (2) 20-22 (1) 22-00 (2) 00-06 (1)	18-20 (1) 20-22 (2) 22-02 (3) 02-04 (2) 04-05 (1) 19-21 (1)* 21-01 (2)* 01-04 (1)*
Peru, Bolivia, Paraguay, Brazil, Chile, Argentina & Uruguay	10-12 (1) 12-14 (2) 14-15 (1)	08-10 (1) 10-12 (2) 12-13 (3) 13-15 (4) 15-16 (2) 16-17 (1)	08-14 (1) 14-15 (2) 15-16 (3) 16-18 (4) 18-19 (3) 19-20 (2) 20-22 (1) 22-00 (2) 00-06 (1) 06-08 (2)	20-22 (1) 22-01 (2) 01-04 (1) 22-02 (1)*
McMurdo Sound, Antarctica	*Nil*	12-15 (1) 15-16 (2) 16-18 (1)	16-18 (1) 18-19 (2) 19-22 (3) 22-01 (2) 01-03 (1) 07-09 (1)	23-05 (1)

Math's Notes [*from page 45*]

calibration oscillator to WWV. As the beat note decreases in frequency the speed at which the two LED's switch on during positive and negative half cycles of the beat frequency gets slower and slower until one can easily see the individual LED's go on and off. When both LEDs stay off, the receiver is at zero beat! This same application could also be used as a visual c.w. indicator for those so inclined.

In conclusion, the LED is an extremely unique and useful device, quite easy to work with and may solve some of those "unsolvable problems" we all seem to have from time to time.

At this time I would like to wish all of my readers a very happy, healthy, and prosperous New Year and of course a very Merry Christmas. 73, Irv, WA2NDM

SUBSCRIBE TODAY

Don't settle for second. Get the best...

hy-gain Antennas!

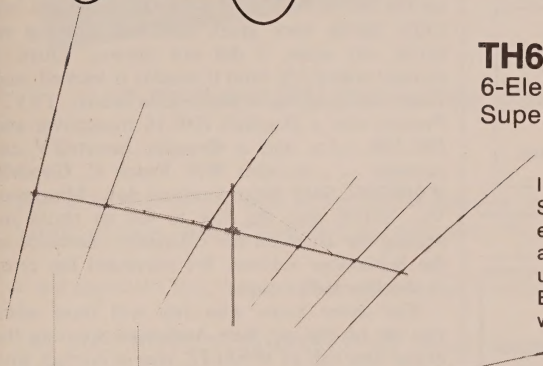

TH6DXX

6-Element Super Thunderbird DX
Superior Performance TriBander!

Impressive coverage 10-15-20 meters. Separate, improved Hy-Q traps for each band...SWR less than 1.5:1 on all bands. Takes maximum legal power, up to 1 kw AM, 2 kw PEP. Exclusive Beta Match. Factory pre-tuned. Feeds with 52 ohm coax.

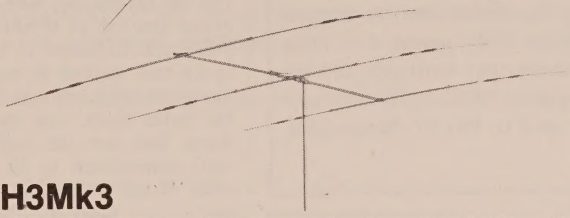

TH3Mk3

3-Element Super Thunderbird Popular TriBand Beam Improved!

Outstanding performance 10-15-20 meters at reasonable cost. Separate, matched Hy-Q traps for each band. Exclusive Beta Match for tapered impedance, DC ground. SWR less than 2:1 at resonance. Accepts maximum legal power and feeds with 52 ohm coax.

18AVT/WB

The Great Wide Band Vertical Super Performer 80 through 10 meters!

Superb omnidirectional capabilities. Automatic band switching. Beefed-up Hy-Q traps. Top loading coil. True 1/4 wave resonance on all bands. SWR 2:1 or less at band edges. Outstanding low radiation pattern. Entirely self-supporting.

18 HT

Incomparable Hy-Tower Finest Multiband on the Market!

Automatic band selection 80 through 10 meters. Unique stub decoupling system isolates electrical 1/4 wavelengths for each band. Takes maximum legal power. Feeds with 52 ohm coax. 24' tower is entirely self-supporting, virtually indestructible. Requires only 4 sq. ft. for installation.

GECC revolving credit available
Use your BankAmericard or Master Charge

ELECTRONIC DISTRIBUTORS, INC.

• Communications specialists for over 35 years.

1960 Peck Street, Muskegon, MI 49441 616/726-3196 Telex 228-411

WORLD QSL BUREAU

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next country, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 6¢ each.

5200 Panama Ave., Richmond, CA USA 94804

HW-12, 22, 32 OWNERS

(Including A, E, & C series): Convert your present rig to an 80-40-20 meter s.s.b./c.w. transceiver. Complete step by step conversion manual only $4.00, postpaid.

R. CHRISTIE

Box A, CQ Magazine, 14 Vanderventer Ave., Port Washington, New York, 11050

SUBSCRIBE TODAY

Be a Part of It All

Join AMSAT—The Radio Amateur Satellite Corporation. Your $5.00 annual dues bring a handsome membership certificate and the quarterly publication "AMSAT Newsletter." Write AMSAT at P.O. Box 27, Washington, D.C. 20044.

EARSPLITTER

"The distinctive Warning Signal"

$35.95

Introductory Price 1.5 pounds Size 6" x 5"

ELECTRONIC SIREN ES-900

Now being used by:

Vol. firemen, aux. police, boats, fire alarm systems, burglar alarm systems, etc.

The EARSPLITTER ES-900 emits a loud, attention-getting, penetrating, rapid yelping sound, just like the new sirens used on the latest police, fire, and emergency vehicles.

No moving parts to wear out or rust!

- The tone varies from low to high automatically.
- Draws less than 1 ampere from battery.
- Will operate on (2) 6 volt lantern batteries.
- Optimum voltage is 13 volts D. C.
- Electronic and aluminum trumpet horns are built into one integral unit which is totally waterproof.

When YOU need attention..... get EARSPLITTER

Also available as car theft alarm $39.95

Send Check or M.O. to

HOUSE OF POWER

P. O. Box 306 Merrick, N. Y. 11566

Novice Shack [*from page 44*]

DXing for Novices because KZ5VV took a real amateur interest in beginners." Thanks also to KZ5EJ, IT, and OD for administering the tests and helping in other ways . . . **Preston Shute, WN4JTP,** 232 Pinewood Dr., Holiday, Fla. 33589 reports, "The first or second night I got on the air, a "VE" and a "TVV" answered my CQ's. Being very green and not wanting to break any rules, I did not answer. Later, I learned where VE land (Canada) is located, and I am still kicking myself. How about TVV?" Preston uses a Heathkit HW-16 transceiver and HG-10B v.f.o. and a 40-meter inverted-V antenna . . . Another WN, **Frank C. Goodell, WN4GFG,** 9405 Westmoreland Ave., Manassas, Va., 22110, was the first to tell us about inverting the equation for capacitive reactance in the September column. We corrected the error in the November copy.

You never know who you will raise when you get on the air. **Ken Anderson,** sporting the brand new call of **WN5LIT,** was in contact with WN5LQI. Unknown to Ken, a small green grass snake had worked its way up the table leg and along side of Ken's arm. Ken's wife walked into the radio shack, saw the snake and screamed. Then, Ken saw the visitor and his code speed went immediately to 30 w.p.m. At least, that is what **Hugh, WB5GLZ**—an honest Texan—reports . . . **Gary L. Feldman, WN2UGO,** 28 Pine Tree Dr., Poughkeepsie, N.Y. 12603, represents the majority view in our informal poll by voting for more items about what makes "Hamming" so much fun and less fundamental theory in the NOVICE SHACK. He says that there are lots of books on theory but only one NOVICE SHACK. He cites examples, which I hope happened to him: the thrill of working a rare DX station that you had worked previously and having the operator call you by name; working an amateur stationed on a Navy base in Maine and working the same amateur a few months later on board a ship on a training mission off Puerto Rico; or going camping and setting up your station, powered by a 12-volt battery, and feeding a make-shift antenna in a rain storm and working a rare DX station in a "pile up." In six months, Gary has worked 45 states and 30 countries using an FT-101B transceiver. For antennas, he uses a CB vertical, 5/8-wave ground plane on 15 meters and a Murch dipole on 40 and 80 meters. And when conditions get better, look out!

As we come to the bottom of the page again, we remind you that the NOVICE SHACK is your column. Send your "News and Views," comments and suggestions to the address on the first page. And you are invited to submit a sharp photograph in our monthly Novice Shack Photo Contest. 73, Herb, W9EGQ

Announcing ELECTRONIC FLEAMARKET

a new monthly publication from the publisher of CQ

THE ELECTRONIC FLEAMARKET is a complete new shopping source for anyone interested in buying, selling or swapping used electronic equipment of any kind.

It will appeal to CBers, hams, experimenters and professionals.

THE ELECTRONIC FLEAMARKET will contain thousands of classified ads on transmitters, receivers, transceivers, test equipment, amplifiers, antennas, towers, stereo equipment, etc.

It will also contain ads from retailers, wholesalers, and manufacturers offering used equipment for sale.

Classified ads will be published free of charge to all regular subscribers of CQ. Free ads will be limited exclusively to individuals. Commercial ads may be ordered at a rate of 25 cents per word, with a $3 minimum. Non-commercial ads for non-subscribers are 10 cents per word, $1 minimum. THE ELECTRONIC FLEAMARKET will be available on a paid subscription basis only at a cost of $10 per year. All issues will be mailed by first class mail on the tenth of each month. The first issue will be mailed on February 10, 1975.

SPECIAL CHARTER SUBSCRIPTION rates available to CQ subscribers at a saving of 20%. Use the special sub blank below and get your first year's subscription for just $8. But don't delay. This is a pre-publication offer and subject to cancellation without notice.

CHARTER SUBSCRIPTION $8.00

ELECTRONIC FLEAMARKET
14 Vanderventer Avenue
Port Washington, New York 11o50 11050

Please enroll me as a charter subscriber to
"ELECTRONIC FLEAMARKET" at the rate of **$8.00**

Name _____

Address _____

City _____ State _____ Zip _____

ALUMA TOWERS

LOW PRICED

Made in Aluminum

★ TELESCOPING
★ WALL MOUNTED
★ GUYED

FOR:

TV — CB — HAM
MARINE — MOBILE
RADIO TELEPHONE
COMMERCIAL

Towers to 100 feet. Specials designed & made. See dealer or call.

ALUMA DIVISION

FRED FRANKE, INC.

Box 2806Q
Vero Beach, Florida 32960 U.S.A.
Phone (305)-567-3415
Cable: FREDFRANKE VEROBEACH FL.
Some Territories Available

ARR-52 VHF RECEIVER

As described in the Surplus Sidelights Column (page 58 Oct. issue). Easily converted to 2-meter FM Now set for 163-173 mHz, 16 channels. $19.95 postpaid continental US: Includes schematic diagram and conversion details.

While they last!

$19.95 POSTPAID

EEB is a supplier of used electronic test equipment: H-P, Tektronix, Fluke, G-R, etc. Scopes, Generators, Counters, Power Supplies. We can save your company time and money by offering late model equipment completely reconditioned and guaranteed to meet manufacturer's specifications. Usually 24 hour delivery in USA.

Inquiries welcomed....let us know your needs.

BankAmericard Welcomed

Electronic Equipment Bank, Inc.

516 Mill Street, N.E. Vienna, Virginia 22180
(703) 938-3350

HAM SHOP

Advertising Rates: Non-commercial ads are 10 cents per word including abbreviations and addresses. Commercial and organization ads are 35 cents per word. Minimum charge $1.00. No ad (non-subscriber) will be printed unless accompanied by full remittance.

Closing Date: The 10th day in the third month preceding date of publication. Because the advertisers and equipment contained in Ham Shop have not been investigated, the Publishers of CQ cannot vouch for the merchandise listed therein. Direct all correspondence and ad copy to: **CQ Ham Shop, 14 Vanderventer Ave., Port Washington, New York 11050.**

FOR SALE OR TRADE: (2) 7735A vidicons. You test, make offer. J. Wasiewicz, W2DQC, 229 Sarles Lane, Pleasantville, NY 10570.

LINEAR BUILDERS: Send SASE for Lo-Priced List of HI-power parts. R. Mace, W6RW, 8600 Skyline Drive, Hollywood, CA 90046.

FOR SALE: 50' Rohn Tower. Top Section and one set of guying never even up. $100.00. Tappehorn 2536 Kings Highway, Louisville, KY 40205.

WRITE HAM SENTENCES IN 54 LANGUAGES! K3CHP's DX QSL Guide, $3.95. Joe Mikuckis, 6913 Furman Parkway, Riverdale, MD 20840.

SELL: 3600-0-3600 Xfmr at 1 amp $35, with 110/220 primary. W0AIH. Paul Bittner, 304 W. 17th, Grand Island, NB 68801.

SALE: Galaxy VMh3, AC400 PS, RVI VFO, SC-35 speaker, CAL-35 Calib., F-3 Filter. Complete station excellent condition. $400.00. FM Strickhausen, WA0NLR, 2931 Central Park, Topeka KS 66611.

COLLECTORS OF QST MAGAZINES: 1920 thru May 1967 inclusive. Also various months rare editions, 1915, 1916, 1917 and 1919. Will sell total or part for best offer. R. Horan, 2742 Wabash Dr., NE, Grand Rapids, Michigan 49505. (616) 363-7567.

TRADE: 4x5 Federal foto enlarger with 11x14 adjustable easel, for HW-12A or other Ham Gear. Both in excellent condition. Frentz, K0TQH, Deerwood, MN 56444.

SELL OR TRADE: Have clean 75A4/500 also Johnson Courier linear, needs power transformer and condensers. Want, 312B4, keyer with memories prefer Hallicrafter. Arnold, W6AT, 367 North West, Vacaville, CA 95688.

SELL OR TRADE: HT-220 on 16-76, Drake TR4, NB, RV4, AC4, Mike, Manuals. Both mint. Bell & Howell, Home study Course 162 Lessons & Answers. R. Pohorence, 2334 Regal Court, Lawrenceville, GA 30245.

QSL Cards: Sample, 10 cents. The Print Shop; P.O. Box 353 Lockport, IL 60441.

SELL OR TRADE: Models 14, 15, 19, RTTY and associated power, TD's, etc. Basham, W7TCT, 735 Caves HWY, Cave JCT, OR 97523.

NEW! WORKED CENTRAL AMERICA CERTIFICATE: Work all 7 countries. Send list and $1. HC1TH, 4805 Willowbend Blvd., Houston, TX 77035.

WANTED: Touch Tone Pads. Price? H. Perozzo, W7UD, 8515 37th West, Tacoma, WA 98466.

WANTED: Wireless gear, old radio receivers, Msc. parts, catalogs, etc., regardless of condition, Horvarth 522 Third St., San Rafael, CA 94901.

Purchase your SWAN from AMATEUR ELECTRONIC SUPPLY

300B 80-10m 110vac Transceiver	$519.95
300B with SS-16B Filter installed	589.95
14A 12vdc Convertor for 300B	49.95
700CX 80-10m Transceiver	599.95
700CX with SS-16B Filter installed	669.95
250C 6m Transceiver	499.95
CYGNET 1200X Linear	299.95
Mark II 80-10m Linear	749.95
117XC AC Supply w/spkr. in cabinet	124.95
230XC 230v AC Supply, spkr., cabinet	134.95
14-117 12v DC Supply w/cable	149.95
14C 12v DC Module/cable ONLY	84.95
117X Basic AC Supply - w/117v cord	79.95
510X MARS Oscillator - less crystals	54.95
508 Full coverage VFO	189.95
VX-2 Plug-in VOX	44.95
FP-1 Phone Patch	54.95
MTK Mobile Mounting Kit	9.95
GMTK "Gimbel type" mobile mtg. kit	5.20
SS-16B Custom Crystal Lattice Filter	89.95
600T 80-10m Transmitter, 600w	589.95
600RC CUSTOM Receiver	545.95
600RC CUSTOM Receiver/SS-16B	599.95
600S Speaker for 600R	24.95
600SP Deluxe Speaker (w/phone patch)	69.95
600 Hz CW Filter for 600R	34.50
AM Filter for 600R	44.50
SWAN 444 Desk Mike	35.95
SWAN 404 Hand Mike	24.95
WM-1500 Wattmeter	64.95
Solid-State 80-10m Transceivers (12 volt)	
SS-15 15 watt PEP input	$599.95
SS-15 with SS-16B installed	669.95
SS-200A 300 watt PEP input	799.95
SS-200A with SS-16B installed	869.95
Mobile Mounting Kits for SS-15, 200	
SSCMTK "Gimbel type" (under dash)	$ 11.95
SSMTK Hump-mount kit	16.95
PS-10 AC Supply for SS-15	99.95
PS-20 AC Supply for SS-200	159.95
PS-210 220 volt AC supply	109.95
PS-220 220 volt AC supply	169.95
SS-208 External VFO	189.95
610X Crystal-controlled oscillator	54.95
Solid-State Mono-Banders (12 volt)	
MB-40 40m Xcvr, 75w PEP input	$299.95
MB-80 80m Xcvr, 75w PEP input	299.95
MB-40A 40m Xcvr, 160w PEP input	329.95
MB-80A 80m Xcvr, 160w PEP input	329.95
P-1215 AC supply for above MB's	49.95
P-2015 220v AC Supply for MB's	59.95
MBCW CW Monitor for MB's	19.95
Model 45 80-10m Antenna	84.95
Kwik-on Connector	7.95
BMT Bumper Mount	26.95
FM-2XA 2m FM Transceiver	$259.95
AC Supply for above	40.00
FM-1210A 2m FM Transceiver	319.95
AC Supply for above	40.00
Crystals for FM-2XA and 1210A . each	5.00
MD-4 2m Antenna	21.95
TMD Trunk mount for MD-4	9.95
RMD Roof mount for MD-4	5.95

SAVE $70

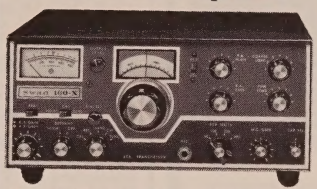

SWAN 160X 160m Xcvr, 1.8 to 2MHz. 1KHz Readout, Switchable pwr. - 50, 100, 200 or 400 watts PEP. Less pwr. supply (117XC)
Reg. $469 NOW ONLY $399

SAVE $50

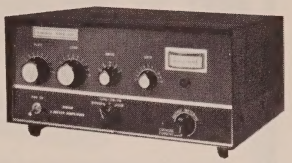

SWAN VHF-150 2m amplifier (143-149MHz). 180 PEP or 150W DC input on CW & FM with 6 to 10w of drive. Built-in AC supply.
Reg. $299 NOW ONLY $249

SAVE $15

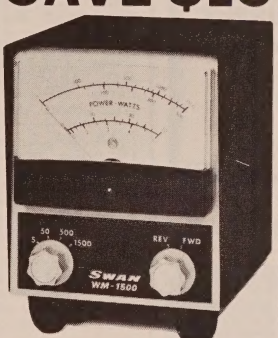

SWAN WM-1500 In-Line Wattmeter 2-30MHz 0 to 5, 50, 500 & 1000 watts.
Reg. $64.95 NOW ONLY $49.95

Now you can use your
SWAN CREDIT CARD
at
AMATEUR ELECTRONIC SUPPLY
to purchase any new Swan equipment

SWAN ELECTRONICS
305 Airport Road Oceanside, CA 92054
Revolving Credit Account Nr. 7388
Issued To: Joe Ham
Address: 599 QSO Lane, Anywhere, USA
Call: W9XYZ
Joe Ham
Signature

NOTE We are able to offer the special price on the WM-1500 due to a large purchase made at the old price

SAVE $30
External VFO for 160X
Reg. $119.95
NOW $89.95

To: AMATEUR ELECTRONIC SUPPLY
4828 W. Fond du Lac Ave, Milwaukee, Wis. 53216

am interested in the following new equipment:

I have the following to trade: (what's your deal?)

Ship me:

I Enclose $_____: I will pay balance (if any):
☐ COD Swan Credit Card ☐ GECC Revolving Charge Plan
☐ Master Charge* ☐ BankAmericard ☐ American Express

Account Number:

Expiration DATE _____ *Master Charge Interbank number _____ (4 digits)

Name:

Address:

City & State:

☐ Send used gear list

AMATEUR ELECTRONIC SUPPLY

4828 West Fond du Lac Ave. Milwaukee, Wis. 53216
Phone (414) 442-4200
HOURS: Mon & Fri 9-9; Tues, Wed & Thurs 9-5:30; Sat 9-3

IMPORTANT! – Please Be Sure to send all Mail Orders and Inquiries to our Milwaukee store, whose address is shown above. The following Branch stores are set up to handle Walk-in business only.

17929 Euclid Ave.; Cleveland, Ohio Phone (216) 486–7330
621 Commonwealth Ave.; Orlando, Florida Phone (305) 894–3238

ATLAS
in stock at A.E.S.

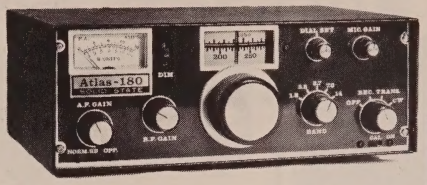

Atlas 180 160-20m Transceiver $479.00
AR-117 AC Power Supply 119.00
AR-230 AC Power Supply (230v.) 129.00
Deluxe mobile mount (plug-in) 40.00
Standard mount (cable & brackets) 10.00

AMATEUR ELECTRONIC SUPPLY
4828 West Fond du Lac Avenue
Milwaukee, Wisconsin 53216
Phone (414) 442–4200
Branch Stores in Cleveland, Ohio and Orlando, Florida

DIAL-A-PROP 516-883-6223

IT TOOK TWENTY YEARS. . . .

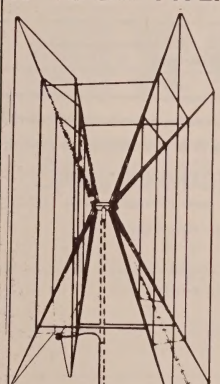

To convince hams that quad antennas will perform as well or better than most beams. Now that you're sold on the quad principle, we want you to have the best quad available.

And the GEM QUAD IS BY FAR THE BEST QUAD in existence.
- better in structural design
- better in quality of materials
- better in over-all performance

That's why more hams have bought GEM QUADS than any other brand, and probably more than any two or three other brands combined. The specs tell you why. So if you're ready to go the quad route, why not go first class?

And first class means GEM QUAD, of course.

- The GEM QUAD is a 2, 3, or 4 element antenna for 10, 15, and 20 meters.
- Nylon tension tubes create an anti-wire breaking device.
- Two element GEM QUAD gives maximum forward gain "where it counts."
- Toroid balun for single 52 ohm feed line matching. Handles the legal limit.
- Mounting spider of heavy duty aluminum alloy. 1 ½ inch o.d. stub; easy mounting.
- Fiberglass arms have withstood 100 m.p.h. winds. (2.5 sq. ft. windload area).
- Tridetic arm design (air passes through the arm).
- Simple assembly and tuning instructions supplied. Takes only minutes.
- Double "Cone-shaped" design resists change in critical measurements under severe weather conditions. Weather resistant.
- Complete antenna weighs 22 lbs., 3 element 35 lbs. TV rotator is adequate.

$129.00
Two Element Quad
includes U.S. Custom Import Duty or Canadian Federal Sales Tax.
Shipped Collect
Please includs check or money order with your order.

GEM QUAD PRODUCTS
BOX 53 TRANSCONA, MANITOBA CANADA
R2C 2Z5

Did you know that supplements to the book, "CQ YL," are available? They bring the book up to date with YLRL Officers through 1973 and the 6th YLRL Convention, held at Long Beach in May '72. If you have a copy of "CQ YL" and would like to add the new supplements (the pages are "slotted" so they fit directly into the "CQ YL" spiral backbone), drop a note with your request to author/publisher, W5RZJ, Louisa Sando, 4417 - 11th St., NW, Albuquerque, NM 87107. Please enclose two 10 cent stamps to cover cost of mailing. The one and only book about YLs in ham radio, "CQ YL," contains 21 chapters, over 600 photographs. Order your autographed copy, or a gift copy, from W5RZJ, $3.00 postpaid.

FOR SALE: ECS8 Vacuum Variable, 2 to 8 mmf. ideal for neutralizing capacitor, $17 postpaid. A. Dorhoffer, K2EEK, CQ Magazine, 14 Vanderventer Ave., Port Washington, NY 11050.

FOR SALE: Tubes 25L6 Swap for other tubes of equal value. A. Bielenda, W2IDA, 43 Chestnut Ridge Road, Saddle River, NJ 07458.

FORT WAYNE AMATEURS: Join the Fort Wayne Radio Club. Receive Newsletter and more. Contact WB9LJC.

FOR SALE: Clegg FM 27A, needs work, $225. Lafayette, HE45B Complete with HEG1 VFO mike and power cords, $50. C. Roeder, 329 Wheatland Ave., Shillington, PA 19067.

FOR SALE: National HC270, $85, NC183, $85, Viking 122 VFO, $20. Heath VFI-VFO $20, Globe, DSB-100 incl. CW, $70. All good condition. UPS-extra. WPRK, 5106 Sylvan Rd., Westover Hills Richmond VA 23225.

FOR SALE: Hammarlund HQ-170AC-VHF with IF noise immunizer, $300.00. Heath HO-13 panoramic adaptor, $50.00. H)-10 monitor scope,-WA3OHW, Philadelphia, PA 19148.

FOR SALE: Unique 80-10 Random Length wire tuner, $45. Postpaid in USA. Dave Lambert, WA1JSD, RFD 3, Derry, NH 03038.

FOR SALE: Bargain; Two Westinghouse 0-300 volt AC meters. New, cartoned. Ideal 110/220 volt line meters. Both for $5.00 ppd. Samkofsky, 4808 Brenda Dr., Orlando, FL 32806.

WORLDS Largest DX'er/Awards Hunter Club, CHC publishes world Directory of Awards. W/K $7.00, DX is $5.50. Box 385, Bonita, CA 92002.

SELL: RME 69 receiver, preselector, and speaker or trade for old wireless gear. TG Soukup, 161 Bob Hill Rd., Ridgefield CT 06877.

WANTED: Robot model 61 Viewfinder. FOR SALE: HP 200J Audio OSC., BC-221 AL with PS University Sound CP-1 Cassette Player. Mike Ludkiewicz, 143 Richmond Road, Ludlow, MA 01056.

CLEANING OUT: NC-303 with calibrator, $160. SX-101A, Needs a little work, $80.; Ranger, $70.; NCX-500 with A.C. and D.C. Supplies, $250.; much more. SASE for list. James Shank, W3CNS, 21 Terrace Lane, Elizabethtown, PA 17022.

WANTED: Any equipment, books, or manual on Cryptography. L. Kruh, WN2TSD, 17 Alfred Rd., W. Merrick, NY 11566. (516)378-0263.

FOR SALE: Hallicrafters SR-500 xcvr, 80-20M, 500W, AC, DC P.S., mike, spkr, $360.00. Joe Pluth WB9JHS, 6092 Chase Ave., Downers Grove, IL 60515.

ENGLISH SWL exchanges used checks and cinderella items. Selection checks for 1 dollar postage Bogus passports etc. 7 dollars. Will swap anything. Brian Smith, P.O. Box 4, Uckfield, Sussex, England.

FOR SALE: CX7-A (Signal One), CW and RTTY optional filters, manual and custom dust cover. Reported to be last one made at Calif. plant. One owner-no time to use $1295. Will accept as partial trade new R-390A, Commercial RTTY and or SSB transmitter (SRT16, TMC, Collins, etc.) or Lugar pistol. Steve Hose, WA9AXE, Forest Lake Estates, Hope, IN 47246.

BRAND NEW MARS SWR BRIDGES, 1.5-150Mhz $10.00. 2" and 2 1/4" SWR Meters new, $1.50. New S Meters w/cabinets, $6.00. Excellent used Jennings UCSXF 1200 Variable cap, $65.00. Include $1.50 postage on all meters. Make checks or money orders to Dick Clothier, WA7GFD, P.O. Box 1230, Pocatello, Idaho 83201.

WANTED: Microphones, 1920 to 1940, also literature. Write Bob Paquette 443 N. 31rst St., Milwaukee Wisconsin 53208.

FCC test answers updated any class, $5; Specify. Dixie Tec, Box 8352 Savannah, GA 31402.

DX QSL Bureau for all outgoing Foreign Cards. 4 cents each; for additional information contact Q-Aide, 321 Main Street, Watertown, MA 02172.

WANTED: Old radio show transcription discs. Any size or speed. Bill Stricklin, W4GJG, 118 Coburn Drive, Chattanooga, TN 37415.

TWO PLASTIC HOLDERS, Frame and Display 40 QSL's for $1.00, or 7 holders enhance 140 cards for $3.00 from your Dealer, or prepaid direct: TEPABCO, Box 198Q, Gallatin, TN 37066.

HAMFEST DATE FOR 1975: May 31st, Marriott Inn is new Headquarters. Information? Write WNY Hamfest, Box 1388, Rochester, NY 14603.

CONFIDENTIAL FREQUENCY LIST! Thousands of classified frequencies: spies, aircraft, ships, government, teletype, emergency, many more! $4.00 postpaid. Bob Grove, WA4PYQ, 6601A S.W. 56th St., Davie, FL 33314.

HIGH GLOSS QSL CARDS: From $10.95/1000 Full color catalog. $1.00. Lijon Graphics, Box 48, East Longmeadow, Mass. 01028.

SELL: ROBOT SSTV Models 80 Camera and 70 Original cartons and instruction books. Excellent condition. $500.00. Gordon Buckner, W0VZK, Box 721, Marshall, Missouri 65340.

MAGAZINES FOR SALE: CQ/73/QST/HAM RADIO issues at 10 cents each (plus shipping) from Lockheed Ham Club, 2814 Empire, Burbank, CA 91504. Send list and check. Available issues and any refund due will be sent promptly.

FOR SALE: Spectra Physics 2.0 mw 071-2 HeNe laser tube, brand new with power supply schematic, $110.00. WA2NDM, 5 Melville Rd., Great Neck, NY 11023.

LOOKING FOR old Lionel trains. Interested only in "O" gauge, excellent to like-new condition. Primary interest is locomotives prior to 1952, but will consider complete sets or more recent models. Am willing to buy outright for cash or swap radio gear to meet your needs. Write Dick Cowan, WA2LRO, c/o CQ Magazine, or call 516/883-6200.

NOW paying $2000.00 and up for ARC-94/618T ARC-102/618T, $1200.00 and up for ARC-51BX, $1500.00 and up for 490T-1 antenna couplers. We also need these control boxes-C-6287/ARC-51BX, C-6476/ARC-51BX, C-714E-2. We also need R-1051 receivers RT-662/Grc-106 tranceivers. We buy all late aircraft and ground radio equipment. Also pack radios. We are buyers not talkers. Bring your equipment in and you are paid on the spot. Ship it in and you are paid within 24 hours. We pay all shipping charges. If you want the best price for your equipment. Call us. Call collect if you have and want to sell or trade. We also sell. What do you need? D & R Electronics, R.D. 1, Box 56, Milton PA 17847. (717)742-4604.

SURPLUS. Giant bargain-packed catalog, $1. Etco Electronics, Dept. CQ, Box 741, Montreal A, H3C 2V2.

WILL BUY: Inoperative HRO-60 or HRO-50 receiver. Need: Working National Selectoject and HCU-50-2 Crystal Calibrator. Joe, K9UKX, 51625 Chestnut Road, Granger, IN 46530.

MERRY CHRISTMAS and HAPPY NEW YEAR from W0CVU. First amateur in the world awarded the RSGB EMPIRE AWARD on two way SSB in 1962.

what is an antenna noise bridge?

Antenna Noise Bridge (an-'ten-a noiz brij), n. Omega-t's name for a specialized testing device that checks your antenna system for resonant frequency and coaxial impedance.

Obtain maximum efficiency by determining the resonant frequency for any type of antenna with the solid state, self-contained Antenna Noise Bridge...

Two models...TE7-01 for 1-100 MHz range, $29.95...the TE7-02 for 1-300 MHz range, $39.95.

Sold through amateur radio dealers or direct from the factory.

omega-t systems® incorporated

320 TERRACE VILLAGE • RICHARDSON, TEXAS 75080 • (214) 231-5121

YOU'VE SEEN THE MAGAZINE ARTICLES

Here's what you can expect from the **DX ENGINEERING RF Speech Processor**

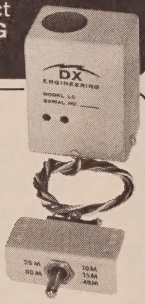

- **6 db INCREASE IN AVERAGE POWER**
- **MAINTAINS VOICE QUALITY**
- **IMPROVES INTELLIGIBILITY**
- **NO CABLES OR BENCH SPACE REQUIRED**
- **EXCELLENT FOR PHONE PATCH**
- **NO ADDITIONAL ADJUSTMENTS — MIKE GAIN ADJUSTS CLIPPING LEVEL**
- **UNIQUE PLUG-IN UNIT — NO MODIFICATIONS REQUIRED**

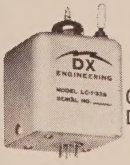

This is RF Envelope Clipping—the feature being used in new transmitter designs for amateur and military use.

Models Now Available

Collins 32S, KWM-2 ..... **$ 98.50 ea.**

Drake TR-3, TR-4, TR-6 **$128.50 ea.**

Postpaid — Calif. Residents add 6% Tax

Watch for other models later!

DX Engineering

1050 East Walnut, Pasadena, Calif. 91106

TUNABLE SLOTLINE FILTERS

**FOR REPEATERS-
BASE STATIONS-
MOBILES**

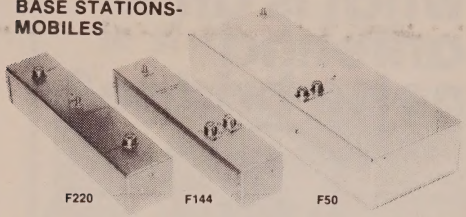

Suppresses harmonics and spurious radiation equally well with transmitter and receiver

Compact **Easy to install**

Low cost **No maintenance**

SPECIFICATIONS

BAND WIDTH: At tuned center frequency 60KC usable
INSERTION LOSS: No greater than 1.2 db maximum, adjusted
HARMONIC REJECTION: Greater than 80db
TUNED LINE: Silver plated
POWER INPUT: 150W R.F. Maximum

INPUT MATCHING: ¼ wave length of R G-8/R G-58
BILATERAL: Input and output are symmetrical
HOUSING: Selective gold anodized aluminum
EXTERNAL GROUND CONNECTION: 10-32 stud

Model F220 Rejection to adjacent signals -6db min
$39.95 Tuning range 220 - 225 MHz
Approximate dimensions 12"x3"x3"

Model F144 Rejection to adjacent signals -3db min
$39.95 Tuning range 143 - 149 MHz
Approximate dimensions 12"x3"x3"

Model F50 Rejection to adjacent signals -5db min
$49.95 Tuning range 48 - 54 MHz
Approximate dimensions 17"x4"x6"

Prepaid in U.S. Send check or M.O. to: **WIREX, INC.**

Ia. Res. add 3% Sales Tax

319-323-6014

**P. O. Box 964
602-608 Harrison Street
Davenport, Iowa 52805**

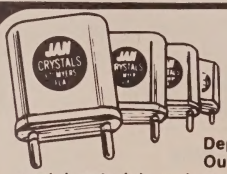

For FREQ. STABILITY

Depend on JAN Crystals. Our large stock of quartz crystal materials and components assures Fast Delivery from us.

CRYSTAL SPECIALS

2-METER FM for most Transceivers ea. $3.75
144-148 MHz — .0025 Tol.

Frequency Standards
100 KHz (HC 13/U) 4.50
1000 KHz (HC 6/U) 4.50

Almost all CB Sets, Tr. or Rec. 2.50
(CB Synthesizer Crystal on request)

Any Amateur Band in FT-243 1.50
(80-meter, $3.00 - 160-meter not avail.) **4 for 5.00**

For 1st class mail, add 20c per crystal. For Airmail, add 25c. Send check or money order. No dealers, please.

JAN CRYSTALS

**Division of Bob Whan & Son Electronics, Inc.
2400 Crystal Drive
Ft. Myers, Florida
33901**

**All Phones
(813) 936-2397**

Send 10c for new catalog with 12 oscillator circuits and lists of frequencies in stock.

WANTED: HRO60 and 50 coil sets. Details on modifications for HRO60 and 50. NEED: Schematic or copy of one for National NC400. Will pay for. K9UKX, Joe, 51625 Chestnut Road, Granger, IN 46530.

WE'LL PRINT ANYTHING: Comfy call letter "Tee" shirt or Sweatshirt. Choose your slogan or call letters and handle. (up to 30 letters). Tee shirt $3.95, Sweatshirt $5.95. Add $2.00 for printing on both sides. 10 or more with same slogan (may have different call letters) deduct 10%. Satisfaction or your money glumly refunded. Send check or money order with size to: T. Reginald Abare, K1VNE, P.O. Box 231, Brattleboro, Vermont, 05301.

COLLINS STATION: 32S-1, 516F-2, 75S-1, 312B-4, cables, manuals. Sell complete only. $900.00. SWAN 500 with power supply and manual. $320. All super clean. Will ship prepaid. K6DRE, 10103 Olivia Terrace, Sun Valley, California 91352. (213-768-2934).

FOR SALE: Morse International tape perforator manufactured by Teletype Corporation and Companion Boehme 4-DB tape transmitter. Both excellent operating condition with tables. $125.00 total plus shipping. Mike Langner, K5MGR, 929 Alameda Road NW, Albuquerque, New Mexico, 87114.

2 METER FM MOBILE "CARTOP" ANTENNAS: 1/4 Wave and 1/2 Wave models. Unique, secure instant mount. No magnets; no drilling holes. Omnidirectional - unlike trunk lid mounts. Tuneable 1:1 SWR. Money back guarantee. 1/4 Wave model $16.95; 1/2 Wave $18.50. Add $1.00 for shipping and handling. (Conn. residents - Sales Tax). MARSH DEVICES, P.O. Box 154, Old Greenwich, Connecticut 06870. Literature available.

TECH MANUALS: For Govt. Surplus gear, $6.50 each: URM-25D, URM-32, R-220/URR, R-274/FRR, R-390/URR, TS-497B/URR, TS-382D/U, LM-21, PRC-10. Thousands more available. Send 50 cents (coin) for large list. W3IHD, 7218 Roanne Drive, Washington, DC 20021.

WANTED: Tunaverter Converter, Model SWL, 9.5-16 MC. Fred Haines, 132 Rural Ave., Lewisburg, PA 17837.

MUST SELL: Going to college; Hallic. SR-500 xcvr, AC P.S.; Heath SB-610 scope; good condition; $350; WA4YCF, 312 Main St., Apt. 8 Georgetown, Kentucky 40324.

APARTMENT DWELLERS W6TYP won a world record with a Partridge six Band VFA System from a hotel room. Details; Partridge Electronics LTD., Broadstairs, Kent, England.

BUY-SELL-TRADE: Write for monthly Mailer, Give name, address, and call letters. Complete stock of major brands new and reconditioned equipment. Call us for best deals. We buy Collins, Drake, Swan, etc. SSB & FM. Associated Radio, 8012 Conser, Overland Park, Kansas 66204. (913)381-5901.

OSCAR SLIDES: Set of 5, $1.25, Lift-off and Spacecraft. Proceeds AMSAT. K6PGX, P.O. Box 463 Pasadena, CA 91102.

WANTED: Antenna, 10-ft. WWII whip, unfolds by internal spring loading. Herrick, 2160 Mastlands, Oakland, CA 94611.

WANTED: Hallicrafters SX-88 for parts, any condition considered. K0MNA, 4805 Sullivan, Wichita Kansas, 67204.

MIDLAND 2M FM TRANSCEIVERS - THE BUY OF THE YEAR. Sales Agent Samples and Display Units - Most Never Turned On - In Original boxes. Full Factory Warranty! 13-500 (15-watt) 12 Channel Mobile; $213.50, 13-505 (30-watt) 12 Channel Mobile; $241.50. All Equipped with 34/94, 16/76 and 94/94. Also 13-509 220 MC 10-watt 12-channel FM Mobile Transceivers; $188.95. Satisfaction Guaranteed! Send check with order to Mesa, INC. Attn: W0CW, 5460 Buena Vista Drive., Mission, Kansas 66205. (913)262-6565.

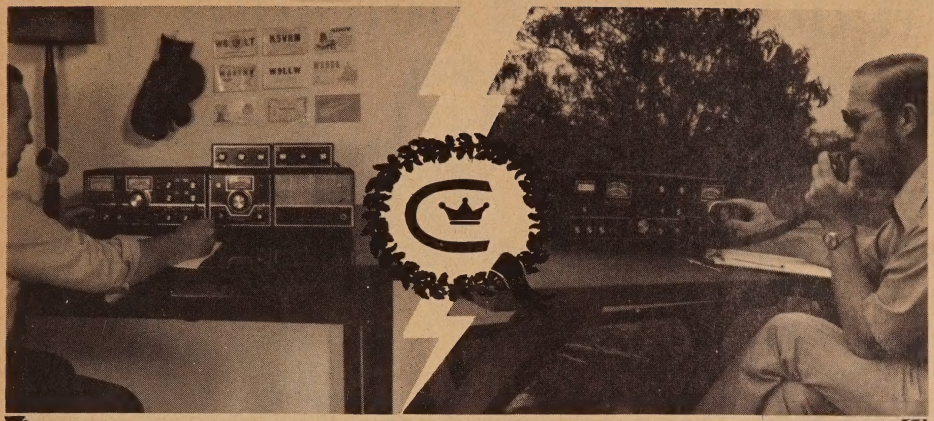

YOUR BEST HOLIDAY BUY

IS AT QUEEN CITY ELECTRONICS

When you're searching for a meaningful gift for that special person this Christmas, you want the best value you can get. Decide on a ham rig that is powerful, reliable, durable . . . and still economical . . . and you've chosen a gift that's sure to please.

Here's how to be certain you get your money's worth when selecting an amateur transceiver:

- Insist on the brand name known for quality *AND* which has the best reputation for outstanding customer service.
- Be sure the unit has Single-Sideband, AM and CW functions on all 5 major ham bands.
- Insure natural voice characteristics with an audio response *AND* bandpass that is essentially flat from 300 to 3000 Hertz.
- Look for a final amplifier using 8950 tubes designed to handle RF power.
- Determine the "Cost-Per-Watt". Divide the total cost of the system by the P.E.P. Input Wattage to find your best buy.
- Use your Swan Revolving Credit for easy to handle deferred payments.

Consider these "Best Buy" examples from Swan Electronics:

700CX Champion Transceiver — Provides 700 Watts P.E.P. Input without an accessory amplifier. Added to an existing A.C. power supply, it costs less than 86¢ per watt! Order early, this is a fast moving item.

300B Cygnet *de novo* **Transceiver —** Totally portable with internal power supply and speaker. Add a 1200X Cygnet Amplifier for 1200 Watts P.E.P. Input. Total cost is just 68¢ per watt!

You can't beat it.

Whether you're upgrading your own station or you want to please that special ham operator on your Christmas gift list . . . see Queen City Electronics . . . your Authorized Swan Dealer.

QUEEN CITY ELECTRONICS INC.

7404 Hamilton Avenue
Cincinnati, Ohio 45231

Telephone (513) 931-1577

Midland puts you into 2-meter FM mobile for under $250

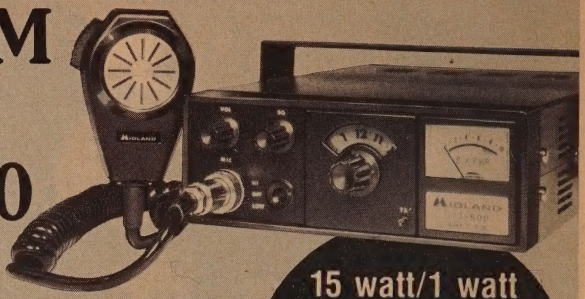

15 watt/1 watt power

•

12 channel

•

Suggested price $249.95

Midland's Model 13-500 is a power packed compact, just 2¼" high x 6" wide x 9" deep. Includes mobile mounting bracket, push-to-talk mike, crystals for .16/.76, .34/.94 and .94/.94. Put it to work now and join in Midland's **R.S.V.P.**, Repeater Service Voucher Program, to help support the repeater service of your choice.

MIDLAND
ELECTRONICS COMPANY®

Free Midland Amateur Radio Catalog – Write Dept. C., Box 19032, Kansas City, Mo. 64141

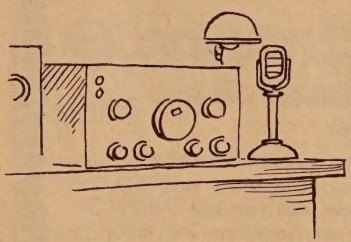

Your SSB Transceiver

+

Dentron 160XV Transverter

= **160 Meters**

Get in on the excitement on 160 meters the easy way with the new Dentron Radio Co. Model 160XV Transverter. No need to buy a new transceiver, this low cost easy to use accessory quickly connects to your existing SSB transmitter, receiver or transceiver with just two simple connections and you are ready to join in on the fun on "top band." With sun spots at their low, there will be a lot of good action in the months ahead and you'll want to be ready.

- 5 watts drive ample for full output
- 100 watts dc input
- Full 1.8-2.0 MHz coverage
- 3.8 to 4.0 MHz input
- Matches 50-ohm antenna
- Built-in power supply for 110/220 V 50/60 Hz
- No modifications to existing equipment
- Receiver sensitivity better than 1 μV

Also the 160AT antenna tuner for your 160-meter 50-ohm exciter just $49.95 postpaid

All units in stock for immediate delivery

ORDER FROM

Your BANKAMERICARD welcome here

DENTRON RADIO CO.
27587 Edgepark Drive
North Olmsted, Ohio 44070
(216) 734-7388

$199.50
PPD U.S.A.

West Coast:
11591 Rabaul Ave
Cypress, Cal. 90630

master charge THE INTERBANK CARD

THE SWAN 600T!

There are five transmitters available to amateur radio operators today providing 5-band coverage in SSB, CW and AM modes. Of these five, only SWAN's 600T supplies 600 watts P.E.P. input. Among the others, one has 240 watts P.E.P.; two have 200 watts P.E.P. (one of these requiring an accessory power supply); and one is a kit capable of a mere 180 watts P.E.P. input.

Compare the cost per watt, then judge for yourself as to which is the best value: The kit retails at $1.67 per watt; the 240 watt unit is $1.41 per watt; the 200 watt rig with the power supply built-in runs $2.30 per watt, while the other 200 watt transmitter costs $2.65 per watt by itself or $3.15 per watt if you buy the power supply recommended.

Now consider the economical SWAN 600T — it gives you a full 600 watts P.E.P. input, about three times the power of the others, for **JUST 98¢ PER WATT!**

The brand YOU should buy is obvious. Visit your authorized SWAN dealer and order your 600T.

WHEREVER THERE'S VALUE IN AMATEUR RADIO, YOU'LL FIND SWAN ELECTRONICS

600T	Transmitter	**$589.95**
600R	Custom Receiver with SS-16B filter	**$615.95**
600S	Speaker	**$ 24.95**
600SP	Deluxe Speaker with FP-1 phone patch	**$ 69.96**
510X	Crystal Oscillator	**$ 54.95**
VX-2	Automatic Voice Control	**$ 44.95**
MARK II	Linear Amplifier (2000 watts P.E.P.)	**$749.95**

DEALERS THROUGHOUT THE WORLD
or order direct from

SWAN ELECTRONICS
A subsidiary of Cubic Corporation

Home Office: 305 Airport Road • Oceanside, CA 92054
Telephone: (714) 757-7525

THE BEST PRACTICAL DEVELOPMENTS IN AMATEUR RADIO

IF YOU NEED A COMMUNICATIONS TOWER UNDER 100' HIGH, COMPARE BEFORE YOU BUY:

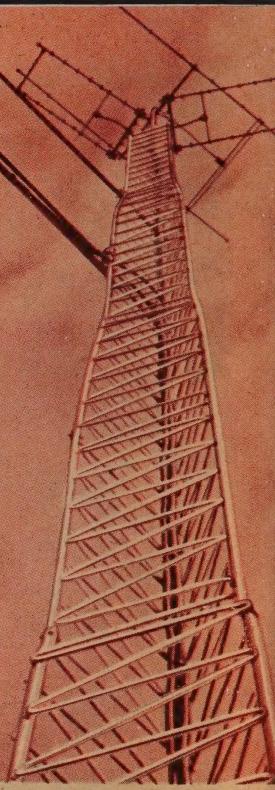

	Free-standing Ascom/Universal Aluminum Tower	Typical Free-standing Commercial Steel Tower
Height	60'	60'
Wind rating	6 Sq. Ft. @ 80 MPH (EIA Standard)	3 Sq. Ft. @ 80 MPH (EIA Standard)
Erection requirement	1 man, 3 hr.	3 men, 8 to 12 hr.
Tower weight	153 lbs.	571 lbs.
Maintenance	none	annual
Mfgr. sugg. list	$466.20	$590.00

Now—can you think of one good reason to buy a steel tower?

ascom® / UNIVERSAL ALUMINUM TOWERS
ascom electronic products
12435 Euclid Ave., Cleveland, Ohio 44106

FM YOUR GONSET

(or your Clegg 22'er, Poly-Comm 2, PC-62, Johnson 6N2, Aerotron 500, HA-460, TX-62 or VHF-1)

- New! Plug-in modulator puts the Communicator transmitter on FM.
- No modification or rewiring on your Communicator. Just plug into mike jack and crystal socket.
- Compact self-contained modulator measures 4" x 3" x1½".

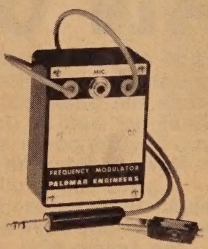

- Works with Communicator I, II, III, IV and GC-105, and other rigs listed.
- FM at a tenth the cost of a new rig.
- Frequency adjust for netting built in.
- $34.50 postpaid U.S.A. $36.50 for PC-2, PC-62, HA-460. Specify transmitter model. California residents add 5% sales tax. (HC-6/U crystal and 9 volt transistor battery not supplied.)
- Send for free descriptive brochure.

PALOMAR ENGINEERS
BOX 455, ESCONDIDO, CA 92025

Communications Engineers and Technicians.

(FOREIGN EMPLOYMENT)

ARAMCO, Saudi Arabia, Needs the following:

ENGINEERS - Graduate with min. 5 years experience in operations & maintenance of communications systems. Digital telemetering systems experience required.

TECHNICIANS - Specialized training in Microwave and Multi-plex carrier systems, preferably Lenkurt equipment. Should have had previous experience in VHF and UHF radio systems. Good schools, hospitals and recreational facilities, all benefits plans plus opportunity for personal savings and extensive travel.

Send resume of education, work experience and personal history to:

EMPLOYMENT SUPERVISOR

ARAMCO SERVICES COMPANY
1100 Milam Building Houston, Texas 77002
An equal opportunity employer

ALL SOLID-STATE 160 WATT MONOBANDER

SSB/CW — CHOOSE 40 or 80 METERS

SWAN's newest and most powerful single-band transceiver. Perfect for mobile use, operating directly from any standard 12V DC battery with a minimum of current drain. No transmitter warm-up time or intricate tuning is necessary. Simply turn the monobander on, dial your frequency and immediately 160 watts P.E.P. input is working for you.

Novices and experienced hams, alike, will appreciate the simplicity and practicality of this newest development in the state-of-the-art for amateur radio. SWAN's MONOBANDER's feature infinite VSWR protection from mismatched antenna loads, as well as an easy to see Transmit LED indicator on the S-meter face to let you know when your signal is getting out.

Select the MB-40A for 7.0 to 7.3 MHz operation, or if you prefer the 3.5 to 4.0 MHz band, you may choose the MB-80A. Whichever you select, one of new 160 watt models or the new improved 75 watt MB-40 or MB-80, you are assured of the superior engineering, workmanship and service that only SWAN ELECTRONICS can give you. Here is excellent performance in a handsome package that blends well with every automobile interior.

See the powerful MONOBANDER at your authorized SWAN dealers showroom this week—*you'll be glad you did!*

MB-40A or MB-80A (160 watt).....**$329.95**
MB-40 or ME-80 (75 watt) **$299.95**
MBCW (Optional CW Monitor) .....**$ 19.95**
SWAN 404 Microphone.....**$ 24.95**

DEALERS THROUGHOUT THE WORLD
or order direct from

SWAN ELECTRONICS
A subsidiary of Cubic Corporation

Home Office: 305 Airport Road • Oceanside, CA 92054
Telephone: (714) 757-7525

THE BEST PRACTICAL DEVELOPMENTS IN AMATEUR RADIO

THE BIG SIGNAL

THE APPROVED LEADING HAM AND COMMERCIAL BALUN IN THE WORLD TODAY.

"W2AU" BALUN $12.95

The proven balun

WITH BUILT-IN LIGHTNING ARRESTER

IT'S WHAT'S INSIDE THAT COUNTS!

1. **HANDLES FULL 2 KW PEP AND THEN SOME.** Broad-Banded 3 to 40 Mc.
2. **HELPS TVI PROBLEMS** By Reducing Coax Line Radiation
3. **NOW ALL STAINLESS STEEL HARDWARE.** SO239 Double Silver Plated
4. **IMPROVES F/B RATIO** By Reducing Coax Line Pick-Up
5. **REPLACES CENTER INSULATOR.** Withstands Antenna Pull of Over 600 Lbs.
6. **BUILT-IN LIGHTNING ARRESTER.** Protects Balun —Could Also Save Your Valuable Gear
7. **BUILT-IN HANG-UP HOOK.** Ideal For Inverted Vees, Multi-Band Antennas, Dipoles, Beam and Quads

NOW BEING USED EXTENSIVELY BY ALL BRANCHES OF THE U.S. ARMED FORCES, FAA, RCA, CIA, CANADIAN DEFENSE DEPT. PLUS THOUSANDS OF HAMS THE WORLD OVER They're built to last

***BIG SIGNALS* DON'T JUST HAPPEN— GIVE YOUR ANTENNA A BREAK**

Comes in 2 models. 1:1 matches 50 or 75 ohm unbalanced (coax line) to 50 or 75 ohm balanced load. 4:1 model matches 50 or 75 ohm unbalanced (coax line) to 200 or 300 ohm balanced load.

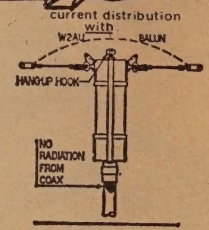

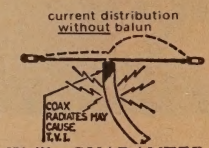

We'll GUARANTEE no other balun, at any price, has all these features.

AVAILABLE AT ALL LEADING DEALERS. IF NOT, ORDER DIRECT

UNADILLA RADIATION PRODUCTS MFRS. OF BALUNS Tel: 607-369-2985 **Dept. CQ UNADILLA, N.Y. 13849**

186 db gain!!... over an isotropic noodle inside a copper box sunk in a full cesspool . . . . .

Tired of Wild Claims . . . . and not so wild performance? Try a KLM Amplifier or Antenna for a pleasant surprise.

10 Watts In

PA 10-140B 2 Mtr. Power Amp

$189.95

140 Watts Out

KLM 13.9-14.4-5 Big Stick 20 Mtr. Monobander 9.7 db gain

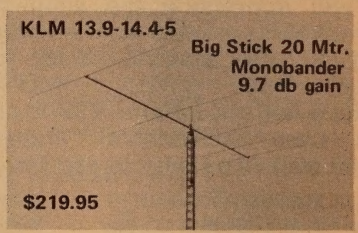

$219.95

Write for our NEW FALL '74 Catalog on Ants & Amps and Accessories.

KLM ELECTRONICS

Dept. Q 1600 DECKER AVENUE SAN MARTIN, CA 95046

408-683-4240

10% Down Delivers Your Choice of Swan Equipment

on approval of your credit application

That's right! A 1200X linear amplifier for just $30 down; a 300B transceiver at $50 down; the powerful 700CX transceiver is yours for only $60 down; or, get that big TB4HA tribeam antenna you've always wanted for a low down payment of $19! Imagine, you can even join the newest trend in amateur radio with one of Swan's new — all-solid-state transceivers for as low as a $60 down payment. Any new Swan product can be purchased on credit.

Because we've been servicing credit plans for hams longer than any other amateur radio manufacturer, we know hams have excellent credit ratings. That's why we simplify things. Pick up an application from your Swan dealer or, if you prefer, write us and we'll send you a form and complete information. Your request is processed the day we receive it and a credit card is issued as soon as approval is completed. Then, whether you purchase from a dealer or direct from the factory, you can simply say "Charge it."

With Swan's Revolving Credit Service you can pay-off your account within 25 days of billing and avoid any finance charge or, you can spread your payments over a number of months. 10% is the minimum down payment required and $10 is the minimum monthly payment, depending on your account balance.

An important fact to remember is that this plan is available directly from Swan. We personally, and confidentially, handle the servicing of your purchase from beginning to end. We will not sell your account to some other financing institution.

While you're thinking about it, fill in the coupon and mail it. We'll rush full information and an application to you free of charge.

SWAN ELECTRONICS
A subsidiary of Cubic Corporation

305 Airport Road • Oceanside, CA 92054 • Phone (714) 757-7525

C674

Mail to: *SWAN ELECTRONICS,* 305 Airport Road — Oceanside, CA 92054

Gentlemen:
I am interested in opening a SWAN Revolving Credit Service account. Please send me full information and an application form.

Name:_____ Call: _____

Address: _____

City:_____ State:_____ Zip: _____

☐ Please include a copy of the latest SWAN Catalog of equipment.

NEW HT-144B

TWO METER F.M. PORTABLE

CRYSTAL SOCKETS INCLUDED ! .35 uV SENSITIVITY OR BETTER !
IMPROVED TRANSMIT AUDIO ! .25 SQUELCH SENSITIVITY !
UP TO 6 KHZ DEVIATION ! F.C.C. TYPE APPROVAL PENDING !

IMPROVED INSTRUCTION MANUAL !

KIT ONLY $129.95 COMPLETE less batteries
AND for a limited time only we will furnish
ONE SET OF CRYSTALS FREE !
Your choice of 94-94; 52-52; or 34-94

IT'S AN EVEN BETTER BUY NOW ! ! ! ! ! ! ! !

ACCESORIES: "Rubber Duckie" Antenna (BNC Connectors) $12.95
Nicad Batterie Charger ..... $ 4.95
Sealed 12 v Nicad Battery Pack $29.95

Please include $1.00 for Shipping and Handling - N.Y.S. residents add sales tax

Your BANKAMERICARD welcome here

VHF ENGINEERING

– DIV. of BROWNIAN ELECT. CORP. –

320 WATER ST. POB 1921 BINGHAMTON, NY 13902 607-723-9574

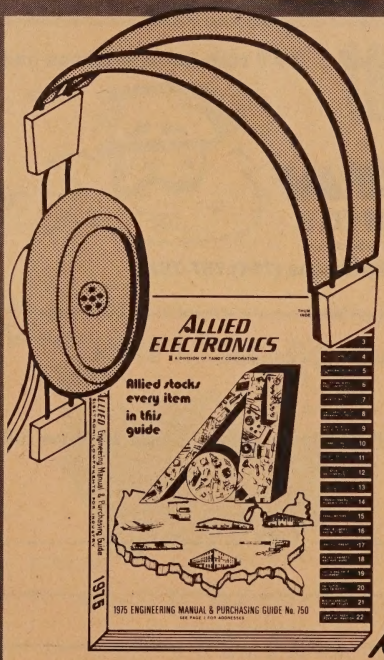

Only $2.99

FOR DELUXE HEADPHONE AND GET FREE ALLIED ELECTRONICS' 1975 ENGINEERING MANUAL & PURCHASING GUIDE WITH PURCHASE...

Don't miss out, Get in on this great buy while quantities last! Originally $5.95, headphone is yours now for only $2.99. It features comfortable vinyl-covered headband with foam rubber temple-cushion, plastic receiver housing equipped with removable earcushion, and captive 5' cord equipped with 1/4" phone plug. 1000 ohms. With purchase you get free Allied's $5-value 1975 Purchasing Guide which gives you complete finger-tip access to our broad line of electronic gear and components. **Send your check or money order for $2.99 now to Dept. SK, Allied Electronics, 1355 Sleepy Hollow Rd., Elgin, Ill. 60120.**

ALLIED ELECTRONICS

A DIVISION OF TANDY CORPORATION

Powerful Portability

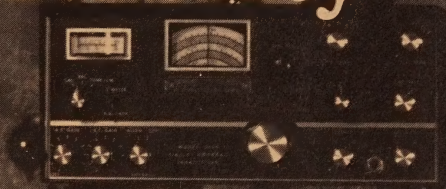

Team-Up with Dual Cygnets to Punch Through QRM — AND Do It Economically!

68¢ PER WATT!

1200 watt P.E.P. input, 1200X Cygnet Linear Amplifier

Use this coupon to order direct from the factory.
(California residents please include sales tax.)

DEALERS THROUGHOUT THE WORLD
or order direct from

SWAN®
ELECTRONICS
A subsidiary of Cubic Corporation

305 Airport Road
Oceanside, CA 92054
Telephone (714) 757-7525

Analyze the real expense of your ham station. Add up all your costs and divide by your rated wattage. Find out what you're really paying for every watt you use.

Want quality and functional economy? Here's a suggestion: Install a Swan 1200X Cygnet Linear Amplifier driven by a Swan 300B Cygnet *de novo* Transceiver. Both have internal power supplies, operate 10 through 80 meters, have SSB and CW modes, and utilize 8950 tubes for RF amplification. A built-in speaker and CW sidetone monitor comes with the 300B while the 1200X has excellent metering plus a bypass switch so you can operate barefoot. Swan provides the quality and functions, now look at the economics.

Add the $519.95 price of the 300B to the $299.95 price of the 1200X. Then divide by 1200 watts P.E.P. input. The result is a most respectable power level for a very low cost of just 68¢ per watt!

Try to beat that figure anywhere else, today.

It's pure common sense — the heart of any station is its quality; its power; and, these days, its economy. Investigate the Cygnets — you won't be disappointed. If you still want a few extras, like a VOX or VFO, Swan has them, too. Visit an authorized Swan dealer soon or, if you wish, you can use the coupon below to order your Cygnets now.

Gentlemen:
Please ship the following Swan products best way.

- ☐ 300B Cygnet *de novo* Transceiver (300 watts P.E.P. input) $519.95
- ☐ 300B with SS-16B Super-selective I.F. filter $589.95
- ☐ 1200X Cygnet Linear Amplifier (1200 watts P.E.P. input) $299.95
- ☐ 508 External VFO $189.95
- ☐ 14-A DC Coverter $49.95
- ☐ VX-2 Plug-in VOX $44.95

TOTAL AMOUNT OF ORDER IS $ _____

- ☐ 20% down payment enclosed, ship C.O.D.
- ☐ Full payment enclosed
- ☐ 10% down payment enclosed, charge to my Swan Credit#_____

Name: _____

Address: _____

City: _____ State: _____

Amateur Call: _____ Zip: _____

Index to *CQ* Vol. 30—1974

ANTENNAS, TOWERS TRANSMISSION LINES

Australian Travelling Wave Broadband Dipole (ANTENNAS) ..... 25, Oct.
Coax Fed Trio for 160, 80, 40 and You, A (DeWitt, W2DD) ..... 30, Apr.
Compact 2-element 40 m. Beam (ANTENNAS) ..... 22, Oct.
Cubical Quad Antenna: Origin and Variations (ANTENNAS) ..... 54, Jan.
Determining Resonant Lengths of Transmission Lines (Glanzer, K7GCO) ..... 37, May
EIA Sets Standards for Amateur Antennas ..... 32, March
Feed Systems for the All-Driven Array (ANTENNAS) ..... 42, June
G5RV Multi-Band Dipole (ANTENNAS) ..... 54, Dec.
HB9CV All-Driven Array for 15 or 6m. (ANTENNAS) ..... 39, Sept.
Hidden Mobile Home Antenna Installation (ANTENNAS) ..... 24, Oct.
"Invisible" Antennas for Difficult Locations (ANTENNAS) ..... 45, July; 27, Aug.; 53, Dec.
Lightweight Yagi Construction, Another Approach to (Schofield, W1RIL) ... 34, May
Loss In Transmission Lines (LaHiff, W2IVT) ..... 49, Dec.
Low Profile Quad Antenna, The (Tyskewicz, W1HXU) ..... 24, Feb.
Multi-band Dipole Covers 40, 20, 15 and 10 m. (ANTENNAS) ..... 40, Sept.
Seven Basic Rules of Antenna Performance (ANTENNAS) ..... 34, Apr.
Seven-Element 2m. Beam (ANTENNAS) ..... 44, March
Simple Antennas for the Novice (Novice Shack) ..... 31, July
Simple Gain Antenna for 2m. (ANTENNAS) ..... 42, March
Single Quad Loop Antenna for 15m. (ANTENNAS) ..... 47, Nov.
Sloping Quad for 80 Meters, A (Liga, K2INA) ..... 46, Apr.
Correction (LETTERS) ..... 7, July
Transmission Line Loss at H.F. and V.H.F. (ANTENNAS) ..... 45, March
Tri-band Dipole from Twin-Lead (ANTENNAS) ..... 40, Sept.
VK5YS Helical Dipole for 40m. (ANTENNAS) ..... 45, March
W3FQJ Longwire Inverted V (QRPp) . 50, May
W9LZX Lazy Quad Loop for 80m. (ANTENNAS) ..... 43, June
WBØCXM Delta Quad for 15m. (ANTENNAS) ..... 41, June
80m. Dipole Array for Short Range Communication (ANTENNAS) ..... 41, Sept.
160 Meter Receiving Loop (ANTENNAS) ..... 42, June

AUDIO AMPLIFIERS, MODULATION

Audio Filters: Active and Passive (QRPp) ..... 36, Oct.
Two-Tone Generator, A One Chip (Olson, W6GXN) ..... 48, Apr.

CIRCUITS AND DESIGN

Designing With Transistors (SSTV)
Emitter Followers ..... 44, Feb.
Low Gain Amplifiers ..... 38, March
High Gain A.C. Amplifiers ..... 42, Apr.
Discrete and IC Timers (MATH'S NOTES) ..... 64, Apr.
Experimental Synthesized VFO (MATH'S NOTES) . 44, July; 25, Aug.; 28, Nov.
FET's In High-Z Volt-Ohmmeters (MATH'S NOTES) ..... 26, Oct.
Filter Design By Frequency/Impedance Scaling (COP'S COLUMN) ..... 31, Oct.
Incremental Tuning for Simple Transceivers (QRPp) ..... 50, Apr.
LED Applications (MATH'S NOTES) ... 45, Dec.
LSI Frequency Divider Chips (MATH'S NOTES) ..... 66, Feb.
SN74S124 Voltage Controlled Oscillator from T. I. (MATH'S NOTES) ..... 66, Feb.
Solid State Switching Methods (MATH'S NOTES) ..... 48, May
Synthesized Variable Frequency Oscillator, Design Thoughts (MATH'. NOTES) ... 50, March
Using Field Effect Transistors (MATH'S NOTES) ..... 36, Sept.; 26, Oct.
Worst-Case-Analysis or "It Doesn't Work!" (Kasser, G3ZCZ/W3) ..... 29, March
100 mw Frequency Doubler Uses 40637A on 156 mHz (MATH'S NOTES) ..... 67, Feb.

COMMERCIAL EQUIPMENT— MODIFIED

FET Conversion of R.F. or I.F. Amplifier (MATH'S NOTES) ..... 27, Oct.
Incremental Tuning for Simple Transceivers (QRPp) ..... 50, Apr.
Modifying the MFJ Enterprises CQF-3 Filter for Variable Notch/Peak Depth and Frequency (QRPp) ..... 37, Oct.
Phelps-Dodge 5/8 Wave Antenna for 2m. (MATH'S NOTES) ..... 25, Aug.

COMMERCIAL EQUIPMENT— REVIEWS

Cepco Model T10-C Touch-Call Decoder, *CQ* Reviews: The (Sternberg, W2JUP) . . 41, July
Heathkit HW-202 2-Meter FM Transceiver, *CQ* Reviews: The (Math, WA2NDM) . . 25, June

ALL AMERICAN MADE

FULLY SOLID-STATE BROADBAND TUNING 300 WATTS P.E.P.

Now there is enough power, from a completely solid-state transceiver, to enjoy clean contacts everytime — without the bother of tuning! Swans' NEW SS-200A provides you with a nominal P.E.P. input of 300 watts on all single sideband transmissions. Turn it on and you're on the air. You don't have to wait for the set to warm up. And look at all the extra features this rugged station includes:

•Broadband circuits to eliminate transmitter tuning on 10, 15, 20, 40 and 80 meters •Infinite VSWR protection •Minimized front-end overload, distortion and cross-modulation •Variable VOX gain •Variable threshold noise-blanker •Semi-break-in CW with CW monitor •25 kHz calibrator •Fast attack/controlled decay AGC •And, more! It's all in this NEW SS-200A transceiver. An ordinary 12V automobile battery supplies the nominal 13.5V DC power required. •Only 0.5 amps current drain on receive mode. Here is an easy to install, reliable, mobile unit.

Your home station can be readily equipped by adding a PS-20 matching 110V AC power supply. Optional accessories include: 610X crystal controlled oscillator, SS-208 VFO, Mark II 2000 watt P.E.P. linear amplifier, microphones and mobile mounting kits.

See this modern transceiver on your next visit to an authorized Swan dealer or, if you prefer, order direct from Swan Electronics.

WHEREVER THERE'S VALUE IN AMATEUR RADIO, YOU'LL FIND SWAN ELECTRONICS

SS-200A 300 Watt Transceiver	**$799.95**
PS-20 110V AC Power Supply	**$159.95**
610X Crystal Oscillator	**$ 54.95**
SS-208 VFO	**$189.95**
Mark II Linear Amplifier	**$749.95**
444 Desk Microphone	**$ 35.95**
404 Hand-held Microphone	**$ 24.95**
SS-MTK Mobile Mounting Kit	**$ 16.95**
SS-GMTK Gimbal Mounting Kit	**$ 11.95**

DEALERS THROUGHOUT THE WORLD
or order direct from

SWAN®
ELECTRONICS
A subsidiary of Cubic Corporation

Home Office: 305 Airport Road • Oceanside, CA 92054
Telephone: (714) 757-7525

THE BEST PRACTICAL DEVELOPMENTS IN AMATEUR RADIO

Heathkit IB-1100 and IB-1102 Frequency Counters, *CQ* Reviews: The (Scherer, W2AEF) ..... 29, Jan.
Robot Research Slow Scan TV Equipment, *CQ* Reviews: The (MacDonald, WØORX) ..... 20, Aug.
Ten-Tec Model 315 Receiver, *CQ* Reviews: The (Scherer, W2AEF) ..... 35, Feb.

CONTESTS

All Asian Contest 1973 North American Results (CONTEST CALENDAR) ..... 60, June
All Time Records, *CQ* W.W. DX Contest (Capossela, Jr., W2IWC)
World ..... 26, Nov.
USA ..... 33, Nov.
CQ 160 Meter DX Contest
1973 Results ..... 38, Jan.
1974 Rules ..... 74, Jan.
1974 Results ..... 33, Oct.
CQ WPX SSB Contest
1973 Results ..... 31, Feb.
1974 Rules ..... 38, Feb.
1974 Results ..... 53, Dec.
CQ 1973 W.W. DX (C.W.) Contest
Claimed Scores ..... 56, Feb.
Results ..... 33, Aug.
CQ 1973 W.W. DX (Phone) Contest
Claimed Scores ..... 75, Jan.
Results ..... 50, July
CQ W.W. DX Contest
1974 Rules ..... 34, Sept.
QRP ARC 1st Annual QRP Contest Results (QRPp) ..... 42, Feb.
Third Annual QRPp QSO Party Results (QRPp) ..... 52, Apr.
USSR 1973 Contest Results (CONTEST CALENDAR) ..... 62, June
WAEDC 1973 Contest Results (CONTEST CALENDAR) ..... 60, May
25th Annual Armed Forces Day Communications Test, Announcing the ..... 40, May

DX AND OPERATING

Happiness is Visiting A Ham (Pataki, WB2AQC)
Part I ..... 34, Dec. 1973
Part II ..... 34, Jan.
LG5LG and SJ9WL—Morokulien (DX) ..... 54, March
Serrana Bank DXpedition (Lawson, K6JAN) ..... 28, May
Single Band C. W. WAZ number 1 to W8WZ (DX) ..... 60, Jan.
Single Band SSB WAZ Number 1 to WØSFU (DX) ..... 70, Apr.
Visiting the Balkan Hams (Pataki, WB2AQC)
Part I ..... 28, Oct.
Part II ..... 34, Nov.

HISTORICAL

RME Success Story, The (Orr, W6SAI) 30, May
Surplus Story, A (Samkofsky, K4RHU) 41, Apr.
Transistor In 1926? The (Keils) ..... 17, Aug.

KEYING AND KEYERS

Digital Speed Readout In An Electronic Keyer (Gilbert, WA2SKL/WA4SPD) .... 26, Dec.
Morse Code Digital Encoder for C.W., A (Caristi) ..... 16, June

LEGAL

FCC Proposes Rule Changes Re: Commemorative Stations, Automatic Control of Repeaters, Cross-band Repeaters (ZERO BIAS) ... 5, Sept.
Re-Vamping Expected in Amateur License Structure (ZERO BIAS) ..... 5, Feb.
W2OVC Lawsuit (ZERO BIAS) .. 5, June; 5, Apr.

MISCELLANEOUS: GENERAL

CQ-75 (Kahn, K4FW) ..... 62, Apr.
Dr. H. E. Stricker, W8WZ (DX) ..... 42, Oct.
Handy-Talkie Operation In Aircraft ('JUP On FM) ..... 30, June
"Let Your Fingers Do The Talking" (Kruger, K2LDC) ..... 35, March
Phantom Copying, A Transitional Step to QRQ (D'Onofrio, W2PRO) ..... 21, June
Radio Communications In Primitive New Guinea (Mann, W9PRH) ..... 27, Feb.

MISCELLANEOUS: TECHNICAL

Audio Filters: Active and Passive (QRPp) ..... 36, Oct.
Designing With Transistors (SSTV)
Emitter Followers ..... 44, Feb.
Low Gain Amplifiers ..... 38, March
High Gain A.C. Amplifiers ..... 42, Apr.
Discrete and IC Timers (MATH'S NOTES) ..... 64, Apr.
Filter Design By Frequency/Impedance Scaling (COP'S COLUMN) ..... 31, Oct.
Solid State Switching Methods (MATH'S NOTES) ..... 48, May
Synthesized Variable Frequency Oscillator, Design Thoughts (MATH'S NOTES) ... 50, March
Using Field Effect Transistors (MATH'S NOTES) ..... 36, Sept.
Worst-Case-Analysis, or "It Doesn't Work!" (Kasser, G3ZCZ/W3) ..... 29, March

NOVICE AND BEGINNER

Alternating Currents (NOVICE SHACK) .. 53, June
Calling "CQ" (NOVICE SHACK) ..... 57, Feb.
Capacitor Fundamentals (NOVICE SHACK) ..... 62, Sept.
Correction ..... 30, Nov.
Code Practice Before and After the Novice Test (NOVICE SHACK) ..... 51, Jan.
Electron Theory (NOVICE SHACK) ..... 54, May
Phantom Copying, A Transitional Step to QRQ (D'Onofrio, W2PRO) ..... 21, June
Sending And Receiving QSL Cards (NOVICE SHACK) ..... 58, March
Signal Strength and S-Meter Readings (NOVICE SHACK) ..... 66, Apr.
Simple Antennas for the Novice (NOVICE SHACK) ..... 31, July

POWER SUPPLY

Dual 15 Volt Power Supply
(MATH'S NOTES) ..... 68, Jan.
Simple, Super-Regulated 12 Volt Supply
(Clarke, K4JYM) ..... 61, Apr.

PROPAGATION

Short-Term Predictions for Ionospheric Propagation (Cohen, W4UMF) ..... 27, Sept.
Sunspot Cycle, The, Analysis and Prediction
(Cohen, W4UMF, and Lintz) .... 24, March

RECEIVERS AND RECEIVING

AN/ARN-14 Navigation Receiver
(SURPLUS SIDELIGHTS) ..... 68, Dec.
AN/ARR-52 VHF FM Receiver
(SURPLUS SIDELIGHTS) ..... 58, Oct.
Collins R-648/ARR-41 Receiver
(SURPLUS SIDELIGHTS) ..... 69, May
Direct Conversion Receiver Characteristics
(QRPp) ..... 48, March; 56, June
FET Conversion of R.F. or I.F. Amplifier
(MATH'S NOTES) ..... 27, Oct.
Incremental Tuning for Simple Transceivers
(QRPp) ..... 50, Apr.
R-392/URR Receiver
(SURPLUS SIDELIGHTS) ..... 64, Nov.

RTTY

Index of Military RTTY Test Sets
(SURPLUS SIDELIGHTS) ..... 70, March
RTTY Machine Models Described
(SURPLUS SIDELIGHTS) ..... 68, Feb.
Stelma DAC-V RTTY Test Set
(SURPLUS SIDELIGHTS) ..... 87, Apr.
Surplus RTTY Equipment: What's Available?
(SURPLUS SIDELIGHTS) ..... 76, Jan.
Teletype Model 28 Stunt Box
(SURPLUS SIDELIGHTS) .... 67, June; 68, July; 65, Aug.
TS-383/GG or Teletype DXD RTTY Test Set
(SURPLUS SIDELIGHTS) ..... 69, March

SLOW SCAN TELEVISION

Line-to-Line Jitter: Causes and Cures
(COP'S COLUMN) ..... 50, Sept.
Simultaneous Voice and SSTV Transmission
(COP'S COLUMN) ..... 41, May
SSTV Frequency Spectrum, The
(SSTV) ..... 48, Jan.
SSTV Keyboard, An
(Suding, WØLMD) ..... 20, Sept.

SPACE COMMUNICATIONS

OSCAR News
(Smith, VE2BYG) ..... 27, Apr.; 27, June
OSCAR News and Orbital Data
(Jacobs, W3ASK) ..... 40, Feb.
OSCAR-7 Should Be In Orbit This Month
(October 1974) (Jacobs, W3ASK) .. 17, Oct.

SURPLUS

AN/ARN-14 Navigation Receiver
(SURPLUS SIDELIGHTS) ..... 68, Dec.
AN/ARR-52 VHF FM Receiver
(SURPLUS SIDELIGHTS) ..... 58, Oct.
Collins R-648/ARR-41 Receiver
(SURPLUS SIDELIGHTS) ..... 69, May
R-392/URR Receiver
(SURPLUS SIDELIGHTS) ..... 64, Nov.
Surplus RTTY Equipment: What's Available?
(SURPLUS SIDELIGHTS) ..... 76, Jan.

TEST EQUIPMENT AND MEASUREMENTS

FET's In High-Z Volt-Ohmmeters
(MATH'S NOTES) ..... 26, Oct.
Impedance Measurements At Radio Frequencies
(Nagle, K4KJ) ..... 18, Nov.
Index of Military RTTY Test Sets
(SURPLUS SIDELIGHTS) ..... 70, March
$HB(S+1) + C^2 =$ Counters: Homebrew Counters from Surplus Parts
(Fincutter, K3STU) ..... 22, Jan.
QRP In-Line Wattmeter/SWR Bridge
(QRPp) ..... 42, Jan.
Scaler for Frequency Counters, A Solid State
(Peck, W3CRG) ..... 24, Apr.
Solid State Component Curve Tracer, An Accurate (Klappenberger, K3KWX) ... 20, July
Stelma DAC-V/RTTY Test Set
(SURPLUS SIDELIGHTS) ..... 87, Apr.
S.W.R. Bridge from Surplus Directional Coupler
(MATH'S NOTES) ..... 43, July
TS-383/GG or Teletype DXD RTTY Test Set
(SURPLUS SIDELIGHTS) ..... 69, March
Two-Tone Generator, A One Chip
(Olson, W6GXN) ..... 48, Apr.

TRANSMITTERS AND TRANSMITTING

Contest Rig for 160, A
(Webb, W4YDK) ..... 26, Jan.
R.F. Interference
(COP'S COLUMN) ..... 36, Nov.; 40, Dec.

VHF, UHF and FM

AN/ARR-52 VHF FM Receiver
(SURPLUS SIDELIGHTS) ..... 58, Oct.
Field Intensity Vs. Output Power and Antenna Heights ('JUP On FM) ..... 45, May
Handy-Talkie Operation In Aircraft
('JUP On FM) ..... 30, June
Phelps Dodge 5/8 Wave Antenna for 2m.
(MATH'S NOTES) ..... 25, Aug.
Seven-Element 2m. Beam
(ANTENNAS) ..... 44, March
Simple Gain Antenna for 2m.
(ANTENNAS) ..... 42, March

READER SERVICE

To obtain literature from advertisers, simply check the number next to the name of each advertiser listed below whose product or service is of interest to you.

DECEMBER, 1974

1 Allied Electronics
2 Amateur Electronic Supply
3 Antenna Specialists Co.
4 Aramco Services Company
5 Atlas Radio Inc.
6 Christie, R.
7 Cush-Craft Corporation
8 DX Engineering
9 Datak Corp., The
10 Dentron Radio Co.
11 Ehrhorn Technological Operations, Inc.
12 Eimac, Div. of Varian
13 Electronic Distributors, Inc.
14 Electronic Equipment Bank, Inc.
15 Electronics Center, Inc.
16 Emergency Beacon Corp. (EBC)
17 Fair Radio Sales
18 Franke, Fred, Inc.
19 G&G Radio Electronics Company
20 Gem Quad Products
21 Genave
22 H & L Associates
23 Heath Company
24 Henry Radio
25 Hewlett-Packard
26 Hy-Gain Electronics Corp.
27 International Crystal Mfg. Co.
28 Jan Crystals
29 KLM Electronics
30 Midland Electronics Company
31 Millen, James, Mfg. Co., Inc.
32 New-Tronics Corporation
33 Omega-T Systems, Inc.
34 Palomar Engineers
35 Queen City Electronics, Inc.
36 Ramco Electronics
37 SST Electronics
38 Scientific Radio Systems
39 Shure Brothers, Inc.
40 Space Electronics Co.
41 Sumner Electronics & Eng. Co., Inc.
42 Swan Electronics
43 Telrex Communication—Engineering Laboratories
44 Unadilla Radiation Products
45 VHF Engineering
46 Wirex, Inc
47 World QSL Bureau
48 Yeasu Musen USA Inc.

CQ Reader Service
14 Vanderventer Ave.
Port Washington, N.Y. 11050

Name ..... Call .....

Street Address .....

City ..... State ..... Zip .....

ADVERTISER'S INDEX

Allied Electronics 88
Amateur Electronic Supply 77, 78
Antenna Specialists Co. 84
Aramco Services Company 84
Atlas Radio Inc. 21
Christie, R. 74
Cush-Craft Corporation 52
DX Engineering 79
Datak Corp., The 17
Dentron Radio Co. 82
Ehrhorn Technological Operations, Inc. 8
Eimac, Div. of Varian ..... Cov. IV
Electronic Distributors, Inc. 73
Electronic Equipment Bank, Inc. 76
Electronics Center, Inc. 32
Emergency Beacon Corp. (EBC) 20
Fair Radio Sales 69
Franke, Fred, Inc. 76
G&G Radio Electronics Company 69
Gem Quad Products 78
Genave 14, 15
Gregory Electronics Corp. 95
H & L Associates 69
Hal Communications Corp. 4
Heath Company ..... Cov. II, Card, 1, 2, 3
Henry Radio 12, 25
Hewlett-Packard 17
House of Power 74
Hy-Gain Electronics Corp. 6, 24
International Crystal Mfg. Co. 72
Jan Crystals 80
KLM Electronics 86
Midland Electronics Company 82
Millen, James, Mfg. Co., Inc. 10
New-Tronics Corporation 11
Omega-T Systems, Inc. 79
Palomar Engineers 84
Queen City Electronics, Inc. 81
Ramco Electronics 42
SST Electronics 52
Scientific Radio Systems 19
Shure Brothers, Inc. 18
Space Electronics Co. 69
Sumner Electronics & Eng. Co., Inc. 22, 23
Swan Electronics 83, 85, 87, 89, 91
Telrex Communication Engineering Laboratories 48
Ten-Tec, Inc. 16
Unadilla Radiation Products 86
VHF Engineering 88
Wirex, Inc. 80
World QSL Bureau 74
Yeasu Musen USA Inc. ..... Cov. III

SEND FOR NEW 1975 CATALOG

GREGORY ELECTRONICS CORP.

The FM Used Equipment People.

249 Route 46, Saddle Brook, N. J. 07662
Phone: (201) 489-9000

GENERAL ELECTRIC T.P.L. SOLID STATE TWO-WAY RADIOS

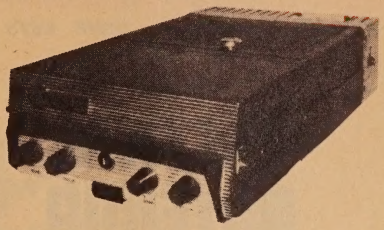

(Specify frequency range)
FE/RE 52, JA1, 2, or 3 series, 25-50 MHz, 12 volts, 35 watts, front or rear mount, fully solid state receive, 3 tubes in transmitter, fully narrow band, complete with accessories **$178**

FE/RE 53, JA6 series, 150-174 MHz, 12 volts, 35 watts, front or rear mount, fully solid state receive, 4 tubes in transmitter, fully narrow band, complete with accessories **$198**

(specify frequency range)
FE/RE 72, JA1, 2, or 3 series, 25-50 MHz, 12 volts, 100 watts, front or rear mount, fully solid state receive, 4 tubes in transmitter, fully narrow band, complete with accessories **$288**

FE/RE 73, JA6 series, 150-174 MHz, 12 volts, 80 watts, front or rear mount, fully solid state receive, 3 tubes in transmitter, fully narrow band, complete with accessories **$298**

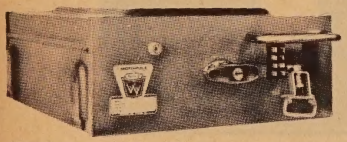

T53GGD, 150-170 MHz., 6/12 volt, 50 watts, dynamotor power supply, transmit narrow band, receive wide band, less accessories **$28**

MOTOROLA

T51G or T51GGV, 40-50 MHz., 6 or 12 volt, 50 watts, vibrator power supply, fully narrow band, less accessories **$58.00**

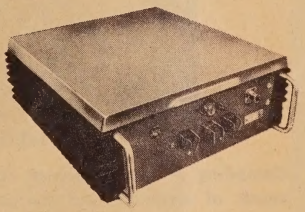

R.C.A.

CMFT50, 25-54 MHz., 12 volt, 50 watts, transistorized power supply, partially transistorized receiver, fully narrow band with accessories **$118.00**

CMCT30, 150-170 MHz., 12 volt, 30 watts, transistorized power supply, fully narrow band, complete with accessories **$98.00**

TECHNICIAN SPECIAL

G.E. Voice Commander 3, 132-150 MHz or 150-174 MHz, 1 watt, all solid state, hand-held portable. NOT IN WORKING CONDITION, but complete, less batteries, with bottom housing ..... $35.
Charger for above unit $7.50
Voice Commander service manual $5.
Carrying case ..... $2.

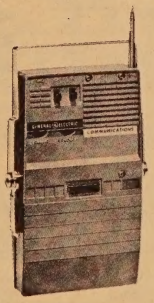

Two Exciting New Books From the Publisher of CQ

from Capt. Paul H. Lee, USNR, K6TS (ex-W3JHR)

THE VERTICAL ANTENNA HANDBOOK

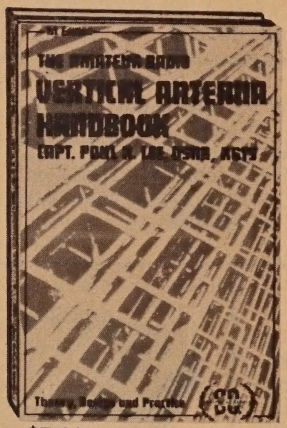

$5.00 postpaid USA.

Compiling in one reference source 22-years-worth of material from the pages of *CQ* on vertical antenna theory, design, installation, construction. Covers vertical arrays, feeding and matching, short verticals, ground effects, multi-band and single-band verticals, and answers many of the most commonly-asked questions about vertical antennas for the amateur. 6" X 9" 136 pages.

from John Shultz, W2EEY

THE Short Wave Listener's Handbook

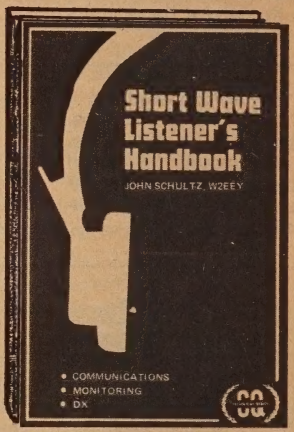

$5.00 postpaid USA.

Whether you're an amateur, an s.w.l. or just like to evesdrop on police and fire department calls, you'll find this new book to be the complete source for information on frequency assignments, radio propagation, transmission modes, antennas, receiver design and operation, large-scale receiving installations, transmission schedules, test equipment and procedures...in short, all you need to know about every aspect of receiving. 6" X 9" 152 pages.

CQ Magazine
14 Vanderventer Avenue, Port Washington, N.Y. 11050

(516) 883-6200

Please send me ..... copies of ☐ The Vertical Antenna Handbook ☐ The Short Wave Listener's Handbook. Enclosed is ☐ Check ☐ Money Order for $..... .

Name _____

Address _____

City _____ State _____ Zip _____

seasons greetings

Advanced communications equipment for the discriminating Amateur..... Available from these leading dealers.

ABC COMMUNICATIONS
17541 15th Avenue NE
Seattle, Washington 98155
206-364-6410

ADIRONDACK RADIO SUPPLY
185 W. Main Street
Amsterdam, New York 12010
518-842-8350

AMATEUR ELECTRONIC SUPPLY
4828 W. Fond du Lac Avenue
Milwaukee, Wisconsin 53216
414-442-4200

AMATEUR ELECTRONIC SUPPLY
621 Commonwealth Avenue
Orlando, Florida 32003
305-894-3238

AMATEUR ELECTRONIC SUPPLY
17929 Euclid Avenue
Cleveland, Ohio 44112
216-486-7330

BURGHARDT AMATEUR CENTER
124 First Avenue NW
Watertown, South Dakota 57201
605-886-7314

COMMUNICATIONS HEADQUARTERS
930 W. Washington Street
San Diego, California 92103
714-298-0680

CONLEY RADIO SUPPLY
405 N. 24th Street
Billings, Montana 59101
406-259-5554

CW ELECTRONICS
1401 Blake Street
Denver, Colorado 80202
303-244-5529

ED JUGE ELECTRONICS
3850 S. Freeway
Fort Worth, Texas 76110
817-926-5221

ELECTRONIC INTERNATIONAL SERVICE CORP.
11305 Elkin Street
Wheaton, Maryland 20902
301-946-1088

FRECK RADIO SUPPLY
68 Biltmore Avenue
Ashville, North Carolina 28807
704-254-9551

GRAHAM ELECTRONICS
133 S. Pennsylvania Street
Indianapolis, Indiana 46204
317-634-8486

HAM RADIO CENTER
8342 Olive Blvd.
St. Louis, Missouri 63732
800-325-3636

HAM RADIO OUTLET
999 Howard Avenue
Burlingame, California 94010
415-342-5757

HAMTRONICS
4033 Brownsville Road
Trevose, Pennsylvania 19047
215-357-1400

HARRISON RADIO
20 Smith Street
Farmingdale, L.I. New York 11735
516-293-7990

HENRY RADIO
11240 W. Olympic Blvd.
Los Angeles, California 90064
213-272-0861

HONOLULU ELECTRONICS
819 Keeaumoku Street
Honolulu, Hawaii 96814
808-949-5564

OREGON HAM SALES
409 W. First Avenue
Albany, Oregon 97321
503-926-4591

QUEEN CITY ELECTRONICS
7404 Hamilton Avenue
Cincinnatti, Ohio 45231
513-931-1577

QUEMENT ELECTRONICS
1000 S. Bascom Ave.
San Jose, California 95128
408-998-5900

RACOM ELECTRONICS
15051 S.E. 128th Street
Renton, Washington 98055
206-255-6656

RADIO INC.
1000 S. Main
Tulsa, Oklahoma 74119
918-587-9123

VICKERS ELECTRONICS
506 E. Main Street
Durham, North Carolina 27702
919-683-1597

WEBSTER RADIO
2602 Ashlan
Fresno, California 97326
209-224-5111

WILSON ELECTRONICS
4784 Boulder Highway
Las Vegas, Nevada 89044
702-451-5791

Specifications subject to change without notice.

YAESU

YAESU
MUSEN USA INC.

Visit your dealer for details or write for our new catalog.

All Yaesu products warranted by the selling dealer. Complete after-warranty service available in Paramount, Calif.

7625 E. Rosecrans Avenue, Unit #29 Paramount, California 90723 (213) 633-4007

EIMAC provides reliability year after year–and now offers a 3,000 hour warranty.

For years, the industry-wide standard warranty for power grid tubes has been 1,000 hours.

For years, the operating lifetimes of EIMAC tubes have exceeded this warranty — reducing down-time and boosting on-the-air time in thousands of transmitters. So, EIMAC offers a new warranty policy for 81% of all standard power grid tubes: 3,000 hours/1 year, with prorated adjustment from 300 to 3,000 hours. Failure during the first 300 hours results in complete replacement.

This warranty is a direct result of reliability that has been built into every EIMAC product for the past 40 years. Our 3,000 hour warranty stands as proof.

For details about which tube types are covered by the new warranty, contact EIMAC, Division of Varian, 301 Industrial Way, San Carlos, California 94070. Or any of the more than 30 Varian/EIMAC Electron Device Group Sales Offices throughout the world.

Eimac®
division
varian